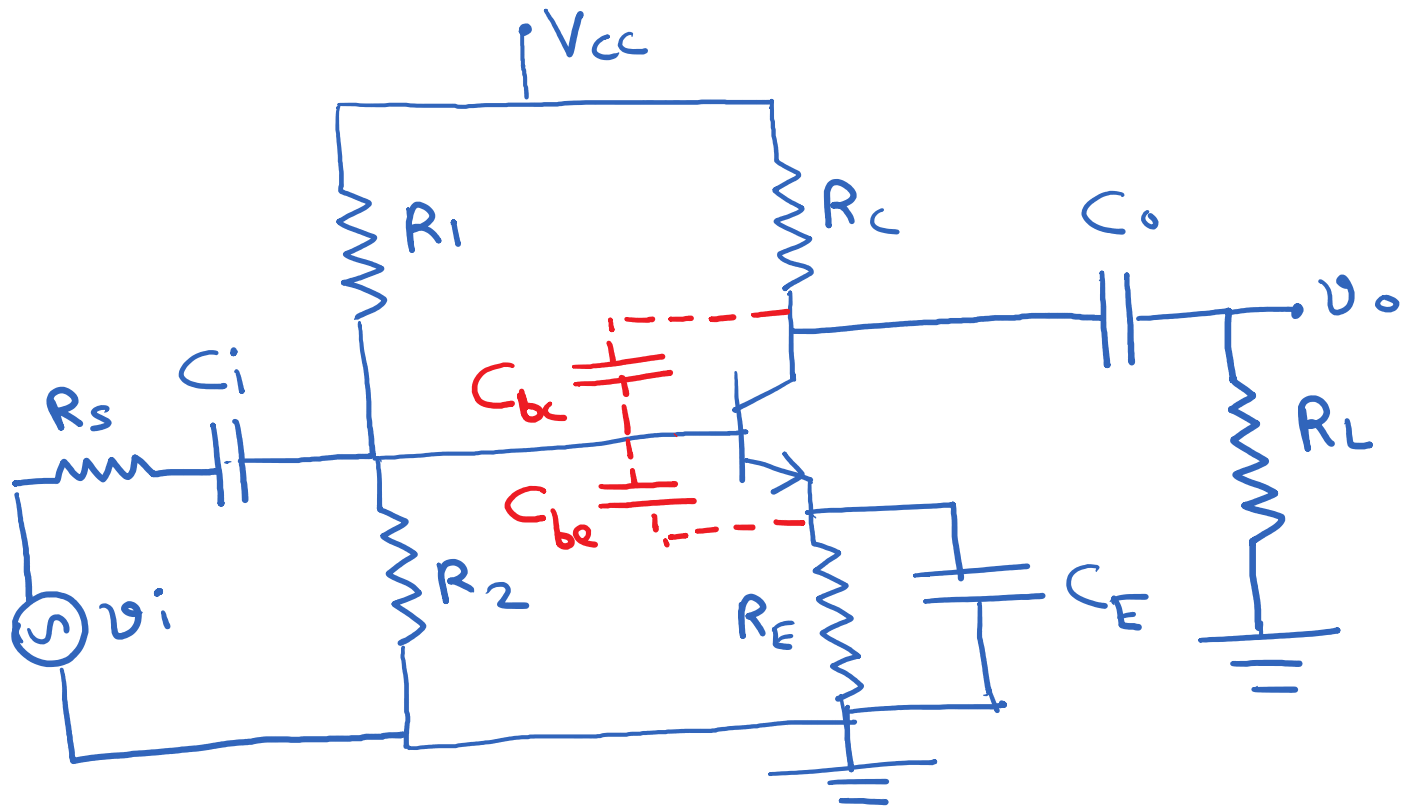


Class-24

Hybrid π -model




$C_i, C_o, C_E \rightarrow$ externally connected capacitors.
 $C_{bc}, C_{be} \rightarrow$ internal junction capacitances of the transistor.

Frequency response defines how the gain of the transistor amplifier is behaving with change of frequency.


The gain that we calculate assuming C_i , C_E and C_o behave as short circuits and C_{be} and C_{bc} behave as open circuits is known as mid-band frequency gain or mid-band gain. This is often denoted by A_o or A_v^o .


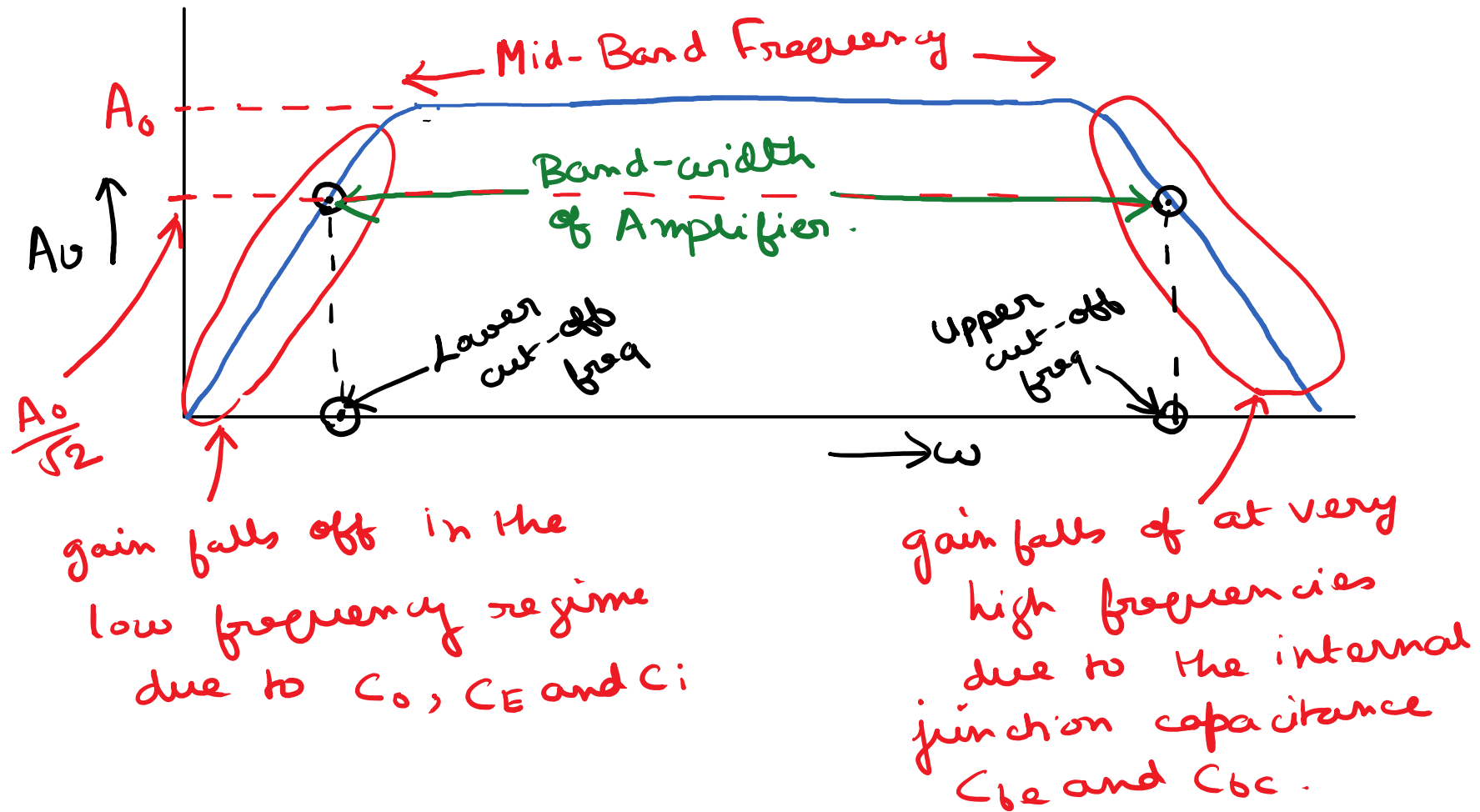
The range of frequency over which C_i , C_o and C_E can be considered to be short-circuits and C_{be} and C_{bc} can be considered to be open-circuits is known as the mid-band frequency range.



$$R_i, A_v = \frac{v_o}{v_i}$$

$$A_i = \left| \frac{i_L}{i_s} \right|$$

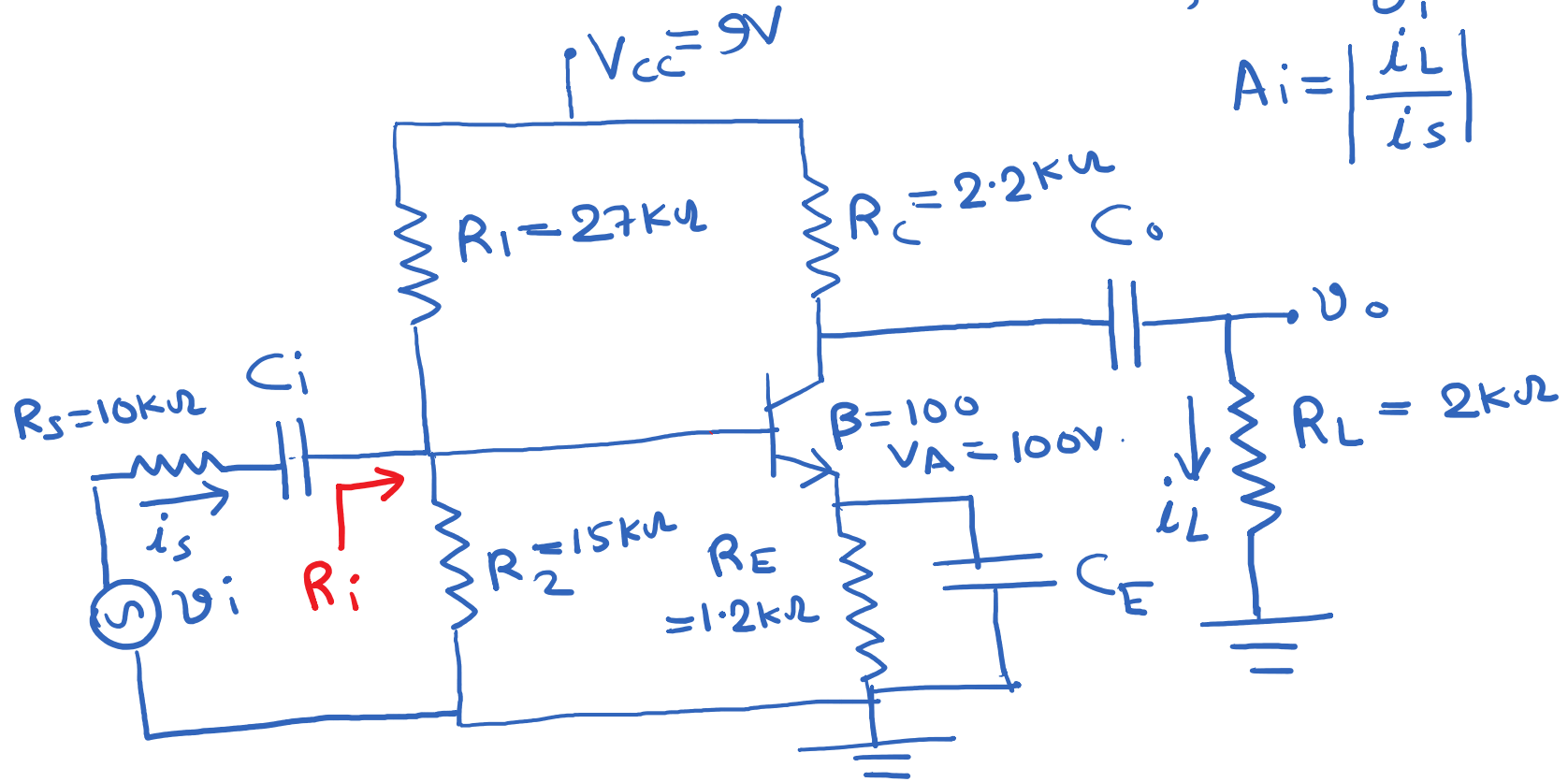

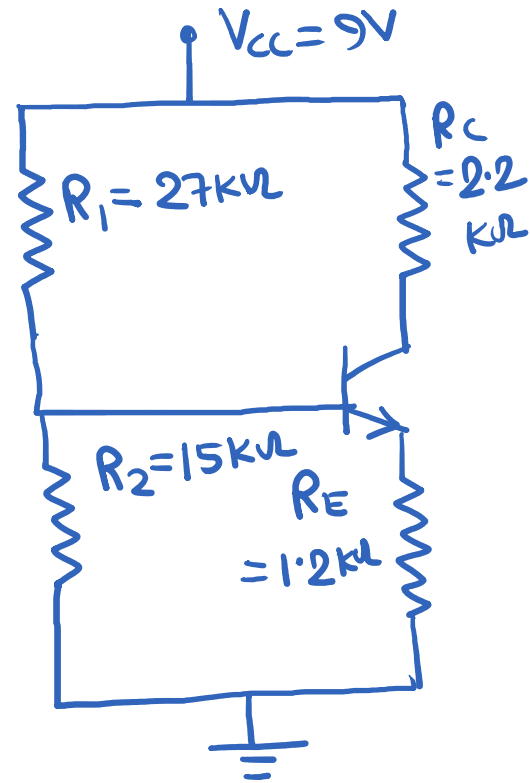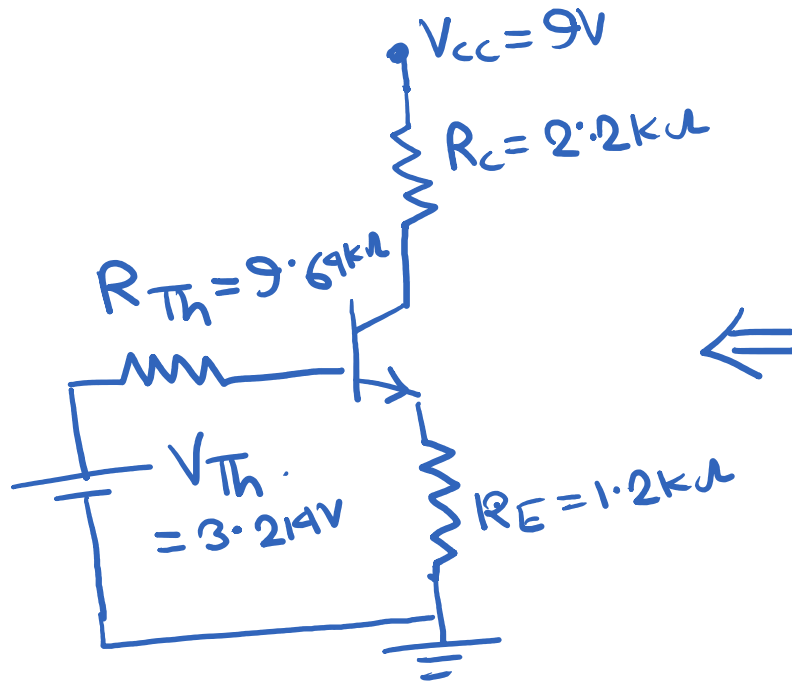

$$V_{Th} = \frac{R_2}{R_1 + R_2} \times V_{CC} = \frac{15}{27 + 15} \times 9V = 3.214V$$

$$R_{Th} = R_1 \parallel R_2 = \frac{15 \times 27}{15 + 27} k\Omega = 9.69k\Omega$$

$$V_{Th} = I_B R_{Th} + V_{BE(ON)} + I_E R_E$$

$$= 9.64 I_B + 0.7V + (\beta + 1) I_B \times 1.2$$


$$\Rightarrow I_B = \frac{V_{Th} - 0.7}{9.64 + (\beta + 1) \times 1.2} \text{ mA}$$

$$= \frac{3.214 - 0.7}{9.64 + 101 \times 1.2}$$

$$= 0.0192 \text{ mA}$$

$$I_C = \beta I_B = 100 \times 0.0192 \text{ mA}$$

$$= 1.92 \text{ mA}$$

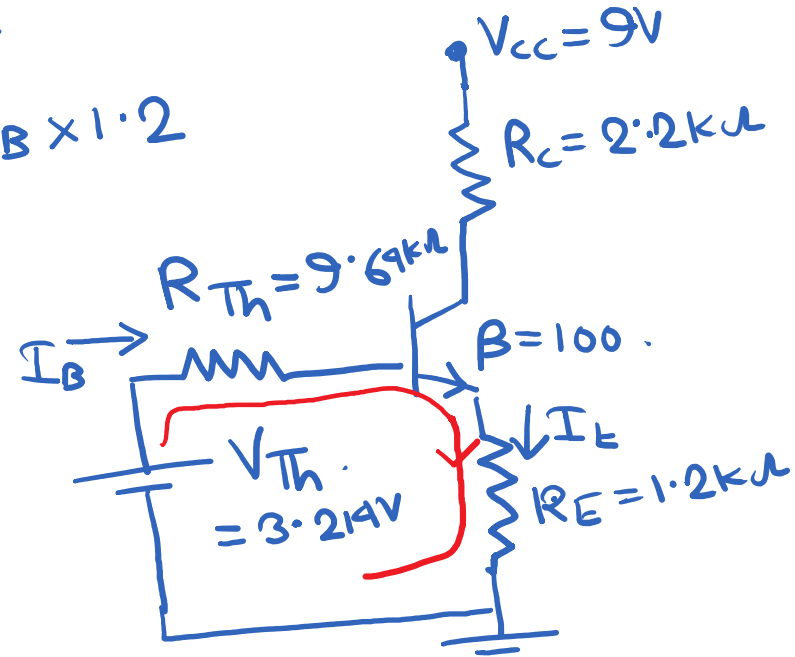


AC
on small
signal
parameters

$$r_{\pi} = \frac{V_T}{I_B} = \frac{0.026V}{0.0192mA} = 1.354k\Omega$$

$$g_m = \frac{\beta}{r_{\pi}} = \frac{100}{1.354k\Omega} = 73.85 \text{ milli-mho.}$$
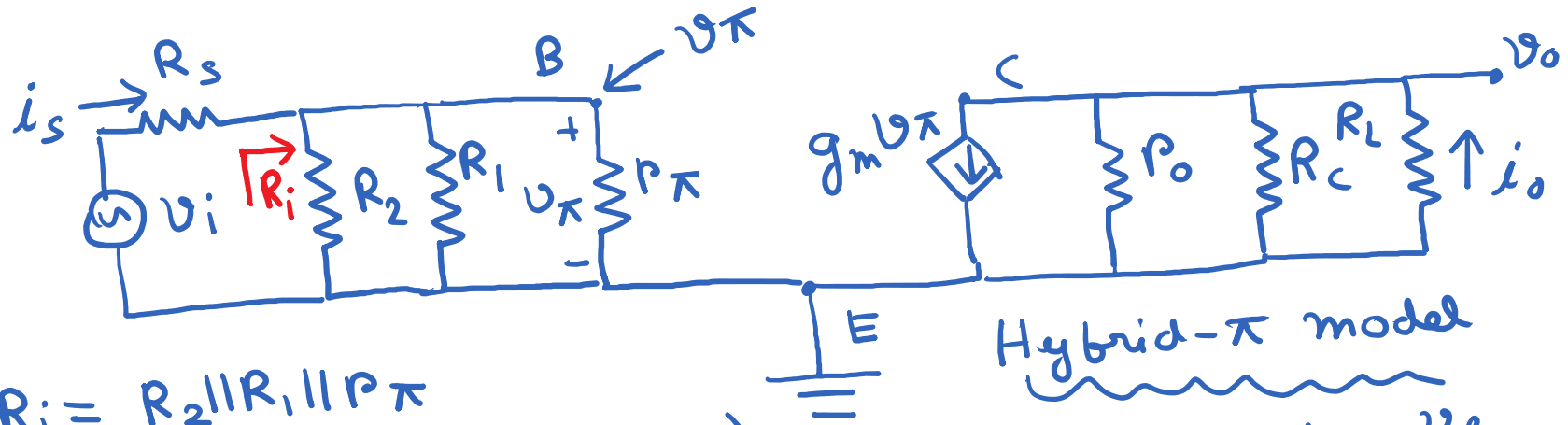
$$r_o = \frac{V_A}{I_C} = \frac{100V}{1.92mA} = 52.08k\Omega.$$



$$R_i = R_2 \parallel R_1 \parallel r_\pi$$

$$= (15\text{ k}\Omega \parallel 27\text{ k}\Omega \parallel 1.35\text{ k}\Omega)$$

$$= 1.187\text{ k}\Omega$$


$$v_\pi = \frac{v_i}{R_s + R_i} \times R_i$$

$$= v_i \times \frac{1.187}{10 + 1.187}$$

$$= 0.106 v_i$$

$$i_o = \frac{v_o}{R_L}$$

$$i_s = \frac{v_s}{R_s + R_i}$$

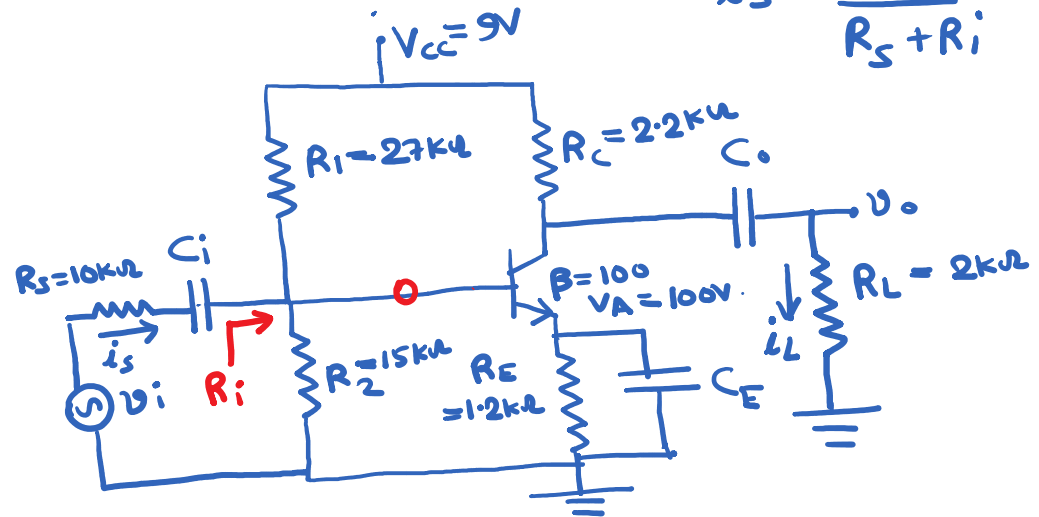

$$R_i = 1.187 \text{ k}\Omega, \quad v_\pi = 0.106 \text{ V}_s$$

$$i_c = g_m v_\pi$$

$$v_o = -i_c \times (r_o \parallel R_c \parallel R_L)$$

$$= -g_m v_\pi (r_o \parallel R_c \parallel R_L)$$

$$= -v_\pi \times 73.85 \text{ milli-mho}$$

$$\times (52.08 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega \parallel 2 \text{ k}\Omega)$$

$$= -v_\pi \times 73.85 \text{ milli-mho} \times 1.027 \text{ k}\Omega$$

$$= -75.84 v_\pi = -75.84 \times 0.106 \text{ V}_s$$

$$= -8.039 \text{ V}_s$$

$$A_v = \frac{v_o}{v_s} = -8.039$$

$$A_i = \left| \frac{i_o}{i_s} \right|$$

$$i_o = \frac{v_o}{R_L}, \quad i_s = \frac{v_s}{R_s + R_i}$$

$$\begin{aligned} \Rightarrow A_i &= \left| \frac{i_o}{i_s} \right| = \left| \frac{v_o}{v_s} \right| \times \frac{R_s + R_i}{R_L} \\ &= |A_v| \times \frac{10 + 1.187}{2} \\ &= 8.039 \times \frac{11.187}{2} \\ &= 44.96. \end{aligned}$$

$$R_i = 1.187 \text{ k}\Omega, \quad A_v = -8.039, \quad A_i = 44.96.$$