

**Department of Electronics and Electrical Communication Engineering,  
Indian Institute of Technology Kharagpur**


<b>Class test-4, Basic Electronics (EC21101), Total marks: 40</b>	<b>Duration: 10-10:45 am 45 mins including the uploading of the answers</b>	<b>Date: 01.04.2021</b>
---	---	-------------------------

**Kindly provide the solution of all sub-parts of a question at one place. A single file (.doc/pdf/zip) to be uploaded for all answers. There are four questions with sub-parts indicated.**


**Q1.** Consider a process technology for which  $\frac{W}{L} = 10$ ,  $t_{ox} = 8 \text{ nm}$ ,  $\mu_n = 450 \frac{\text{cm}^2}{\text{V.s}}$ , and  $V_{TN} = 0.7 \text{ V}$  and  $\epsilon_{ox} = 3.9 \times 8.85 \times 10^{-14} \text{ F/cm}$ . **[1+1+2+2+2 marks]**

- From the given information identify the type of the MOSFET.
- Calculate the oxide capacitance per unit area of the device.
- Calculate the process conduction parameter for the device.
- If the device need to be operated in the ‘saturation’ region with a source current of  $100 \mu\text{A}$ , what should be the applied voltage between gate and source?
- What should be the minimum voltage applied across drain and source?

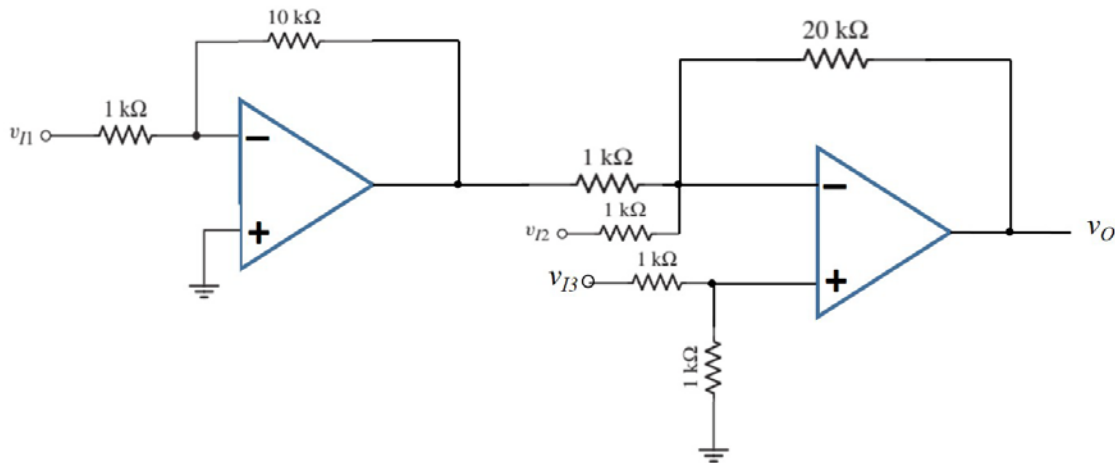**Q2.** For the Fig. shown below, derive and determine the output voltage of the circuit given below, where the op-amp is an ideal. Express in terms of input voltages. **[8 marks]**



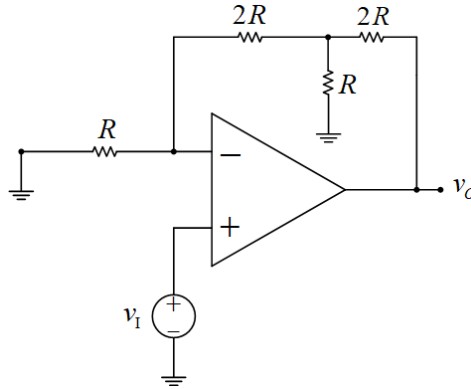**Q3.** Derive and obtain the gain  $A_v = v_o / v_i$  for the ideal circuit in the figure below : **[8 marks]**



**Q4.**

- (a) Obtain the small-signal parameters ( $g_m$ ,  $r_\pi$ ) of a BJT based CE amplifier circuit shown in figure below. The transistor parameters are  $\beta = 100$ ,  $V_{BE}(\text{on}) = 0.7 \text{ V}$ ,  $V_T = 26 \text{ mV}$ ,  $R_1 = 20 \text{ k}\Omega$ ,  $R_2 = 10 \text{ k}\Omega$ ,  $R_C = 3 \text{ k}\Omega$ ,  $R_{E1} = 1 \text{ k}\Omega$ ,  $R_{E2} = 1.1 \text{ k}\Omega$ ,  $C_C = C_E = 10 \mu\text{F}$  and  $V_{CC} = 12 \text{ V}$ . **[6 marks]**
- (b) Draw the hybrid- $\pi$  equivalent circuit if the Early voltage is very large. Also obtain input resistance,  $R_i$  and  $R_{ib}$ . **[2+2+1 marks]**
- (c) Obtain the gain of amplifier circuit when  $C_E$  is not connected. What happens to the gain when  $C_E$  is connected. **[3+2 marks]**

