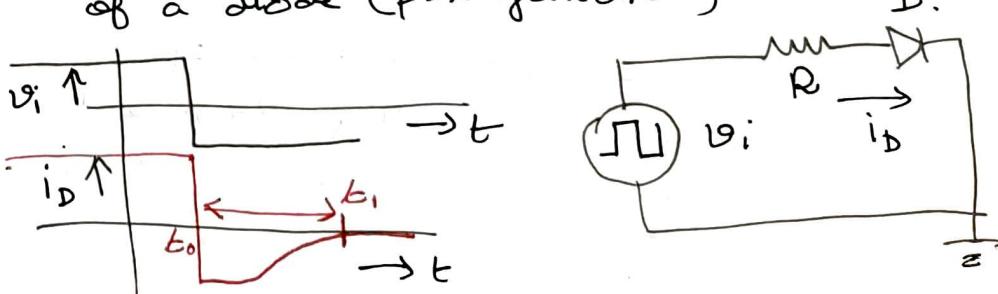


Ans 02  
 We have already noted that the capacitors  $C_i$  and  $C_o$  and  $C_E$  affect the low frequency response of the BJT amplifier. That is they decrease the gain. At low frequency  $C_i$  and  $C_E$  offers a finite impedance to the AC path. As a result the AC component of the voltage that drops across the base to emitter junction ( $V_{BE}$ ) decreases. This


AC component of decrease the base current which in turn decreases the collector current. Hence the gain decreases. The output coupling capacitor  $C_o$  on the other hand provides a finite impedance at the output in series with the load resistor  $R_L$ . Hence the AC component of the voltage drop across the load resistor decreases, thereby decreasing the gain magnitude. Hence, these three coupling capacitors are responsible for decreasing the gain <sup>in</sup> low frequency regime.

The gain in the high frequency regime on the other hand is affected by the junction capacitances of the transistor. To understand this, let us recall the switching characteristics of a diode (p-n junction)



As we already discussed earlier, in the time period between  $t_0$  and  $t_1$ , the current a high magnitude of the reverse current is possible. This current is used to remove the excess concentration of the minority carriers that is stored at near the depletion region and to induce/remove the charge to widen/thin the depletion region. So, ~~The point is that when t~~ As we discussed earlier in the class, the stored depletion charge and minority carriers ~~at~~ give a capacitive effect, ~~start~~ imitating the behaviour of a capacitor: the stored charge ~~or~~ and charge due to excess carriers need to be changed whenever the voltage changes. We have already noted that due to this effect, the small signal model of a diode is

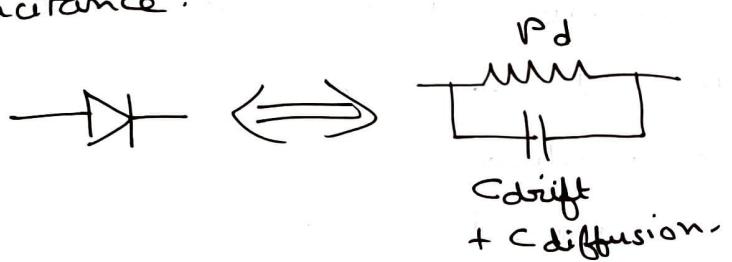given by the parallel combination of the diffusion resistance and the drift and depletion and diffusion capacitance.




It is clear from this model that when the AC signal changes slowly with respect to the minority carrier recombination time, the diode is always in steady state with the applied voltage and so the capacitor in the equivalent model acts more or less like an open circuit and the ~~the~~ AC current is mainly controlled by the diffusion resistance.

However, if the AC signal is of high frequency and change fast

with respect to the minority carrier recombination time, the diode is not in steady state with the applied voltage and now the current is mainly controlled by the parallel capacitance which acts as a short-circuit.

In a transistor ~~this~~ such capacitance capacitive behaviour lies at the junction: The base to emitter and the ~~emitter~~ base to collector junctions. The overall effect is that due to the capacitive behaviour the base-to-emitter junction becomes short-circuited and the magnitude of  $V_A$  decreases. which results in a decrease in the overall gain of the amplifier. The effect of the junction capacitance at the collector to emitter junction

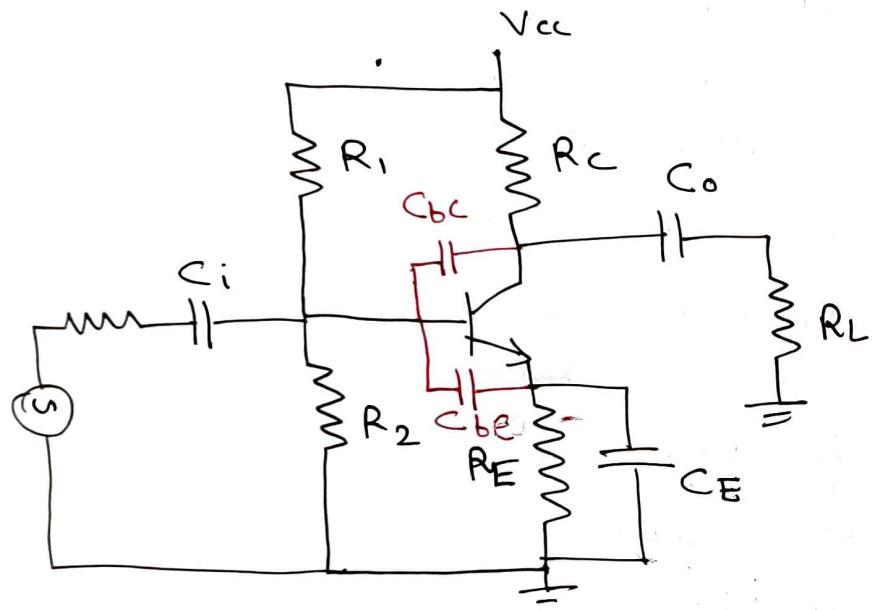may result in a current flow at the collector, which doesn't abide the relation  $i_c = \beta i_b$ .




The effect may be modeled, just as in the case of the diode, by introducing an effective capacitance between the base to emitter and the collector to emitter junction.

Note that the capacitance  $C_i$ ,  $C_o$  and  $C_E$  are externally introduced in the overall circuit. The

capacitors  $C_{be}$  and  $C_{bc}$ , on the other hand are not introduced externally. These are mainly modelling parameters and takes into account the effect of excess stored minority carriers and the stored depletion layer charge that needs to change every time the voltage changes. As can be noted at high frequency  $C_{be}$  may short-circuit the base to emitter junction resulting in a decrease of  $V_T$  which is the AC component of voltage drop across the base-emitter junction. Decrease in  $V_T$  results in decrease of  $i_c = g_m V_T$ , which in turn results in decrease of gain. The modelling parameter  $C_{be}$  and  $C_{bc}$  depend on the

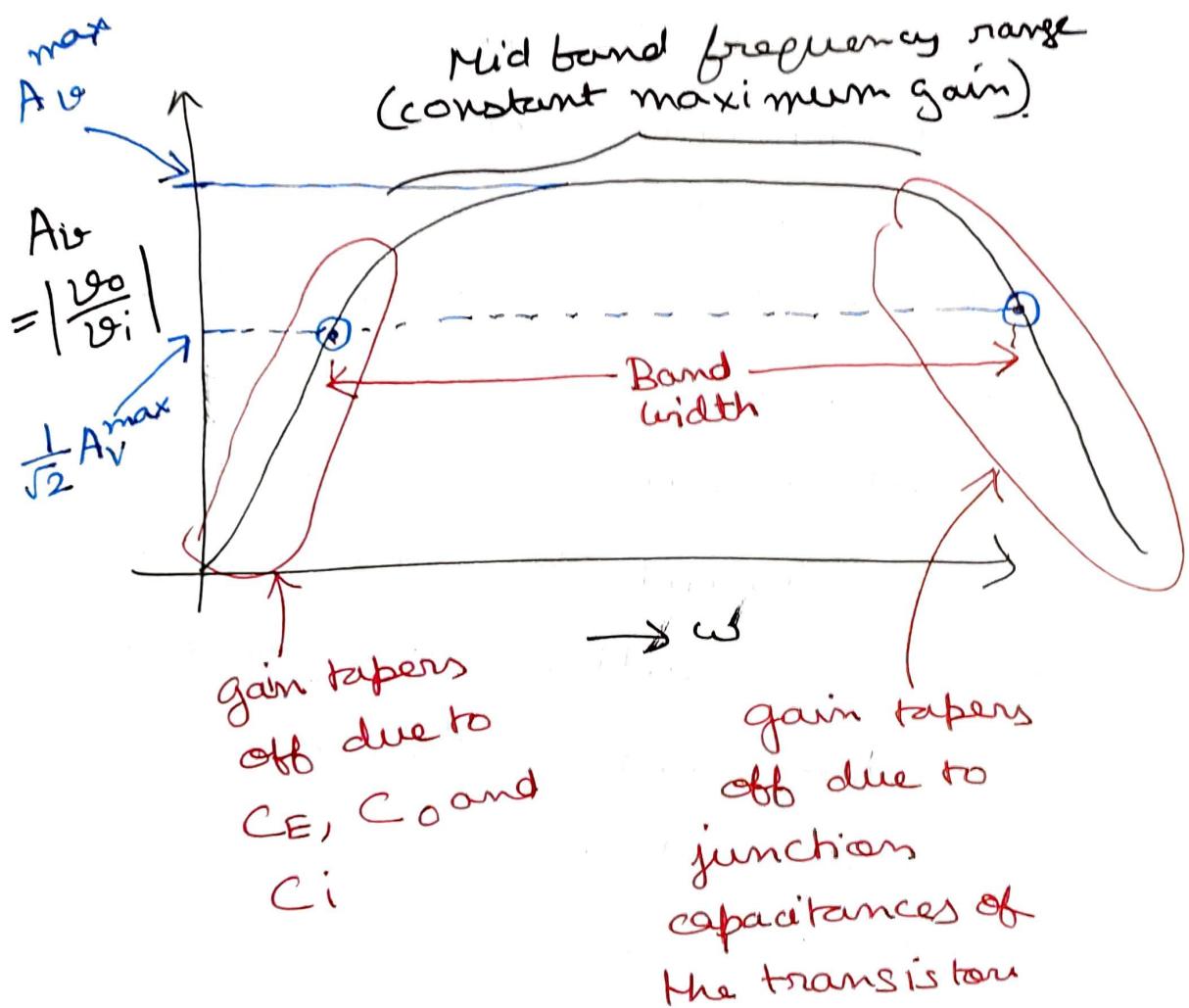minority carrier recombination time and loss to current can be controlled to some extent (although not always) via suitable fabrication steps.



The frequency difference between the points, at which gain is  $\frac{1}{\sqrt{2}}$  times the mid-band gain, is known as the Bandwidth of the amplifier.


6.25

$$\beta = 100, V_A = \infty$$

$$g_m, r_\pi, r_o = ?$$

$$A_{LQ} = \frac{290}{29}$$


$$A_i = \frac{i_o}{i_i}$$

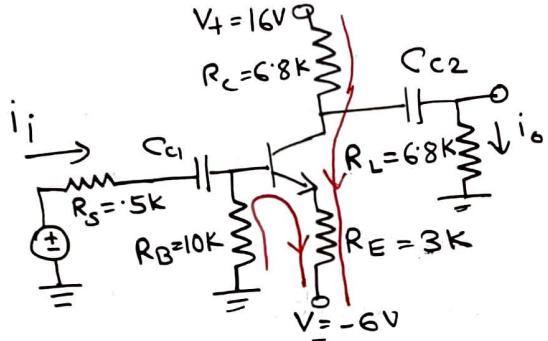

To find the gain, we need to find the small signal parameters of the amplifier, such as  $g_m$ ,  $r_\pi$  and  $r_o$ . To find these parameters, we first need to do a DC analysis of the circuit. This is because the ac or small signal parameters such as  $g_m$ ,  $r_\pi$  etc depend on the DC biasing point or the Q-point of the transistor amplifier.

For DC analysis, we can open circuit the paths containing capacitors because capacitors act as open circuits for DC voltage/currents. The red lines in the figure show the paths of DC currents. Hence

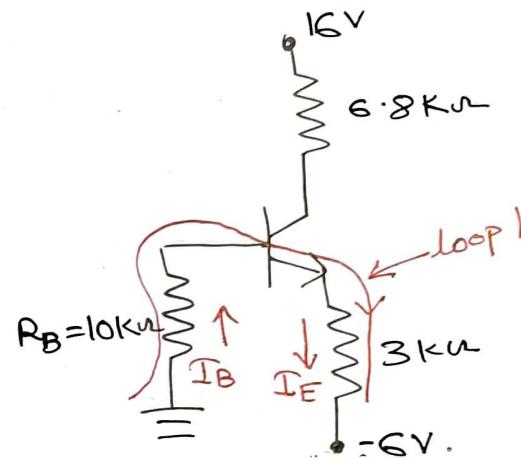for DC analysis, the circuit we need to analyze is the following.



We first analyze loop 1 which contains the base-emitter junction. Applying KVL, we get.

$$6V = I_B \times 10 + V_{BE(on)} + I_E \times 3$$

$$= 10I_B + 0.7 + 10I_E$$

$$\Rightarrow I_B = \frac{6-0.7}{31} \text{ mA} \approx 0.169 \text{ mA.}$$

$$I_E = 10I_B = 10 \times 0.169 \text{ mA.}$$

$$= 1.69 \text{ mA}$$

$$r_\pi = \frac{V_T}{I_B} = \frac{0.026 \text{ mV}}{0.0169 \text{ mA}} = 1.53 \text{ k}\Omega$$

$$g_m = \frac{\beta}{r_\pi} = \frac{100}{1.53 \text{ k}\Omega} = 65.35 \text{ millimho}$$

$$= 0.065 \text{ mho}$$



$$P_0 \approx \frac{V_A}{I_{CQ}} \approx \frac{V_A}{I_{EQ}} \rightarrow Q \approx$$

We have now found out the small signal parameters. Hence, we are now ready for AC analysis. For AC analysis we first derive the small signal model.

Let us recall that a

DC source cannot create AC current.

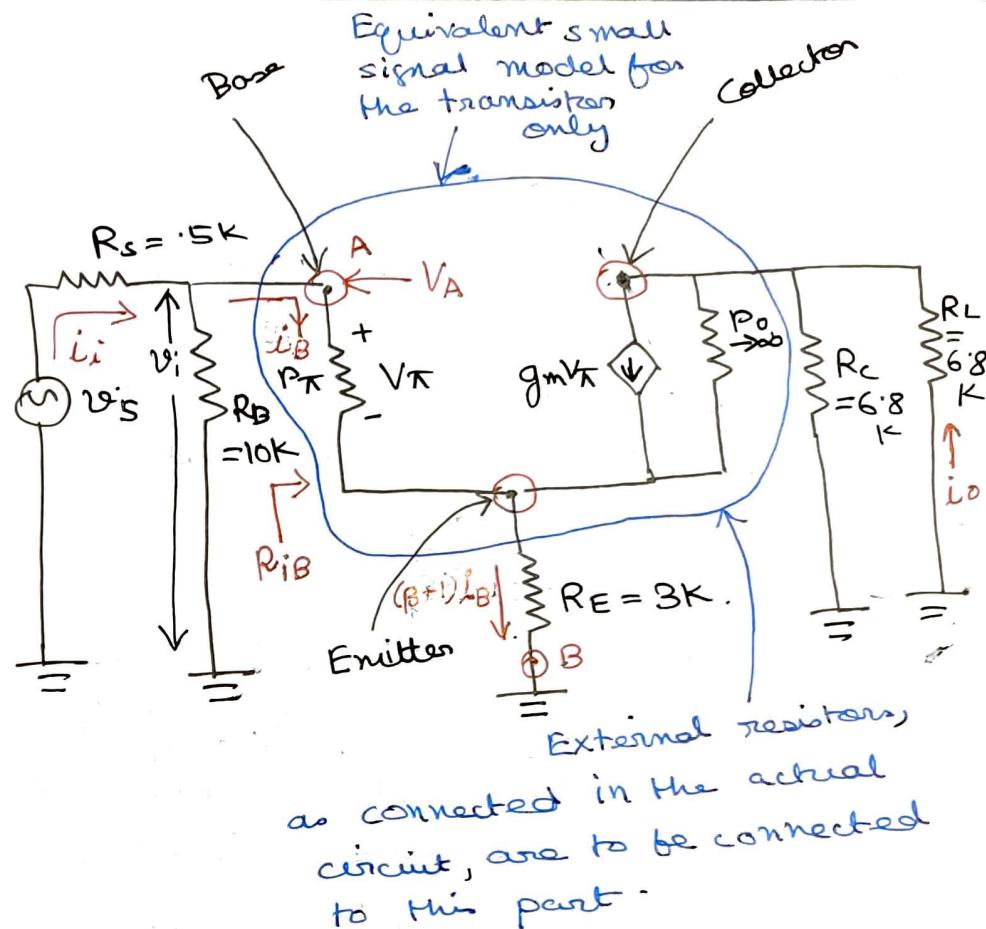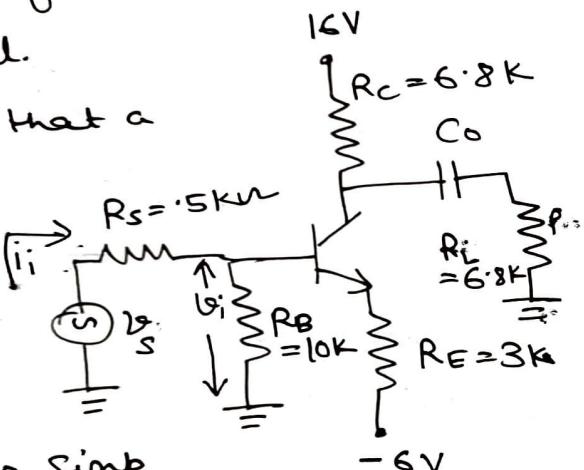Hence, the DC source points can only act as sink for ac currents and that's why we are good to go for AC analysis if we replace the DC source points with AC ground. So, in the small signal model we replace all the DC source points with AC grounds.



In this problem, the analysis is a little bit complicated since the emitter resistor  $R_E$  is not bypassed with a capacitor  $C_E$ . The problem lies in the fact that a current of magnitude  $i_B$  is flowing through  $R_\pi$ . But a current of magnitude  $(\beta + 1)i_B$  is flowing through  $R_E$ , which is in series with  $R_\pi$ .

Here one asks the question: what is the equivalent resistance seen when one looks into the base terminal. In other words, that what is the ratio of the voltage at the base terminal and the current flowing into the base terminal. That is, what is  $R_{iB} = \frac{V_A}{i_B}$ .

$V_A$  and  $i_B$  are shown in the figure. The parameter  $R_{iB} = \frac{V_A}{i_B}$  is known as the input resistance at the Base of the ~~amp~~ transistor.

We again write KVL for the base between the points A and B shown in the figure.

$$V_A = i_B r_\pi + (\beta + 1) i_B R_E$$

$$\Rightarrow \frac{V_A}{i_B} = r_\pi + (\beta + 1) R_E$$

$$\Rightarrow R_{iB} = r_\pi + (\beta + 1) R_E$$

It is noteworthy that the resistance  $R_E$  gets reflected as  $(\beta + 1) R_E$  in the input resistance at the Base due to different magnitudes of current flowing through  $r_\pi$  and  $R_E$ . This is known as the resistance reflection rule.

The total resistance, thus seen by the voltage source  $V_s$  is  $R_i = R_B \parallel R_{iB}$

$$= R_B \parallel [r_\pi + (\beta + 1) R_E]$$

$$R_s = 0.5 \text{ k}\Omega$$

$$R_B = 10 \text{ k}\Omega$$

$$R_{iB} = r_\pi + (\beta + 1) R_E$$

Also called  
the total input  
resistance of.  
 $= 1.535 \text{ k}\Omega + 101 \times 3 \text{ k}\Omega$   
 $= 304.535 \text{ k}\Omega$ .

The ~~R<sub>i</sub>~~ of the amplifier:  
 $R_i = \cancel{0.5 \text{ k}\Omega} + (10 \text{ k}\Omega \parallel 304.535 \text{ k}\Omega)$   
 $= \cancel{0.5 \text{ k}\Omega} + 9.682 \text{ k}\Omega$   
 $= \cancel{0.5 \text{ k}\Omega} + 9.682 \text{ k}\Omega$ .

The voltage between the points A and B  
 $V_{AB} = \frac{V_s}{R_s + R_i} \times (R_B \parallel R_{iB})$

$$= \frac{V_s}{10.182} \times 9.682$$

$$V_\pi = V_{AB} \times \frac{R_\pi}{R_{IB}}$$

$$= V_{AB} \frac{1.535}{304.535}$$

$$= V_s \times \frac{9.682}{10.182} \times \frac{1.535}{304.535}$$

$$= 0.00479 \text{ v}_s.$$

$$i_c = g_m V_\pi$$

$$= 0.0651 \times 0.00479 \text{ v}_s.$$

$$= 0.000311 \text{ v}_s.$$

Since  $R_o \rightarrow \infty$ , the output voltage  $v_o$  is given by:

$$v_o = -i_c (R_o \cdot R_C || R_L)$$

$$= \underline{-0.3}$$

$$= -0.000311 \text{ v}_s \times (6.8 \parallel 6.8) \text{ k}\Omega$$

$$= -1.0602 \text{ v}_s.$$

$$\Rightarrow \frac{v_o}{V_s} = -1.0602$$

The negative sign in front of the gain indicates phase inversion.

It should be noted that we use capital letters to denote DC signals while small letters (in italics) to denote AC signals. For example,  $I_B$  would generally denote the DC component or biasing component of the base current while  $i_B$  is used to denote the AC component of the base current.

Now, let us calculate  $|i_o/i_i|$ .

$$|i_o| = \left| \frac{v_o}{R_L} \right| = \left\{ \frac{g_m V_\pi \times (R_C || R_L)}{R_L} \right\}$$

$$= \underline{g_m V_\pi \times \frac{R_C}{R_C + R_L}}$$


$$= \underline{\frac{g_m V_\pi}{2}}$$

$$= \frac{1.0602 \text{ v}_s}{R_L}$$

$$|i_i| = \frac{V_s}{R_i + R_s}$$

$$\text{So, } \left| \frac{i_o}{i_i} \right| = \frac{1.062(R_i + R_s)}{R_L}$$
$$= \frac{1.062 \times 10.182 \text{ k}\Omega}{6.8 \text{ k}\Omega}$$
$$= 1.5901$$

Some information:

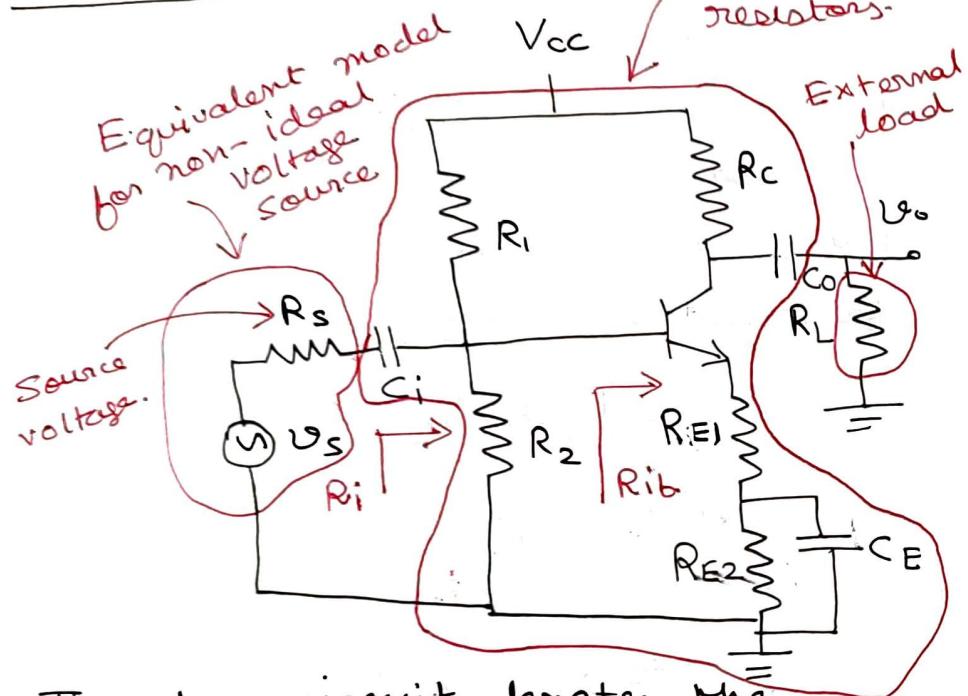

The above circuit denotes the ~~voltage~~-~~it~~ circuit of a practical (but simplest) BJT amplifier in voltage Divider configuration.

- i)  $R_s$  denotes the source resistance and generally can't be controlled.
- ii)  $V_{cc}$  is the biasing voltage and is used to bring the transistor in forward active mode.

iii)  $R_1$  and  $R_2$  are the base to emitter biasing resistors. These two resistors are used to choose or control the ~~ques~~ quiescent base current.  $I_{BQ}$  to some extent.

iv)  $R_c$  and  $R_E$ , on the other hand (and also  $R_E$  to some extent) can be used to choose the value of quiescent  $\Rightarrow$  collector to emitter voltage  $V_{CEQ}$ .

v) The capacitor  $C_i$  is used to prevent the DC current from flowing through  $v_s$ . This results in ~~un~~ necessary power wastage. Moreover, a high value of DC current, if allowed through  $v_s$ , may damage the  $v_s$  source (which may be a delicate electronic component).

vi)  $C_o$  is used to block any DC voltage across  $R_L$  because we only want the AC signal across the load.

vi)  $C_E$  is used to bypass the resistance  $R_{E2}$ .

This reduces the effective resistance seen by the AC path.

vii)  $C_i$ ,  $C_o$  and  $C_E$

The DC current through the emitter sees a resistance  $R_{E1} + R_{E2}$  at the emitter terminal. The emitter resistance is mainly used to stabilize  $I_{CQ}$  and  $V_{CEQ}$  against variation in  $\beta$ . This can be understood by the following Eqs.

$$\begin{aligned} V_{Th} &= I_B R_{Th} + V_{BE(ON)} \\ &\quad + \frac{1}{\beta} I_{CQ} (R_{E1} + R_{E2}). \end{aligned}$$

Equation of KVL for DC current and DC voltage

$$\begin{aligned} \Rightarrow V_{Th} &= -V_{BE(ON)} \\ &= I_{BQ} R_{Th} + (\beta+1) I_{BQ} (R_{E1} + R_{E2}) \\ \Rightarrow I_{BQ} &= \frac{V_{Th} - V_{BE(ON)}}{R_{Th} + (\beta+1)(R_{E1} + R_{E2})} \end{aligned}$$

$$\begin{aligned} I_{CQ} &= \beta I_{BQ} = \\ &= (V_{Th} - V_{BE(ON)}) \times \frac{\beta}{R_{Th} + (\beta+1)(R_{E1} + R_{E2})} \end{aligned}$$

If  $\beta \gg 1$ ,

$$I_{CQ} \approx \frac{V_{Th} - V_{BE(ON)}}{R_{E1} + R_{E2}}.$$

So,  $I_{CQ}$ , and hence  $V_{CEQ}$  does not depend on  $\beta$  and thus the Q-point is stabilized against any variation in  $\beta$ .

viii) It can be seen that  $C_E$  bypasses (for AC signals) a part of the emitter. The resistance  $R_{E1}$  is intentionally left in the AC path. This resistor stabilizes the AC gain of the transistor against any variation in  $\beta$ . It can be shown that if  $\beta \gg 1$ , the AC gain  $A_{vA} \approx -\frac{R_C}{R_E}$  (see section 6.4.2)

ix) The input base resistance  $R_{IB}$  is defined as the resistance seen looking into the base of the transistor. Ask the question:- If the voltage at the base of the transistor increases

by an amount  $\Delta V_B$ , what is the increase in base current  $\Delta I_B$ . The input base resistance relates  $\Delta V_B$  to  $\Delta I_B$  as:-

$$\Delta V_B = R_{IB} \Delta I_B.$$


We already discussed that

$$R_{IB} = P_T + (\beta + 1) R_{E1}$$

Note that the input base resistor is defined only for AC signals. So, the resistance  $R_{E2}$  is not considered (because it is bypassed).

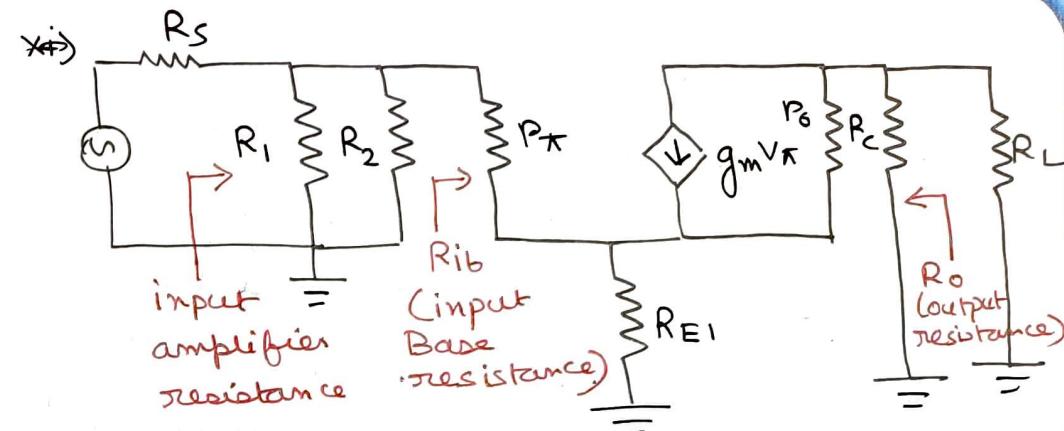x) The input resistance to the amplifier is the resistance seen by the AC source, so,  $R_s$  is left out (because  $R_s$  is a part of the AC source). The resistance seen by the AC source (discussed earlier) is

$$R_i = (R_1 \parallel R_2 \parallel R_{IB})$$



Small signal model for the circuit shown to in the last page.


xii) Output resistance: The output resistance relates the small increase in the output voltage to the small change in collector current.

Since  $R_L$  is not a part of the amplifier,  $R_L$  is not included in the output resistance. So, the output resistance, given  $P_o = \infty$ , is given by

$$R_o = R_c.$$
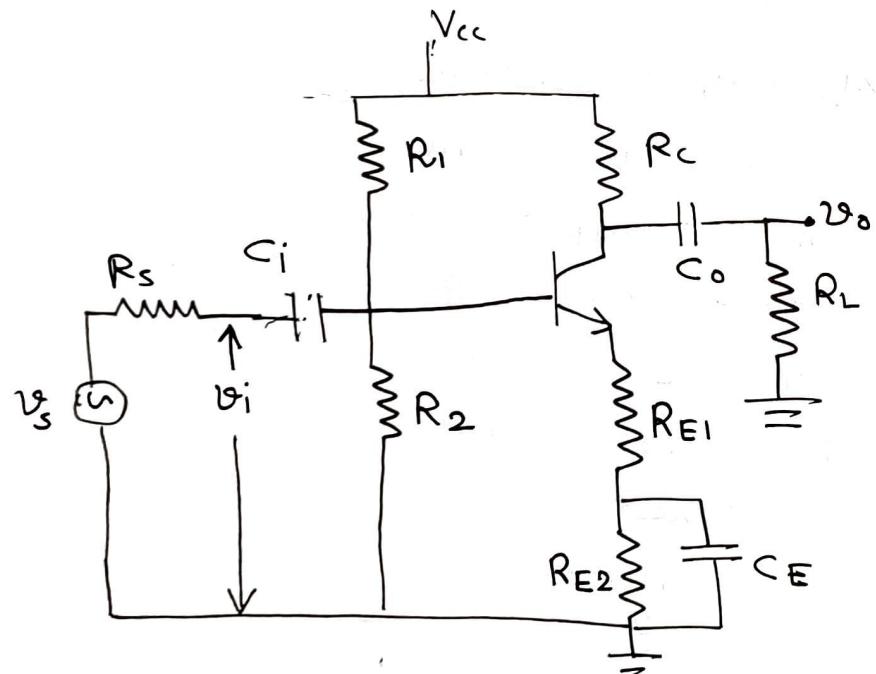
### Loading effect:

A change in overall gain of the amplifier due to external resistors is called loading effect. The resistance  $R_s$  and  $R_L$  denote the source resistance and load resistor and are ~~ext=~~ external resistors to the amplifier.



When a transistor amplifier is bought from the market, the parameter

$$A_{v0}^{\text{no-load}} = \frac{V_o}{V_i} \text{ is specified.}$$

However, Due to  $R_s$  and  $R_L$ , the overall gain is reduced. Let us first consider the source loading effect with  $R_L \rightarrow \infty$ .

$$\begin{aligned} A_{v0} &= \frac{V_o}{V_i} \\ &= \frac{V_o}{V_i} \times \frac{V_i}{V_s} \\ &= \frac{V_o}{V_i} \times \frac{R_i}{R_i + R_s} \quad R_i = \text{input resistance} \\ &= A_{v0}^{\text{no-load}} \times \frac{R_i}{R_i + R_s}. \quad R_i = r_\pi \\ &\quad + (\beta + 1) R_{E1} \end{aligned}$$

Similarly, we can calculate the loading effect of the load resistor  $R_L$ . We will discuss the load resistor loading effect via a numerical problem. Note that the loading while calculating the loading effect, we are only interested in the AC loading effect.