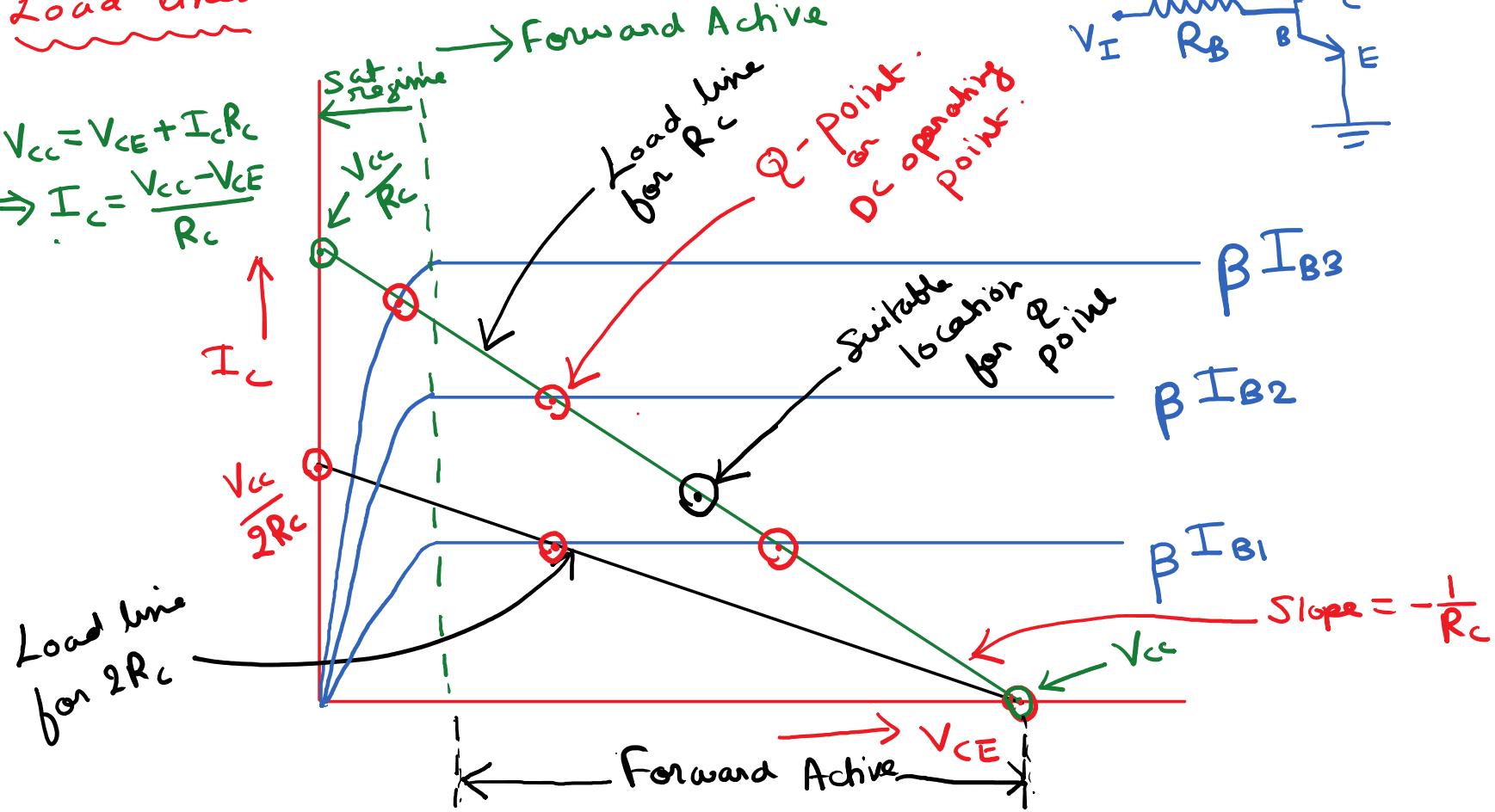


Class - 20

Load lines:

$$V_{CC} = V_{CE} + I_C R_C$$


$$\Rightarrow I_C = \frac{V_{CC} - V_{CE}}{R_C}$$




Q -point or DC operating point is the solution of the DC values of V_{CE} and I_C for a given transistor and a given set of external resistor. Q -point can be changed by changing the resistors R_B and R_C .

A suitable location for Q -point is somewhere near the middle of the active regime or the middle of the load line.

Early effect on Base-width modulation

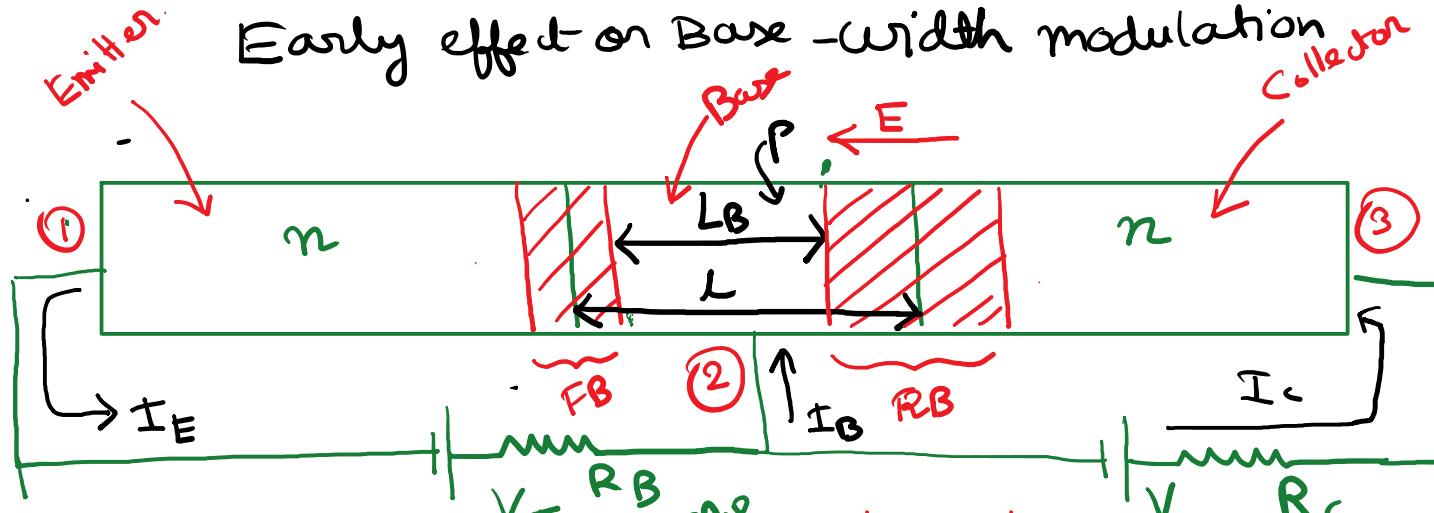


L_B = length of the neutral Base region.

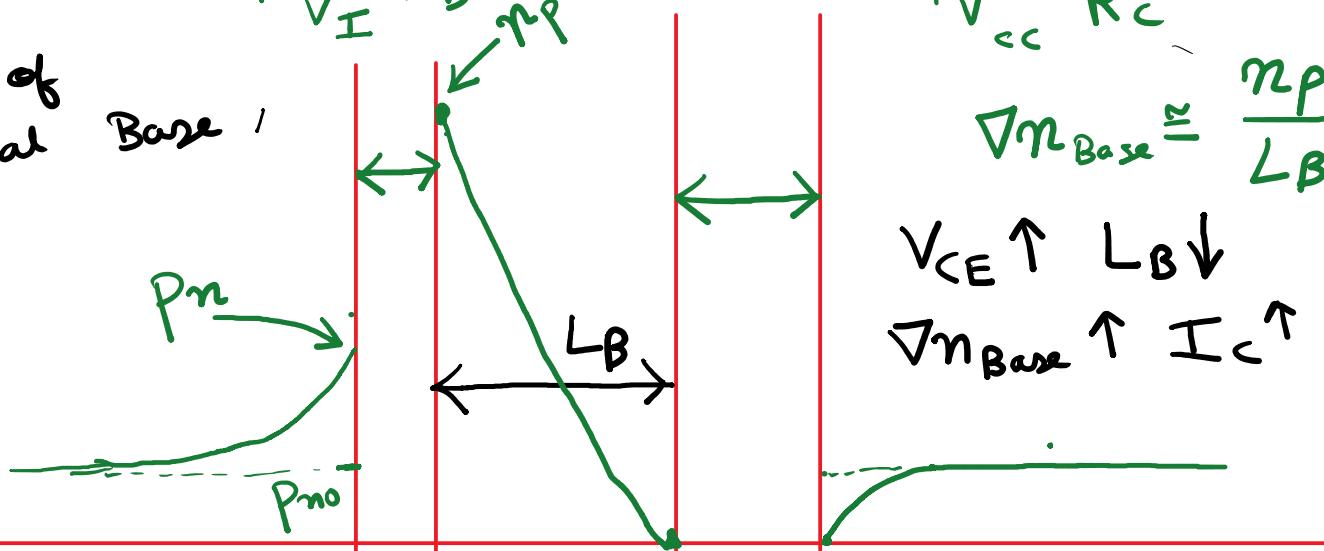

$$I_C = I_{C0} \left(1 + \frac{V_{CE}}{V_A} \right)$$

$$\frac{\partial I_C}{\partial V_{CE}} = \frac{I_{C0}}{V_A} = g_o = \text{output conductance of the transistor.}$$
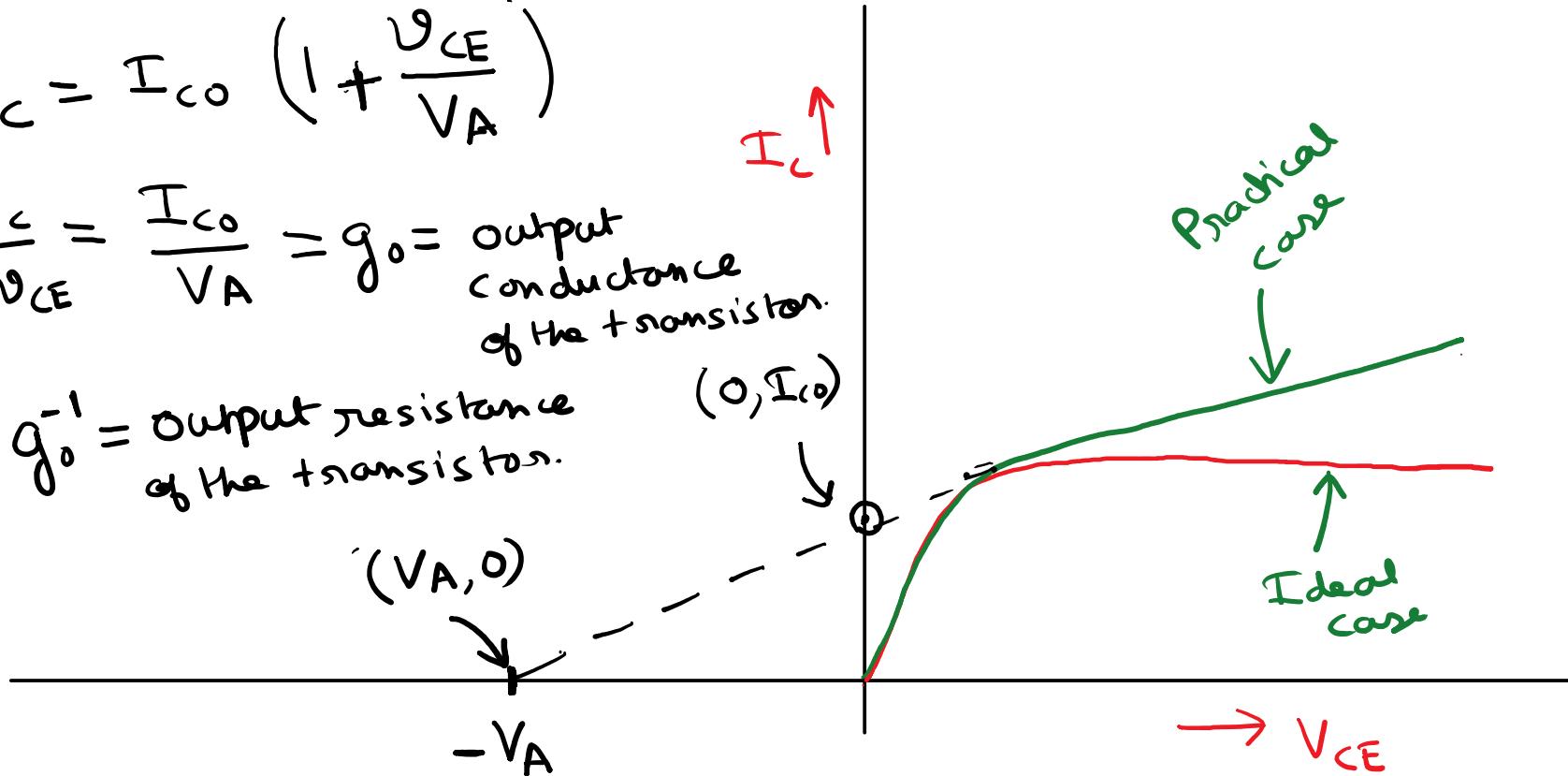
$$r_o = g_o^{-1} = \text{output resistance of the transistor.}$$




V_A = Early voltage

Class - 21

V_I	V_o
Low	High
High	Low

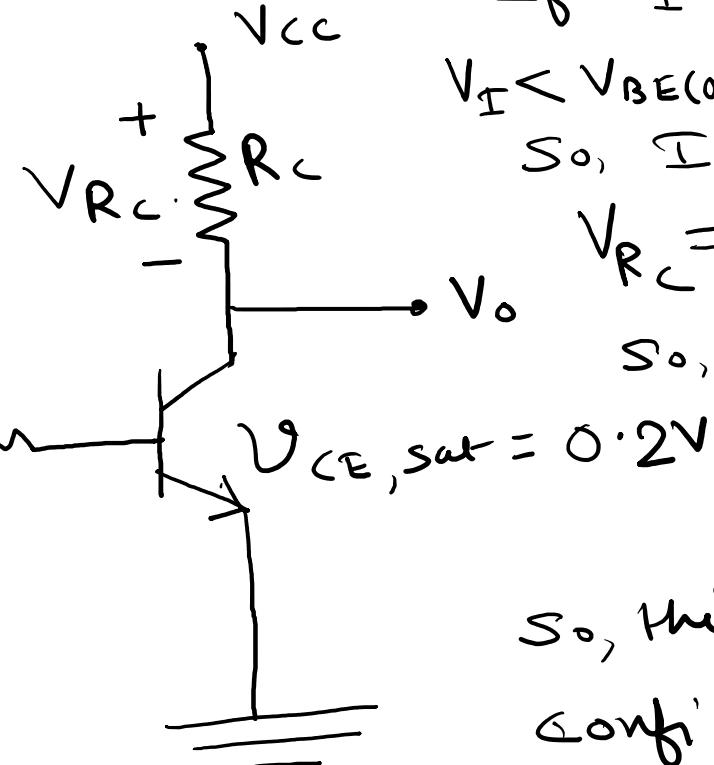Here low value of V_o means $V_o = V_{CE,sat}$




If V_I is low, that is $V_I < V_{BE(on)}$ then $I_B = 0$. So, $I_C = 0$. So, $V_{R_C} = 0$ so, $V_o = V_{cc}$.

So, this configuration acts as a NOT gate.


NAND gate

V_{I1}	V_{I2}	V_o
Low	Low	High
Low	High	High
High	Low	High
High	High	Low

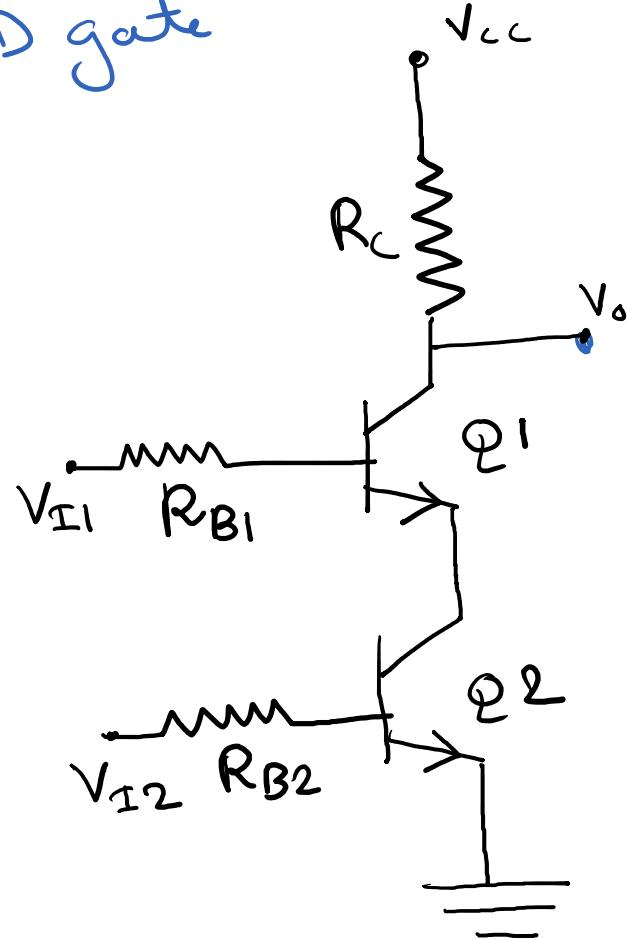


V_{I1}	V_{I2}	V_o
Low	Low	High
Low	High	Low
High	Low	Low
High	High	Low


NOR Gate

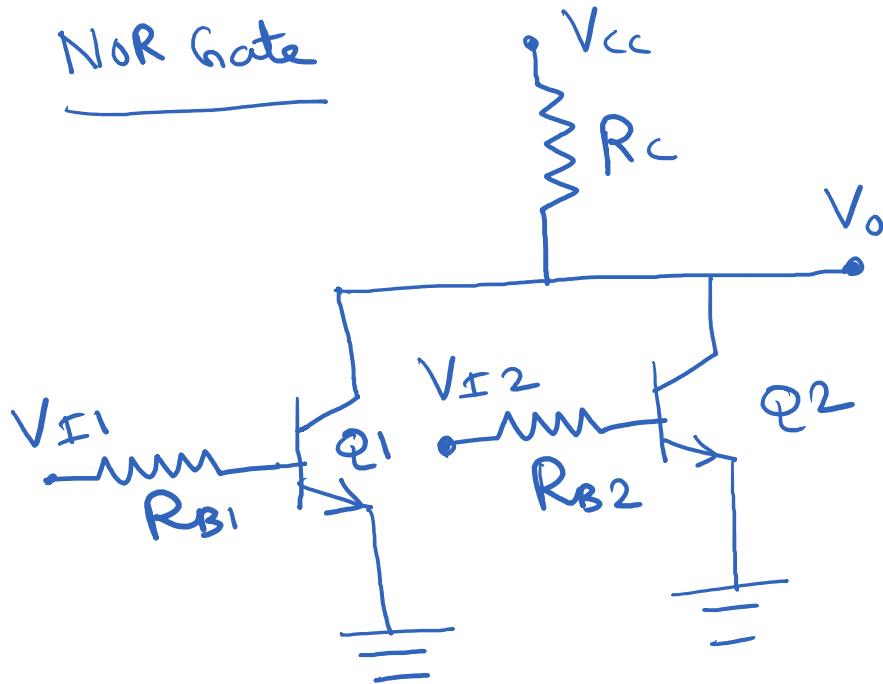

Thevenin's Theorem:-

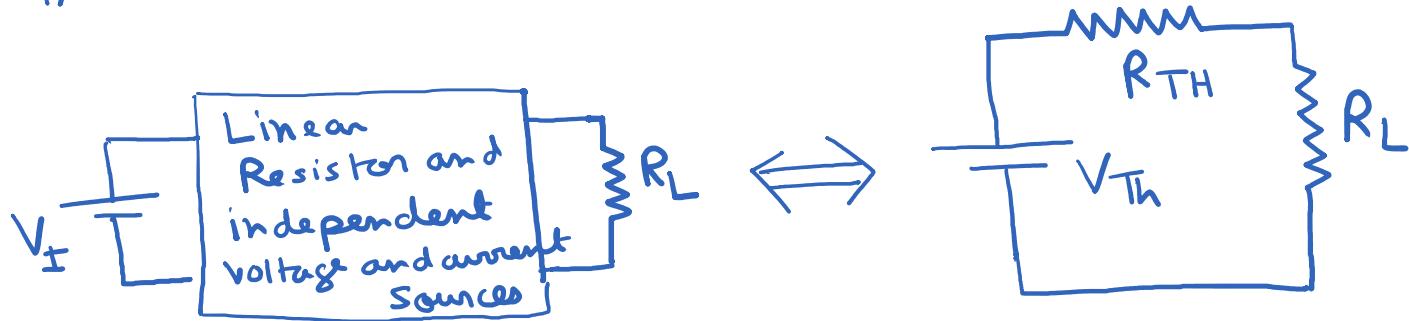



To find V_{Th} :-

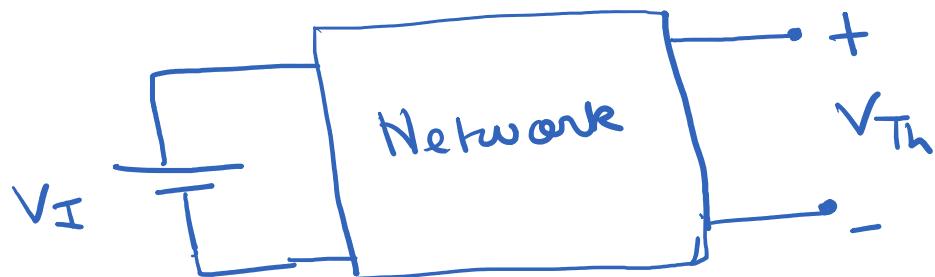

To Find R_{Th} → remove any voltage source and replace it by short circuit

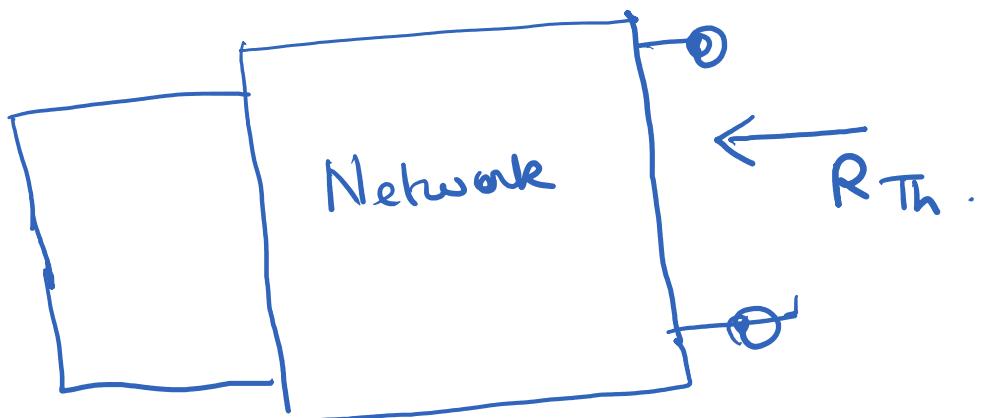→ remove any independent current source and replace by open circuit



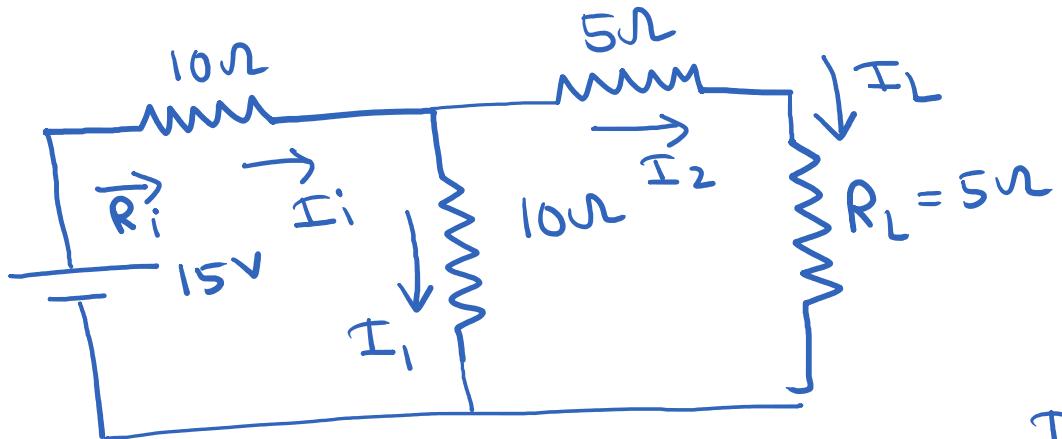

$$R_i = 10\Omega + (10\Omega \parallel 10\Omega)$$

$$= 15\Omega$$



$$I_i = \frac{15V}{15\Omega} = 1A$$

$$I_1 = I_2$$

$$I_1 + I_2 = I_i = 1A$$

$$I_1 = I_2 = \frac{I_i}{2} = 0.5A$$

$$I_L = I_2 = 0.5A$$

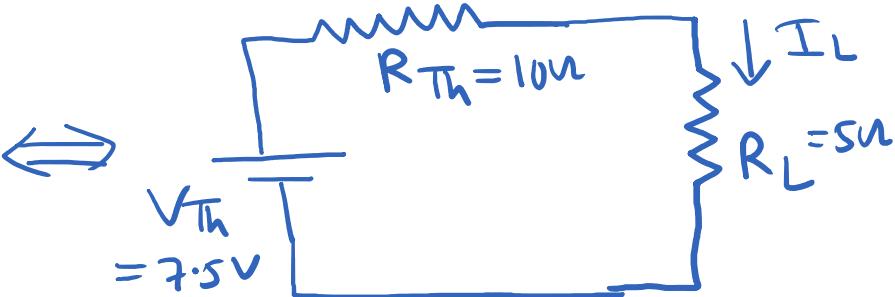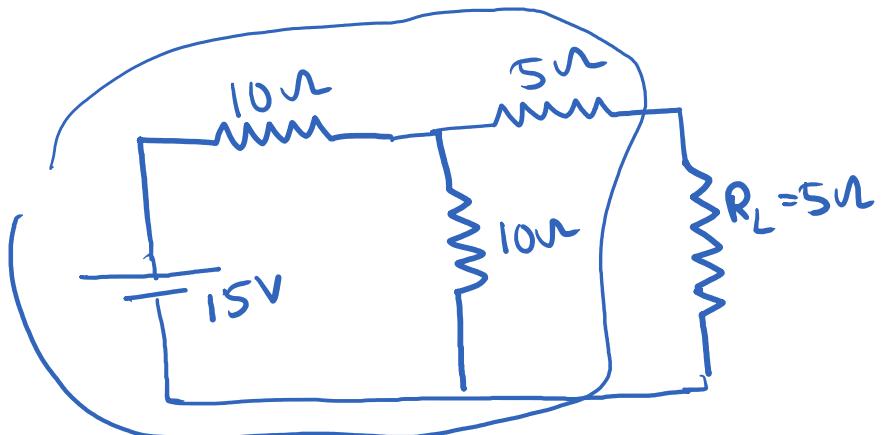

$$V_{Th} = 15V \times \frac{10\Omega}{10\Omega + 10\Omega}$$

$$= 7.5V$$

$$R_{Th} = 5\Omega + (10\Omega || 10\Omega)$$

$$= 10\Omega$$


$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$= \frac{7.5V}{10\Omega + 5\Omega}$$

$$= 0.5A$$


Biasing of Transistors:-
Fixed Biasing scheme.

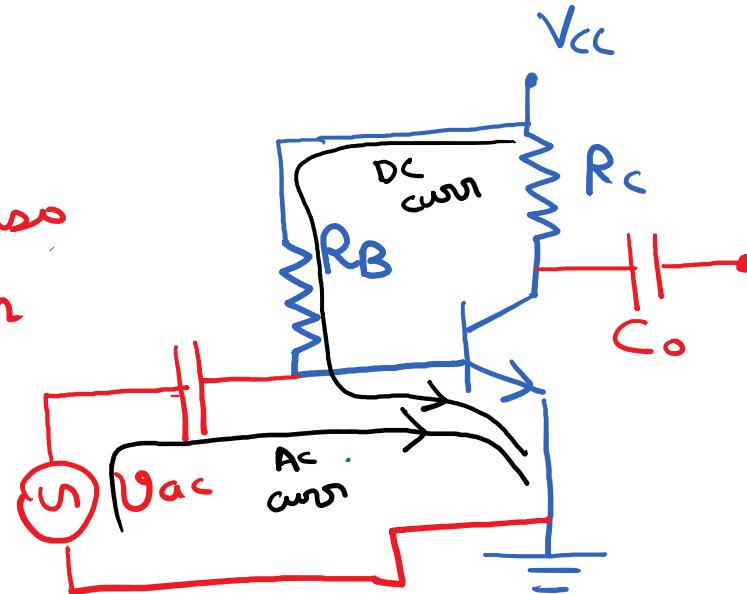This Biasing Scheme is also
known as Single Resistor
Biasing Scheme -



Voltage divider Biasing Scheme.

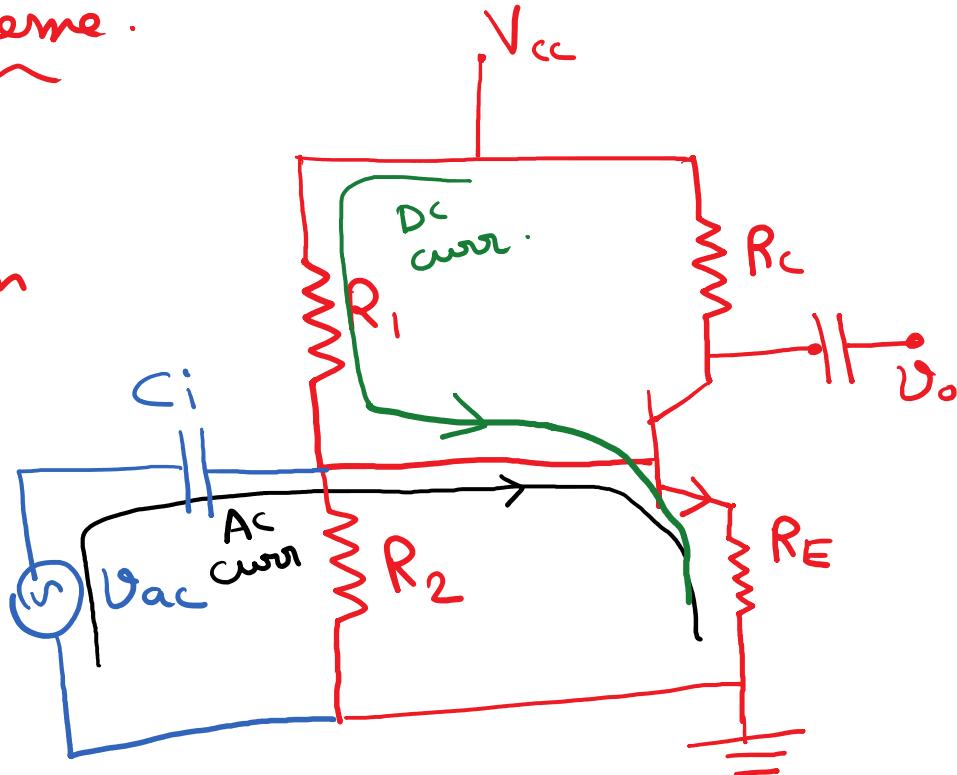R_E is put to enhance biasing stability against variation in β .






Class - 22

V_{Th} , $R_{Th} = ?$

$$V_{Th} = \frac{R_2}{R_1 + R_2} \times V_{CC}$$

$$R_{Th} = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

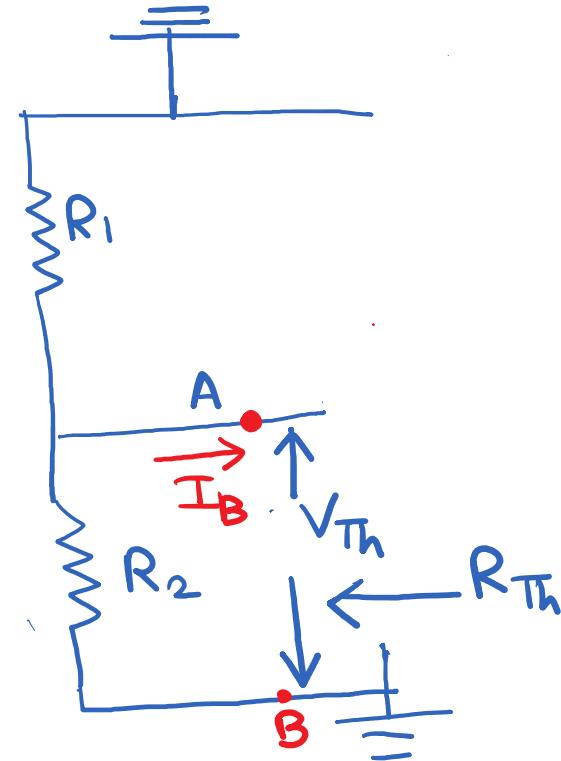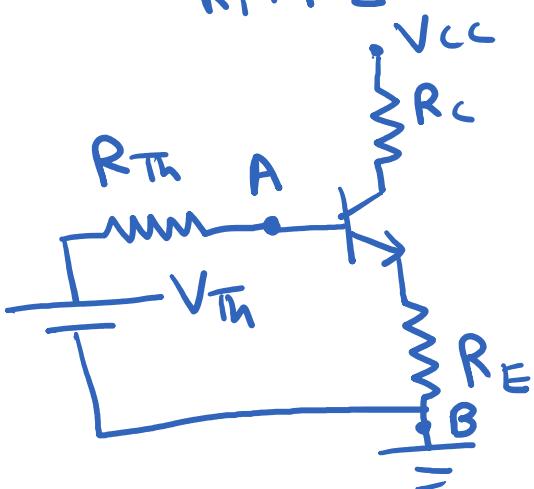

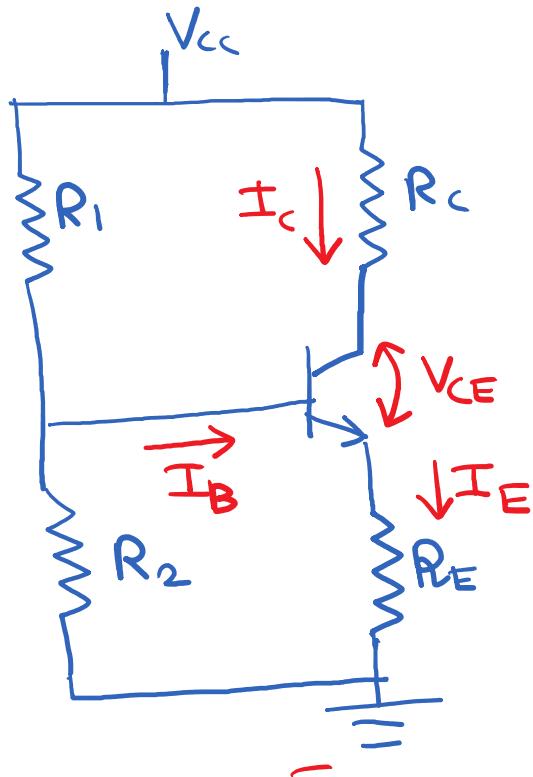

$$V_{Th} = I_B R_{Th} + V_{BE(on)} + I_E R_E$$

$$= I_B R_{Th} + V_{BE(on)} + (\beta + 1) I_B R_E$$

$$\Rightarrow I_B = \frac{V_{Th} - V_{BE(on)}}{R_{Th} + (\beta + 1) R_E}$$


$$I_C = \beta \frac{V_{Th} - V_{BE(on)}}{R_{Th} + (\beta + 1) R_E}$$

$$\because (\beta + 1) R_E \gg R_{Th}$$

$$I_C \approx \beta \frac{V_{Th} - V_{BE(on)}}{(\beta + 1) R_E} = \frac{\beta}{\beta + 1} \frac{V_{Th} - V_{BE(on)}}{R_E}$$

$$\approx \frac{V_{Th} - V_{BE(on)}}{R_E} \quad (\because \beta + 1 \approx \beta)$$

For good transistor
 $\beta > 10000$

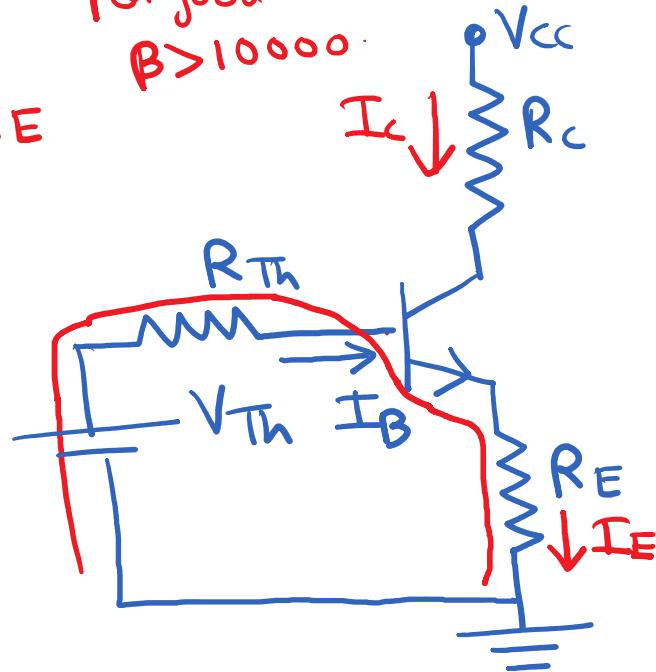

$I_E = (\beta + 1) I_B$
 β can vary due to temperature or due to ageing of transistor.

$$I_{CQ} = \frac{V_{TH} - V_{BE(ON)}}{R_E} \cdot (\beta_{H1} - 1)$$

from
to ageing of transistor.

$$V_{CC} = 18V, R_1 = 33k\Omega, R_2 = 10k\Omega, R_C = 2.2k\Omega$$

$$R_E = 1k\Omega, \beta = 50.$$

I_B, I_C, V_{CE} ?

$$V_{Th} = \frac{R_2}{R_1 + R_2} \times V_{CC} = \frac{10}{43} \times 18V = 4.186V.$$



$$R_{Th} = (R_1 || R_2) = (33k\Omega || 10k\Omega) = 7.67k\Omega$$

$$V_{Th} = R_{Th} \times I_B + V_{BE(ON)} + I_E R_E$$

$$4.186V = 7.67 I_B + 0.7V + 51 I_B \times 1.$$

$$\Rightarrow I_B \times (7.67 + 51) = (4.186 - 0.7)$$
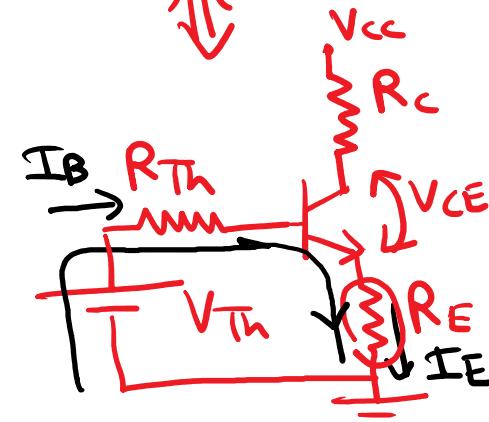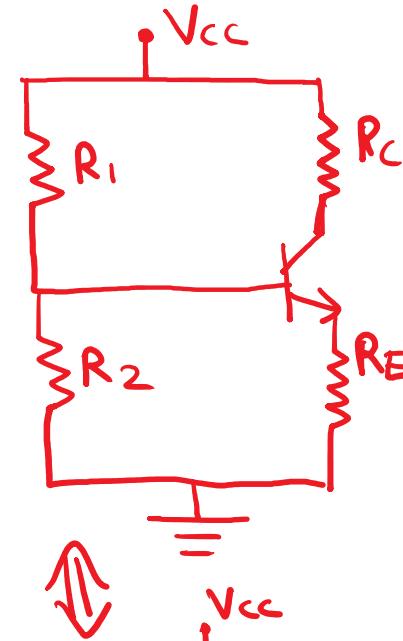
$$\Rightarrow I_B = \frac{3.486}{58.67} mA = 0.0594 mA$$



$$I_C = \beta I_B = 50 \times 0.0594 \text{mA} = 2.97 \text{mA}$$


$$\begin{aligned}V_{CE} &= V_{CC} - I_C R_C - I_E R_E \\&= 18V - 2.97 \times 2.2 - 2.97 \times 1 \\&= 18V - 2.97 \times 3.2V \\&= 8.496V\end{aligned}$$

Small signal or AC model:-

$$I_E \approx I_s \exp \left\{ \frac{V_{BE}}{V_T} \right\}$$

$$I_B = \frac{I_E}{\beta + 1} = \frac{I_s}{\beta + 1} \exp \left\{ \frac{V_{BE}}{V_T} \right\}$$
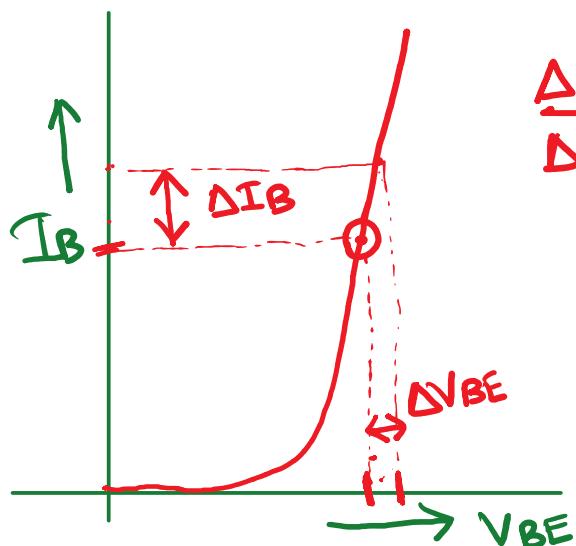
$$= I_{SB} \exp \left\{ \frac{V_{BE}}{V_T} \right\}$$




$\frac{\Delta I_B}{\Delta V_{BE}}$ = Slope of the
 $I_B - V_{BE}$ at the DC operating point

$$= \frac{\partial I_B}{\partial V_{BE}} \Big|_{V_{BE} = V_{BE}\Phi}$$

$$= \frac{I_{SB}}{V_T} \exp \left\{ \frac{V_{BE}\Phi}{V_T} \right\}$$

$$= \frac{I_{BE}\Phi}{V_T}$$

Small signal Base conductance

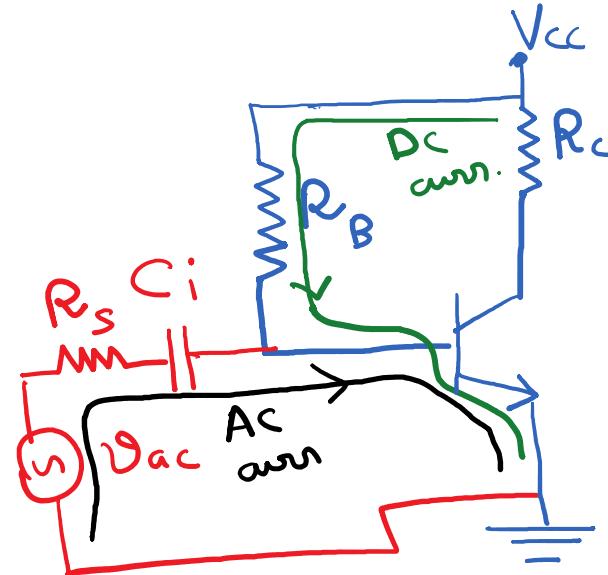

$$\left. \frac{\partial V_{BE}}{\partial I_B} \right|_{V_{BEQ}} = \left(\frac{\partial I_B}{\partial V_{BE}} \right)^{-1} = \frac{V_T}{I_{BEQ}} = r_\pi$$


↑
small signal
Base resistance

$$\frac{\Delta V_{BE}}{\Delta I_B} = r_\pi$$


$\Rightarrow \frac{V_{BE}}{I_B} = r_\pi$

depends
on DC
point biasing

a parameter of the
AC model.

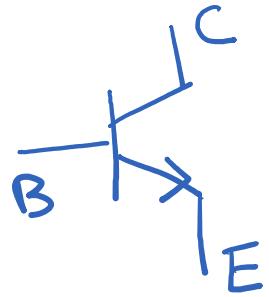

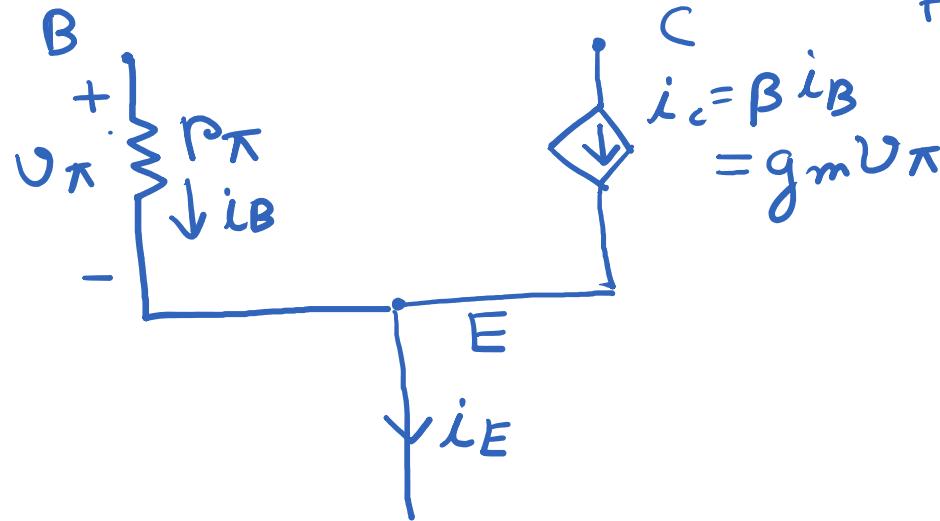small signal model of the
n-p-n transistor.




$$V_\pi = V_{be}$$

$$i_c = \beta i_B = \beta \frac{V_\pi}{r_\pi} = \frac{\beta}{r_\pi} V_\pi = g_m V_\pi$$

small-signal
trans-conductance

trans-conduc-

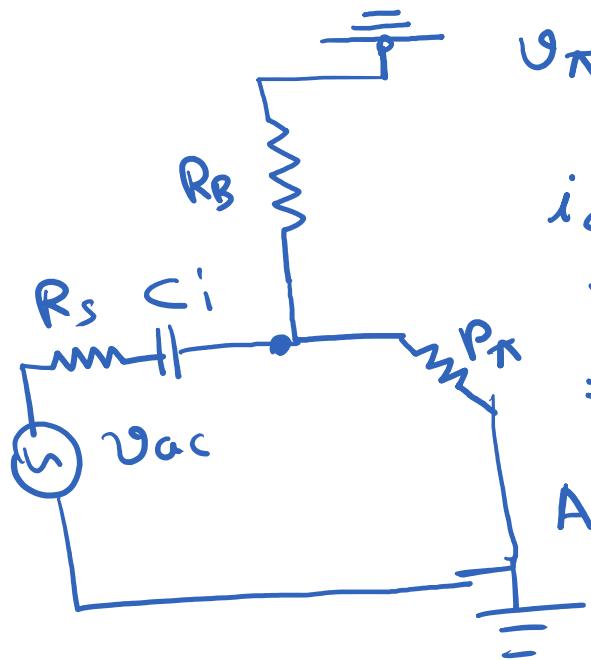




$$g_{\pi} = \frac{(R_B || r_{\pi})}{(R_B || r_{\pi}) + R_s} \times V_{ac}$$

$$i_c = g_m V_{\pi} = \frac{\beta}{r_{\pi}} V_{\pi}$$

$$V_o = -i_c R_c$$

$$= -\frac{\beta}{r_{\pi}} \frac{(R_B || r_{\pi}) R_c \times V_{ac}}{(R_B || r_{\pi}) + R_s}$$

$$A = \frac{V_o}{V_{ac}} = -\frac{\beta R_c}{r_{\pi}} \frac{R_B || r_{\pi}}{(R_B || r_{\pi}) + R_s}$$

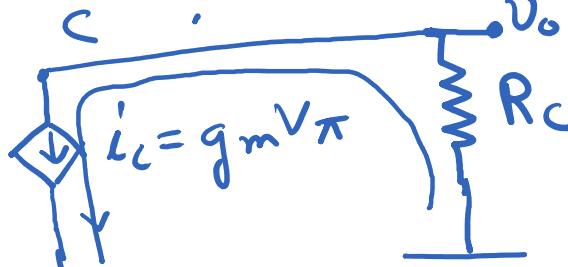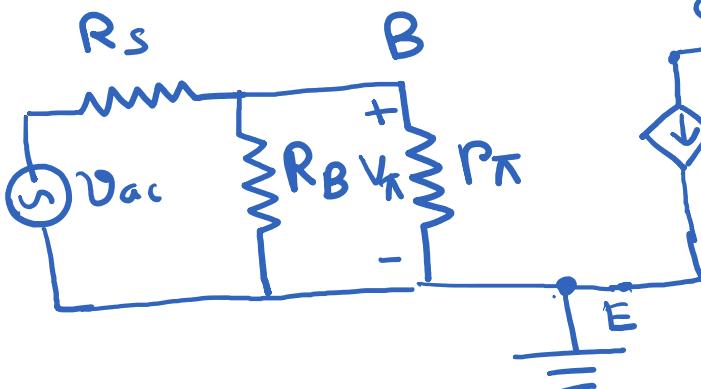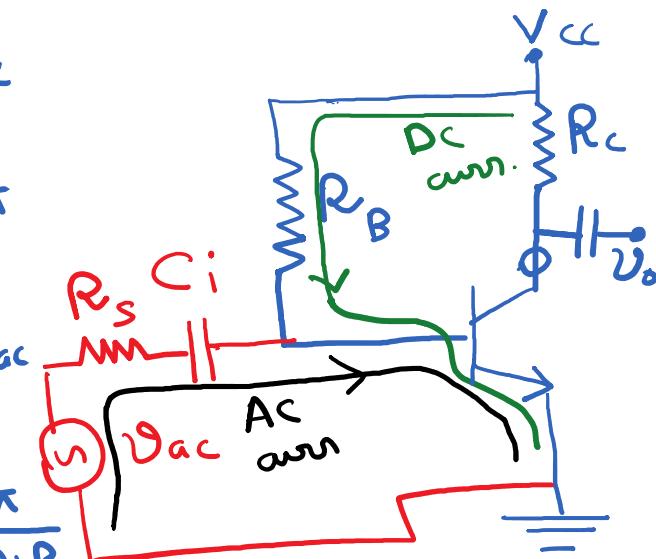



week 6 Page 25

$r_{\pi} \rightarrow$ small signal
Base resistance

$g_m \rightarrow$ small
signal
transconductance

Class-23

Small-signal AC model.

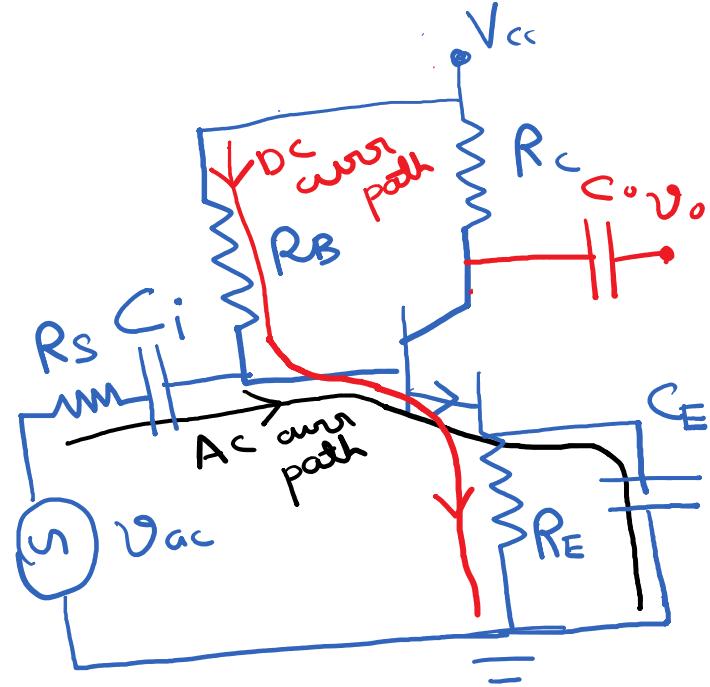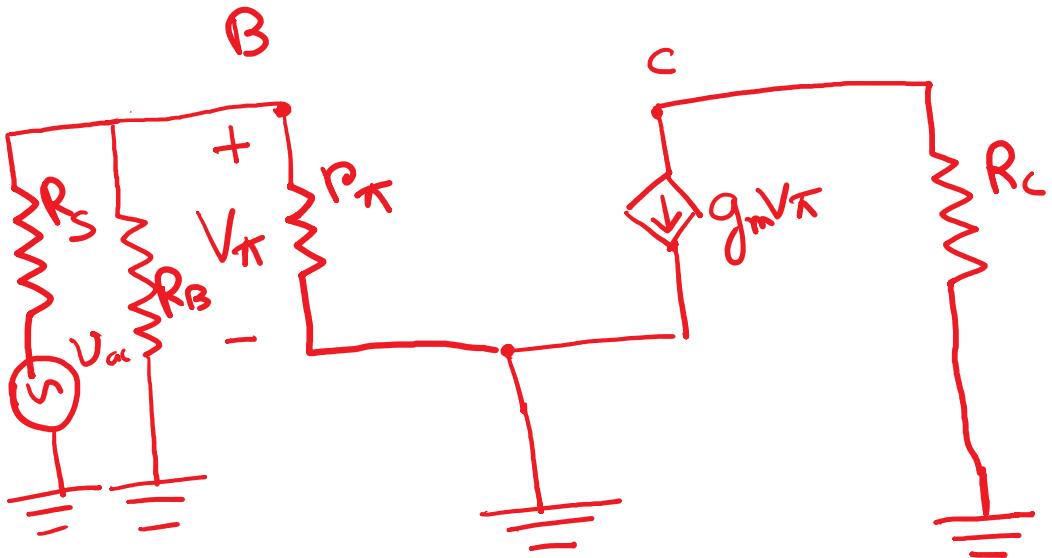

$$\text{Gain} = \frac{V_o}{V_{ac}}$$

$$V_\pi = \frac{R_B \parallel r_\pi}{R_B \parallel r_\pi + R_s} \times V_{ac}$$


$$i_c = g_m V_\pi$$

$$V_o = -i_c R_c$$

$$= -g_m V_\pi R_c$$

$$= -g_m R_c V_\pi = -g_m R_c \frac{R_B \parallel r_\pi}{R_B \parallel r_\pi + R_s} V_{ac}$$
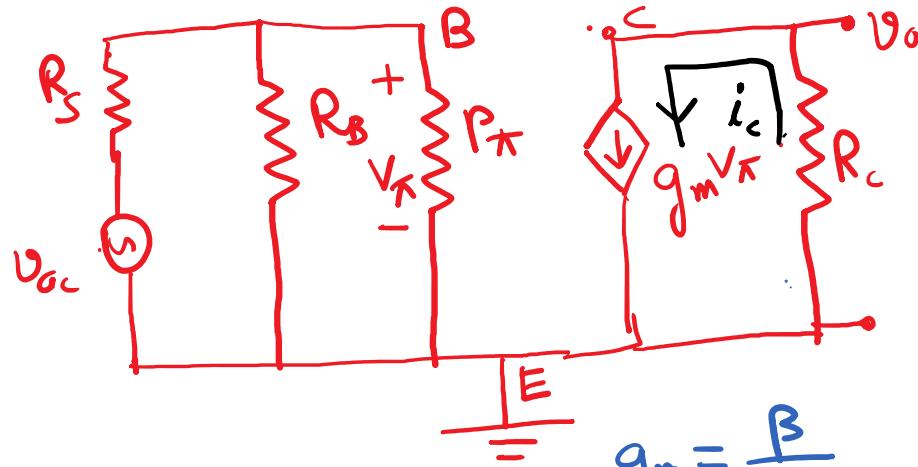
$$A = \frac{V_o}{V_{ac}} = -g_m R_c \frac{R_B \parallel r_\pi}{R_B \parallel r_\pi + R_s} = -\frac{\beta R_c}{r_\pi} \frac{R_B \parallel r_\pi}{R_B \parallel r_\pi + R_s}$$



$$g_m = \frac{\beta}{r_\pi}$$

AC parameters or small signal parameters:-


$$r_{\pi} = \frac{V_T}{I_B Q} \rightarrow \text{small signal Base resistance}$$

$$g_m = \frac{\beta}{r_{\pi}} \rightarrow \text{small signal transconductance.}$$

$r_o \rightarrow$ small signal output resistance

$$\hookrightarrow \frac{V_A}{I_C Q}$$

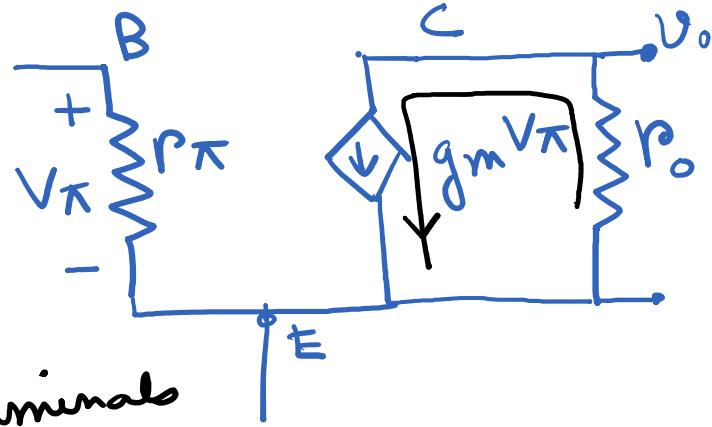
r_o is known as the small signal output resistance or simply the output resistance of a transistor. It is present between the collector and the emitter terminals.



$$I_C \approx I_{CQ} \left(1 + \frac{V_{CE}}{V_A}\right)$$

$$\approx I_{CQ} \left(1 + \frac{V_{CE}}{V_A}\right)$$

$$\frac{dI_C}{dV_{CE}} \Big|_{V_{CE} \rightarrow 0} = \frac{I_{CQ}}{V_A} = \frac{\partial I_C}{\partial V_{CE}} = r_o^{-1} = g_o$$

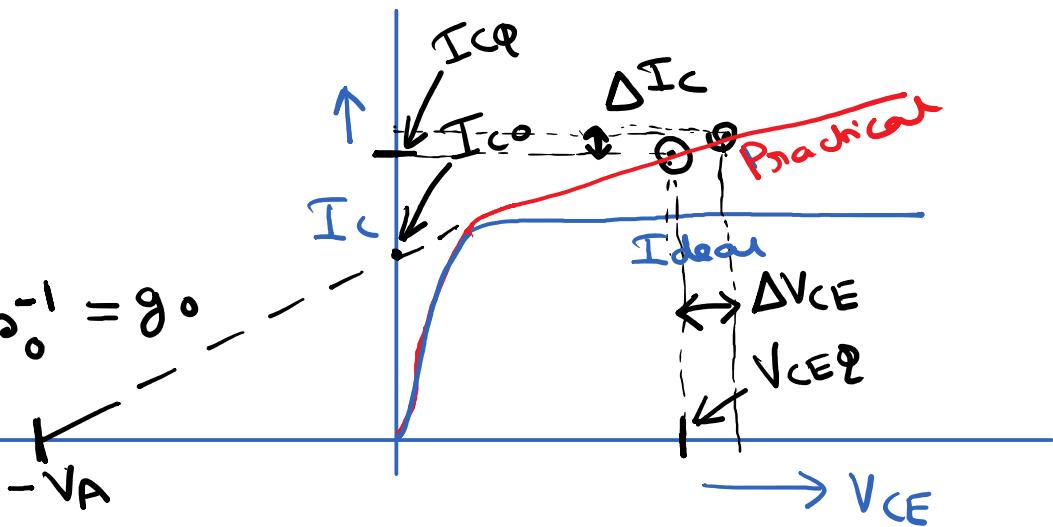


AC parameters

① $g_m, r_{\pi}, r_o = ?$

② $A_i = \frac{i_o}{i_i}$

③ $A_v = \frac{v_o}{v_i}$

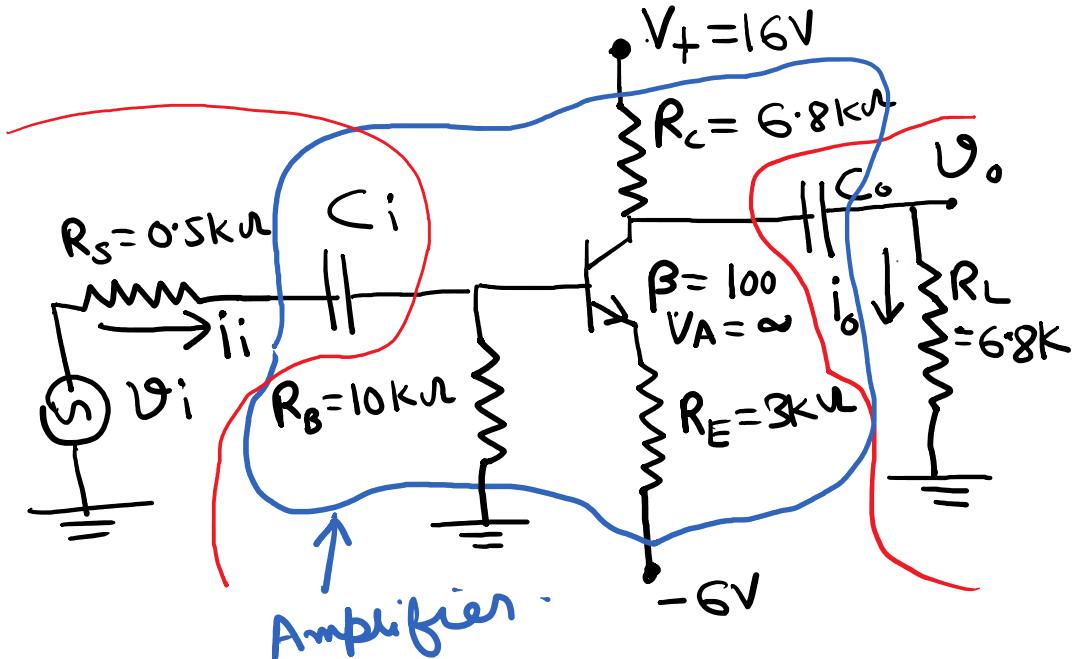

$$g_m = \frac{\beta}{r_{\pi}} , \quad r_{\pi} = \frac{V_T}{I_B q} , \quad r_o = \frac{V_A}{I_C}$$

$$0 - (-6V) = I_B R_B + V_{BE(on)} + I_E R_E$$

$$\Rightarrow 6V = I_B \times 10 + 0.7V + (100+1) I_B \times 3$$

$$\Rightarrow 6V - 0.7V = 10I_B + 303 I_B$$


$$\Rightarrow 5.3V = 313 I_B$$

$$\Rightarrow I_B = \frac{5.3}{313} \text{ mA}$$

$$= 0.0169 \text{ mA}$$

$$r_\pi = \frac{V_T}{I_B} = \frac{0.026V}{0.0169 \text{ mA}} = 1.53 \text{ k}\Omega$$


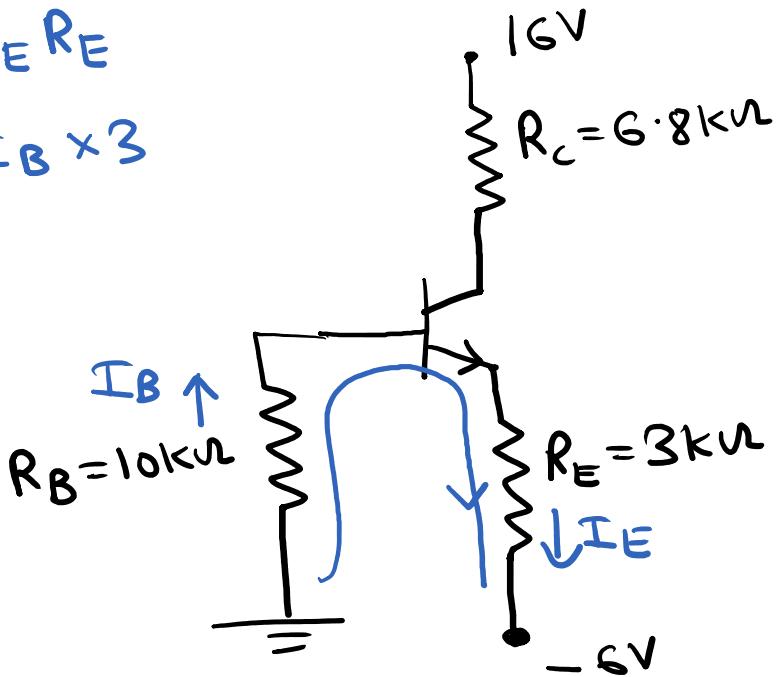
$$g_m = \beta/r_\pi = \frac{100}{1.53} \text{ milli-mho} = 0.065 \text{ milli-mho.}$$




$$r_o = \frac{V_A}{I_{CQ}} = \infty \quad (\because V_A = \infty)$$

$$\boxed{r_T = 1.53 \text{ k}\Omega, g_m = 0.065 \text{ milli-mho}, r_o = \infty}$$
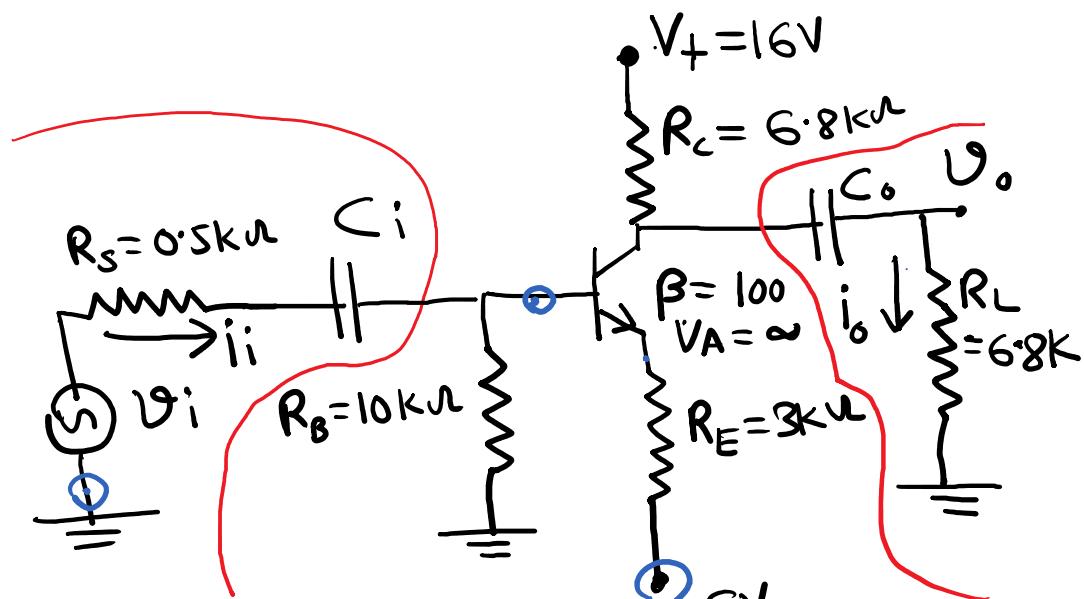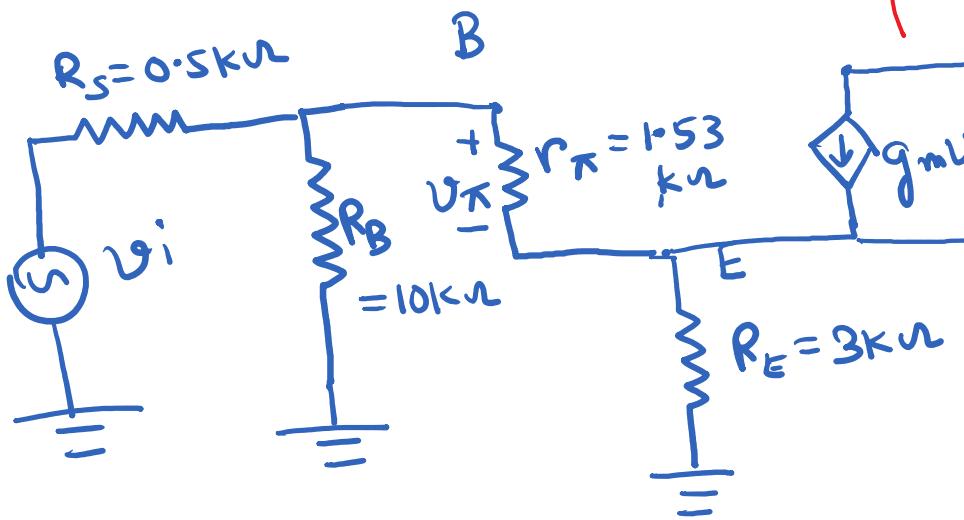
$$A_i = \frac{i_o}{i_i} \quad A_v = \frac{v_o}{v_i}$$



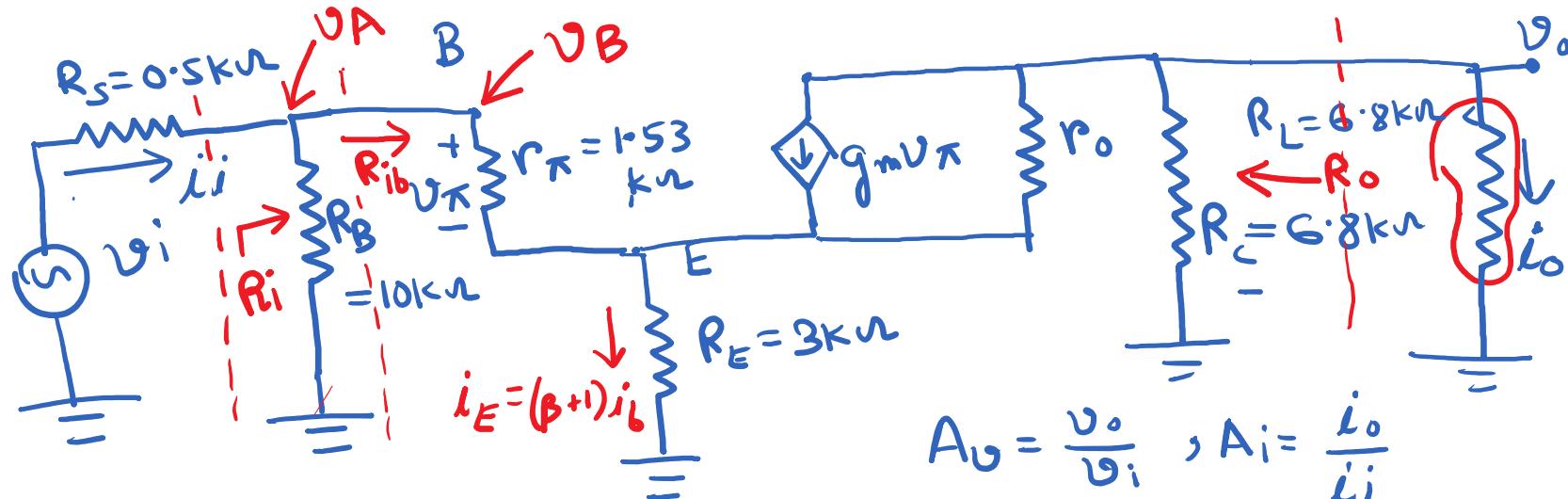

The resistance seen between the base and the ground
is known as the input Base resistance (R_{ib})

$$V_B = r_{\pi} i_b + i_E R_E = r_{\pi} i_b + (\beta + 1) i_b R_E$$

$$\Rightarrow R_{ib} = \frac{V_B}{i_b} = r_{\pi} + (\beta + 1) R_E$$

Since i_E is higher than i_B by a factor of $(\beta + 1)$, therefore the resistance R_E is multiplied by $(\beta + 1)$ when one looks into the Base terminal. This is known as the resistance reflection rule.

The total input resistance (R_i) of the amplifier is the total resistance which one sees when they look into the amplifier input port. The total input resistance excludes the input voltage source resistance (R_s)

$$R_i = R_B \parallel R_{ib}$$

The total resistance which one sees when one looks into the collector terminal is known as the output resistance (R_o). R_o excludes the load resistance.

$$R_o \approx (R_C + R_E) \parallel R_L$$

R_{ib} , R_o and R_i are the characteristics of the amplifier circuit.

$$\begin{aligned}
 R_{ib} &= r_\pi + (\beta + 1)R_E \\
 &= 1.53\text{k}\Omega + 101 \times 3\text{k}\Omega \\
 &= 304.53\text{k}\Omega.
 \end{aligned}$$

$$\begin{aligned}
 R_i &= R_B \parallel R_{ib} = (10\text{k}\Omega \parallel 304.53\text{k}\Omega) \\
 &= 9.68\text{k}\Omega.
 \end{aligned}$$

The voltage at the Base (V_A or V_B)

$$\begin{aligned}
 &= \frac{V_s}{R_s + R_i} \times R_i \\
 &= V_s \times \frac{9.68\text{k}\Omega}{0.5\text{k}\Omega + 9.68\text{k}\Omega} = V_s \times \frac{9.68}{10.18}
 \end{aligned}$$

$$\begin{aligned}
 v_T &= v_A \times \frac{R_T}{R_{ib}} \\
 &= v_A \times \frac{1.53}{304.53} \\
 &= v_S \times \frac{9.68}{10.18} \times \frac{1.53}{304.53} \\
 &= 0.00479 v_S
 \end{aligned}$$

$$\begin{aligned}
 i_c &= g_m v_T \\
 &= 0.065 \times 0.00479 v_S \text{ (mA)} \\
 &= 0.000311 v_S \text{ (mA)}
 \end{aligned}$$

$$V_o = -i_C (R_C || R_L)$$

$$= -0.000311 V_S^{(\text{mA})} \times (6.8 \text{k}\Omega || 6.8 \text{k}\Omega)$$

$$= -0.000311 V_S (\text{mA}) \times 3.4 \text{k}\Omega$$

$$= -1.06 V_S$$

$$A_V = \frac{V_o}{V_S} = -1.06$$

$$|i_o| = \left| \frac{V_o}{R_L} \right| = \frac{|-1.06 V_S|}{R_L} = 1.06 \frac{V_S}{R_L}$$

$$|i_i| = \frac{V_S}{R_S + R_i}$$

$$A_i = \left| \frac{i_o}{i_i} \right| = 1.062 \times \frac{R_i + R_s}{R_L}$$
$$= 1.062 \times \frac{0.5k\Omega + 9.68k\Omega}{6.8k\Omega}$$
$$= 1.59$$