

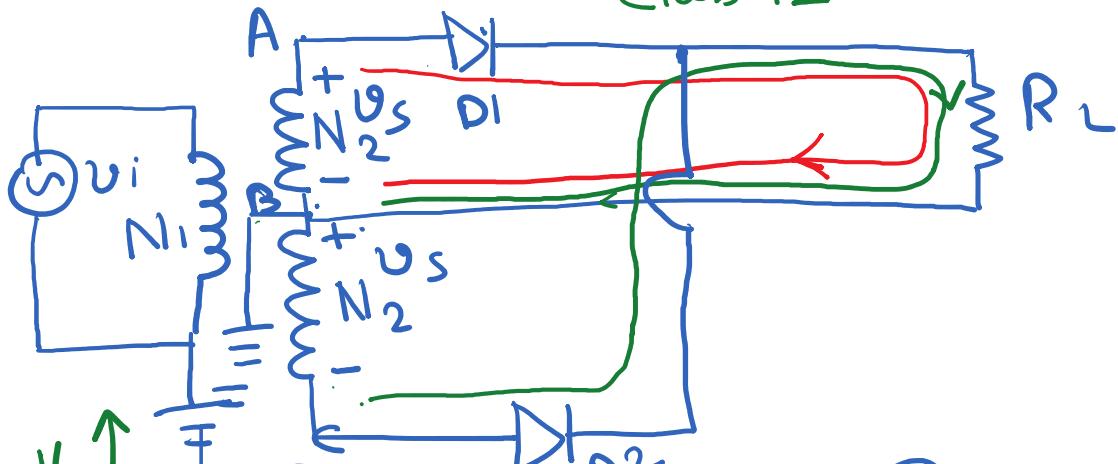


Class-12

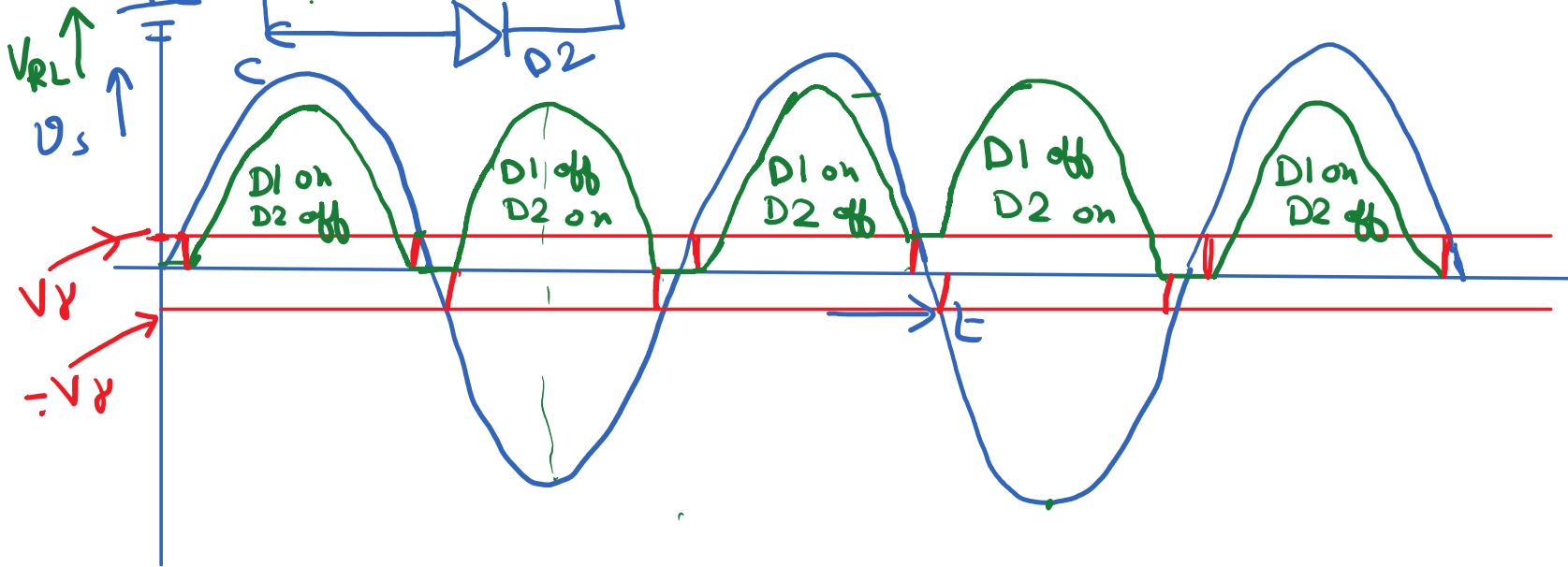

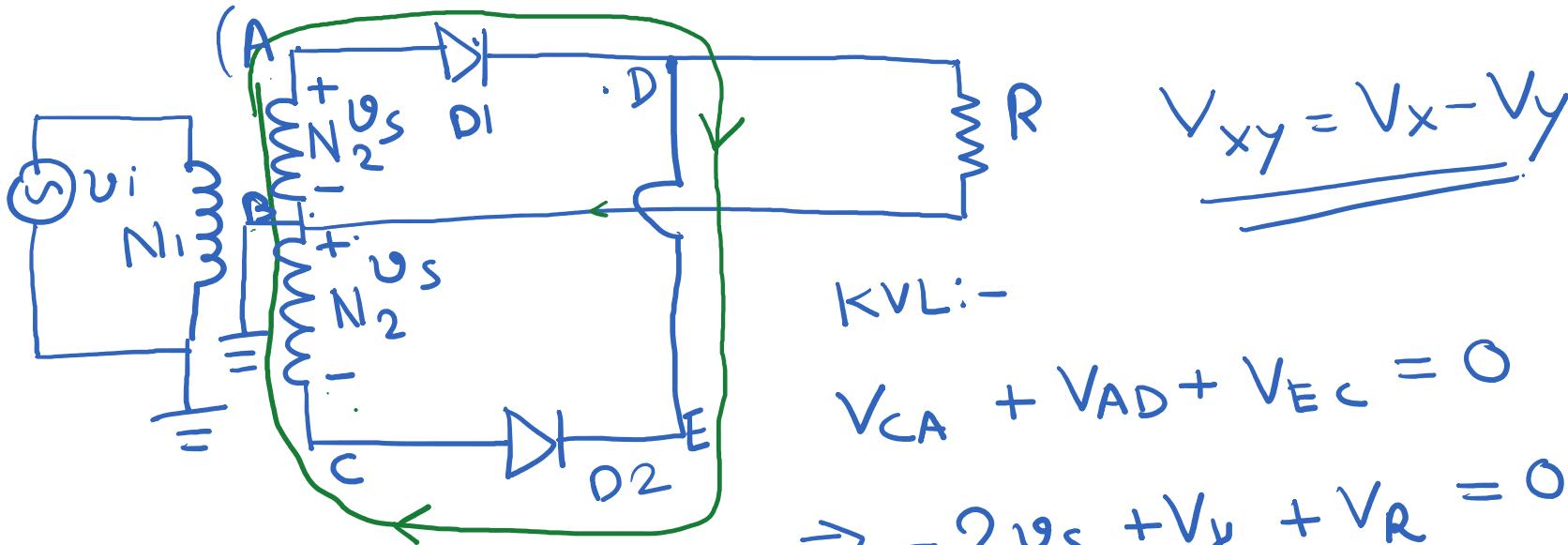Full-wave rectifier
with centre
tapped + transformer.





KVL:-

$$V_{CA} + V_{AD} + V_{EC} = 0$$

$$\Rightarrow -2\vartheta_s + V_y + V_R = 0$$

$$\Rightarrow V_R = 2\vartheta_s - V_y.$$


$$\Rightarrow V_R^{\max} = 2\vartheta_s^{\max} - V_y$$

$$PIN = 2\vartheta_s^{\max} - V_y$$


$$V_{xy} = V_x - V_y$$

Disadvantage :-

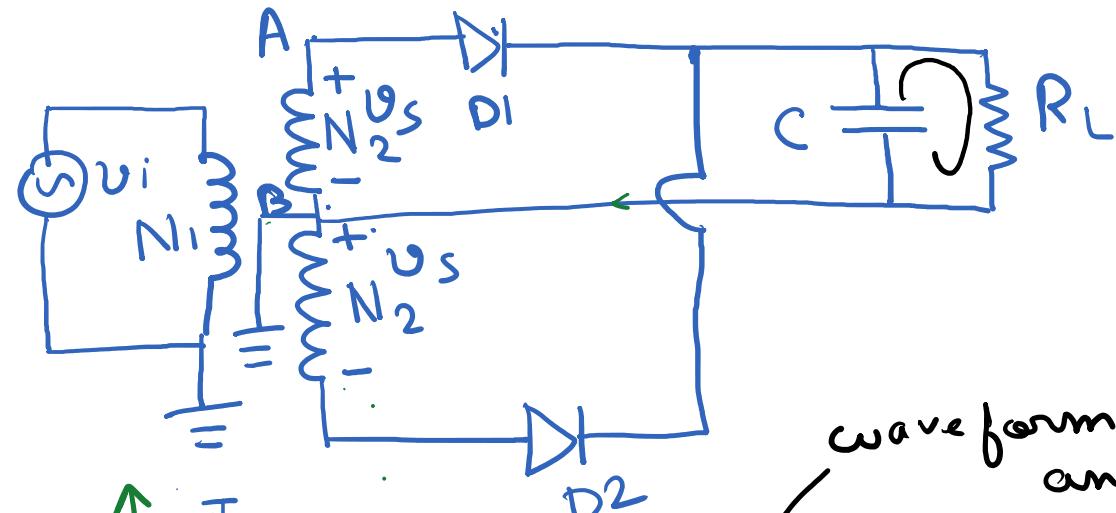- 1) Requires diodes with high PIV rating.
- 2) Needs twice the number of turns on windings in the secondary coil.



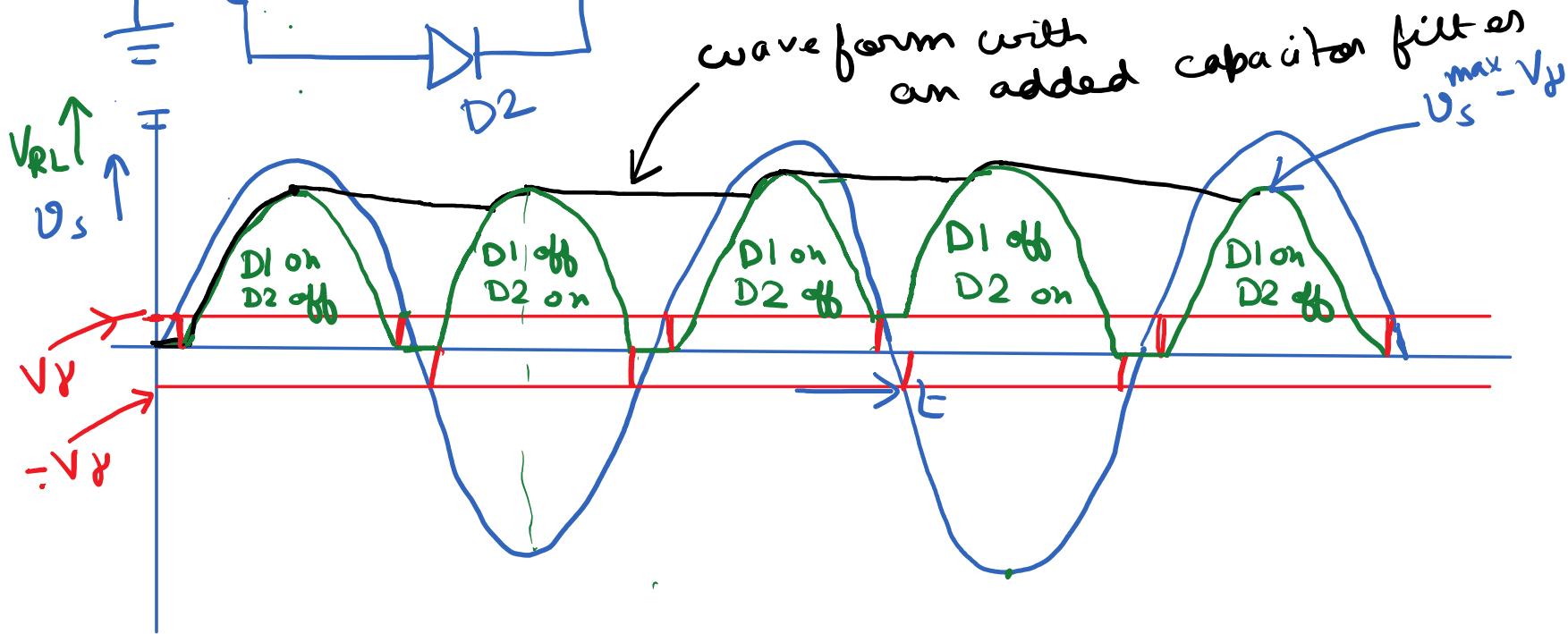Centre tapped
transformer full
wave rectifier.
with capacitor filter




T_p = time period of 2 s.


Here the capacitor charges up twice during each time period T_p . So, the time interval between successive charging events is $T_p/2$

$$V_{\text{ripple}} = V_c^{\max} - V_c^{\min}$$
$$\approx \frac{(T_p/2) V_c^{\max}}{R_L C} = \frac{T_p V_c^{\max}}{2 R_L C}$$

Ripple voltage of a full wave rectifier with capacitor filter is approximately half of that in a half wave rectifier with a capacitor filter

Full-wave Bridge rectifier:-

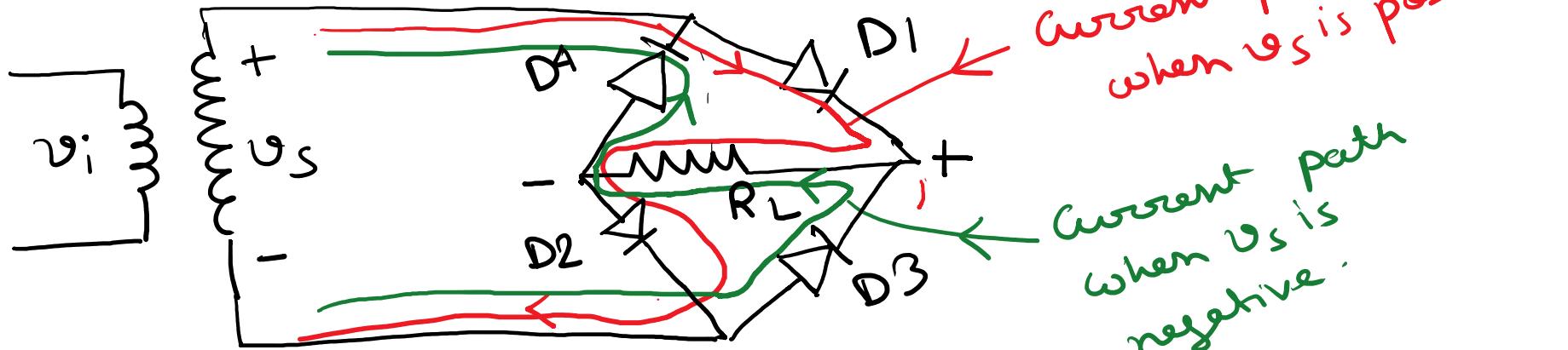

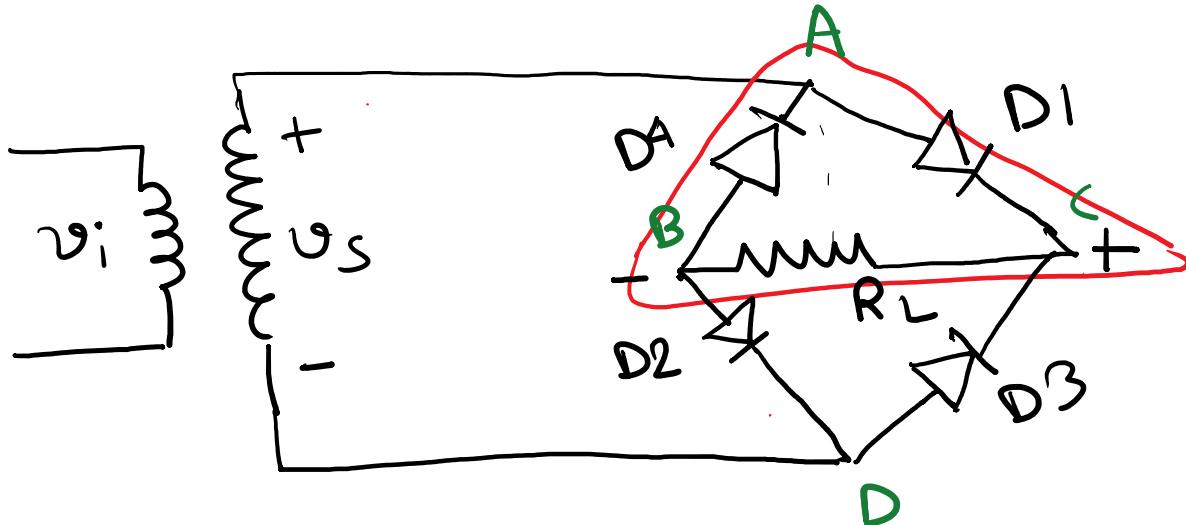

$$\begin{aligned}
 v_s &= v_{D1} + v_{RL} + v_{D2} \\
 &= v_\gamma + v_{RL} + v_\gamma \\
 \Rightarrow v_{RL} &= v_s - 2v_\gamma \\
 \Rightarrow v_{CB} &= v_{RL} \\
 &= v_s - 2v_\gamma
 \end{aligned}$$

KVL: $v_{AC} + v_{CB} + v_{BA} = 0$

$$v_R = v_{AB} = -v_{BA} = (v_{AC} + v_{CB})$$

$$= v_\gamma + (v_s - 2v_\gamma)$$

$$v_R^{\max} = v_s^{\max} - v_\gamma \Rightarrow PIV = v_s^{\max} - v_\gamma$$

- Adv:-
- 1) Lower PIV rating than that of a centre tapped transformer Full wave rectifier.
 - 2) Less number of turns in the secondary coil.


- Disv:-
- 1) Need 4 diodes instead of two.
 - 2) The maximum voltage across load resistor is $V_s^{\max} - 2V_D$ which lower than that of a centre tapped transformer full wave rectifier.

Application of the Breakdown regime of the Diode:-

So, the breakdown regime has sharper characteristics compared to the forward Biased regime

V_Z (a few volts)

$I \uparrow$

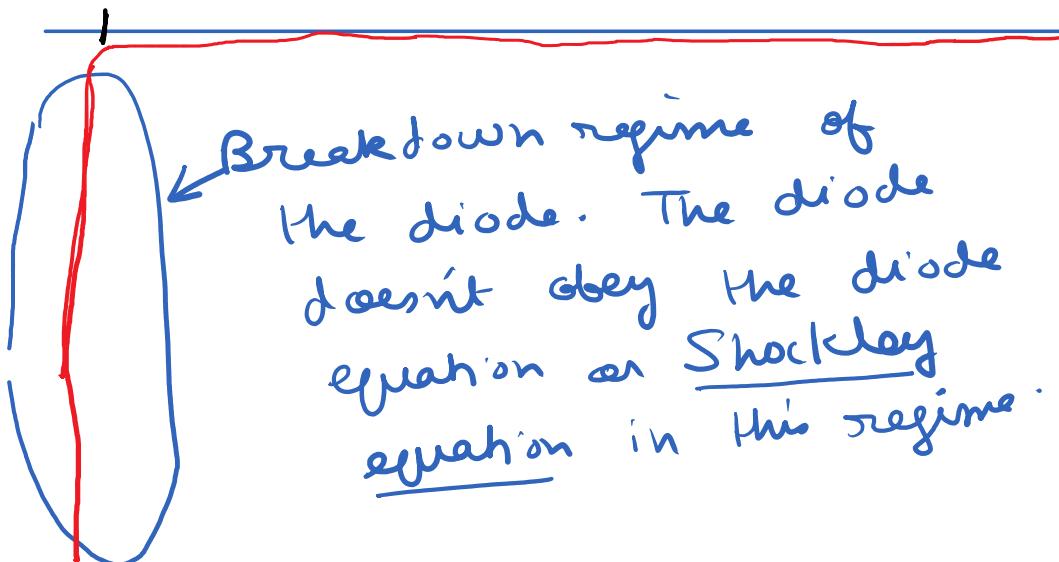


Breakdown regime of the diode. The diode doesn't obey the diode equation or Shockley equation in this regime.

$V_D (.3 \sim .8V) \rightarrow V$

V_Z can be controlled by appropriate fabrication techniques but V_D can't be controlled.

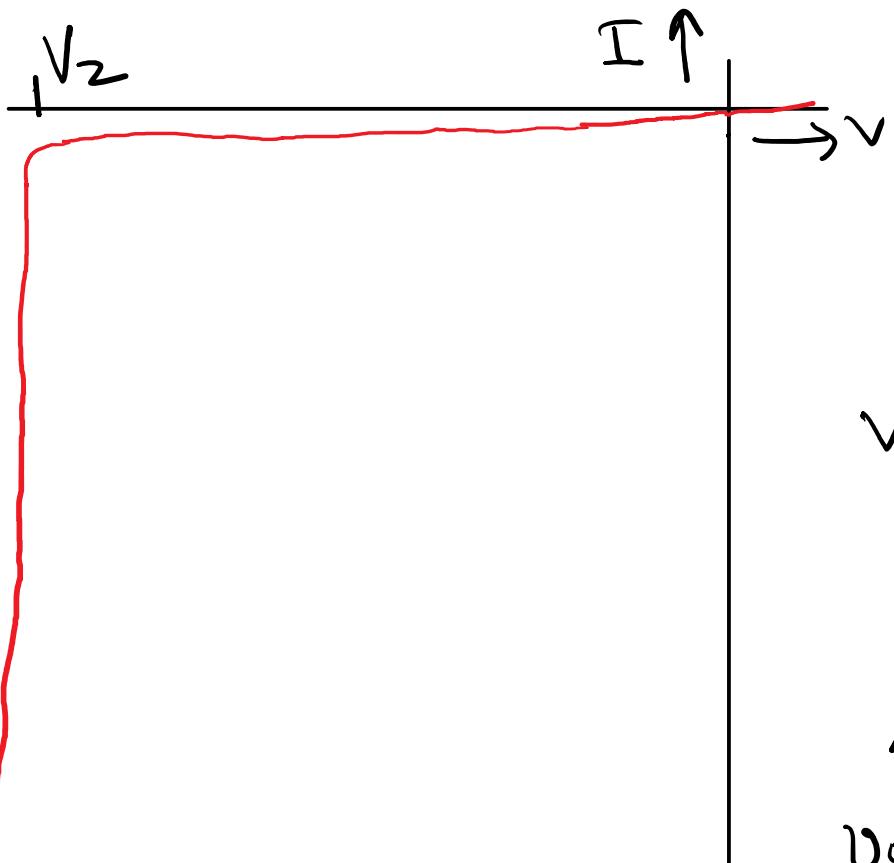
Zener diode :- Highly doped p-n junction where the break down regime depends on quantum tunneling and not on Avalanche mechanism.







$$V_{RI} = \begin{cases} 0 & \text{for } V < V_2 \\ V - V_2 & \text{for } V \geq V_2 \end{cases}$$

R_i

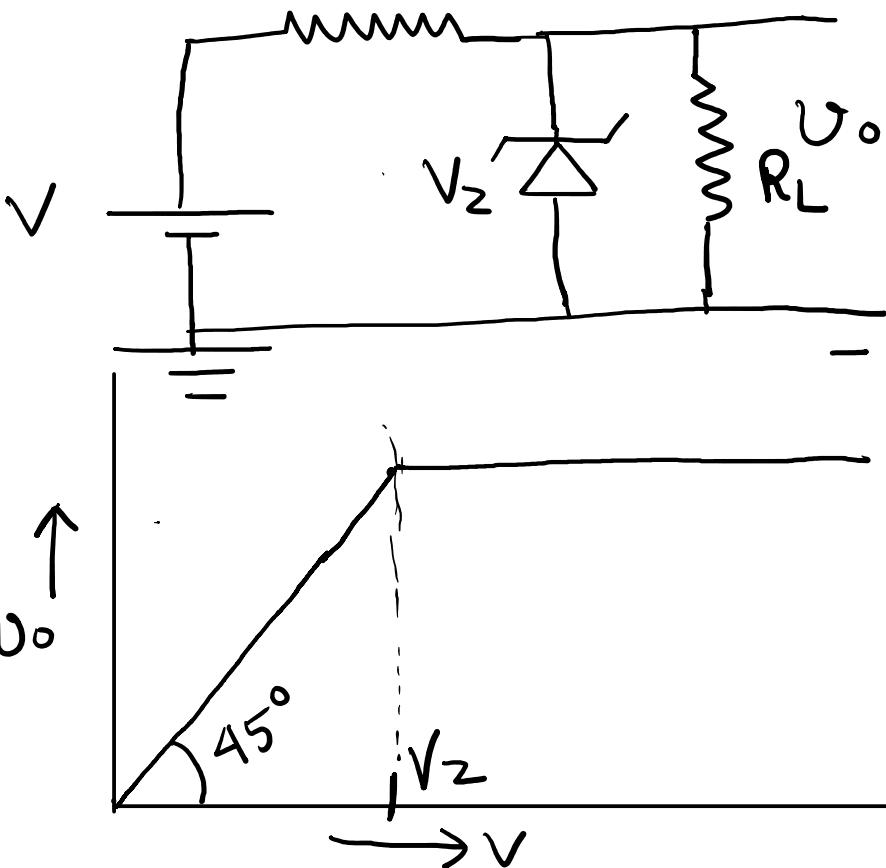

Class-13.

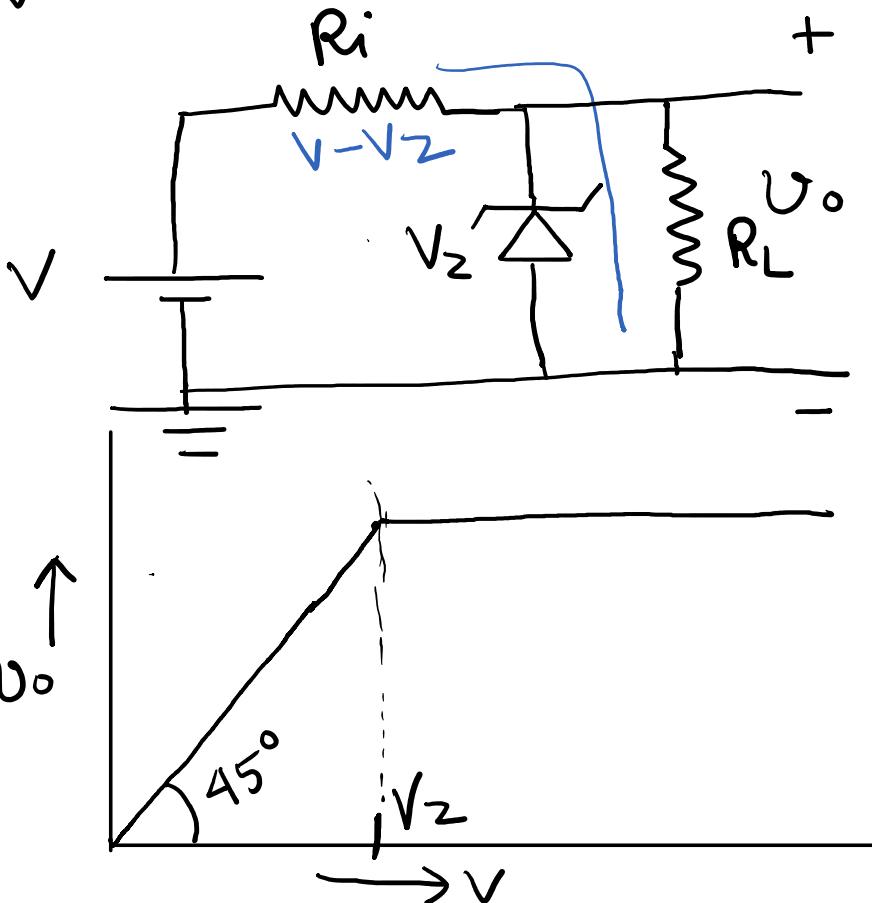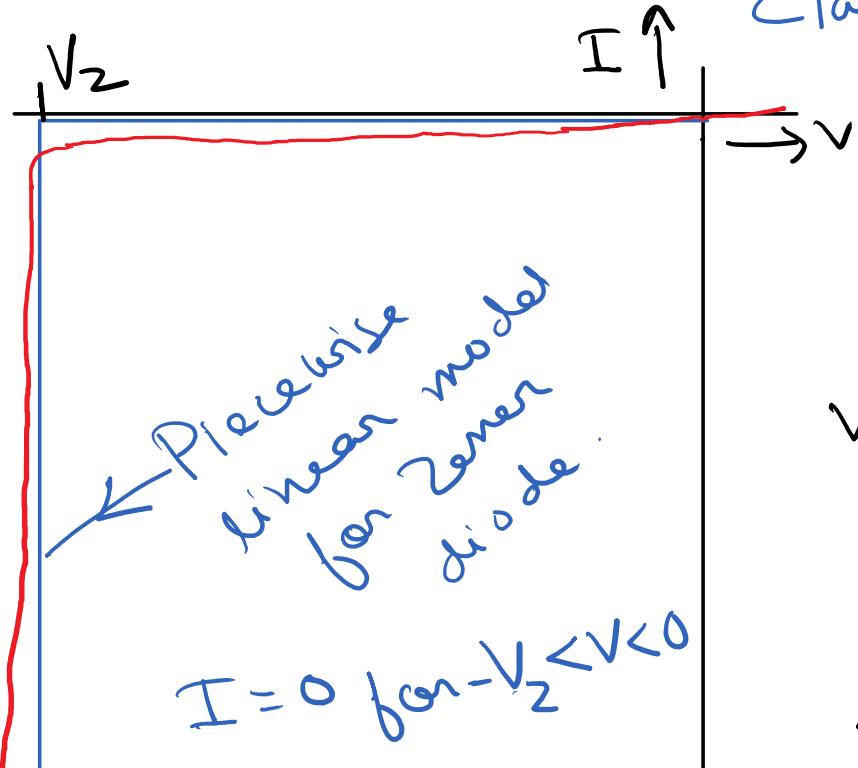

$$V_i = 20V, V_2 = 10V, R_i = 222\Omega$$

$$P_2(\text{max}) = 400mW$$


$$(a) R_L = 380\Omega, I_L, I_2, I_i = ?$$

(b) Value of R_L needed to establish $P_2(\text{max})$

$$(a) I_i = \frac{V_i - V_2}{R_i} = \frac{20V - 10V}{222\Omega} = 0.045A = 45mA$$

$$I_L = \frac{V_{RL}}{R_L} = \frac{V_2}{R_L} = \frac{10V}{380\Omega} = 0.0263A = 26.3mA$$
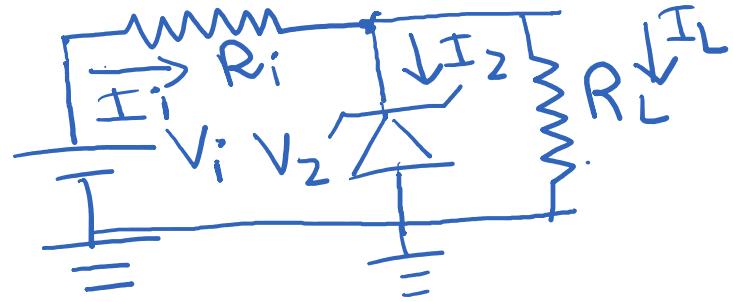
$$I_L + I_2 = I_i \Rightarrow I_2 = I_i - I_L = 45mA - 26.3mA = 18.7mA$$



$$(b) P_Z(\max) = I_Z(\max) \times V_Z$$

$$\Rightarrow 400\text{mW} = I_Z(\max) \times 10\text{V}$$

$$\Rightarrow I_Z(\max) = \frac{400}{10} \text{mA} = 40\text{mA}$$

$$I_i = 45\text{mA}$$
$$I_L^{\min} = I_i - I_Z^{\max} = 45\text{mA} - 40\text{mA} = 5\text{mA}$$

$$R_L = \frac{V_{RL}}{I_L^{\min}} = \frac{V_Z}{I_L^{\min}} = \frac{10\text{V}}{5\text{mA}} = 2\text{k}\Omega$$

$$\underline{Q2} \quad V_2 = 10V$$

$$I_2(\text{min}) = 0.1 I_2(\text{max})$$


V_i varies between 15V and 20V

Determine the value of R_i such that the Zener diode is in breakdown for I_L between 50mA to 500mA.

$$I_2^{\text{min}} \rightarrow V_i = V_i^{\text{min}} \text{ and } I_L = I_L^{\text{max}}$$

$$I_2^{\text{max}} \rightarrow V_i = V_i^{\text{max}} \text{ and } I_L = I_L^{\text{min}}$$
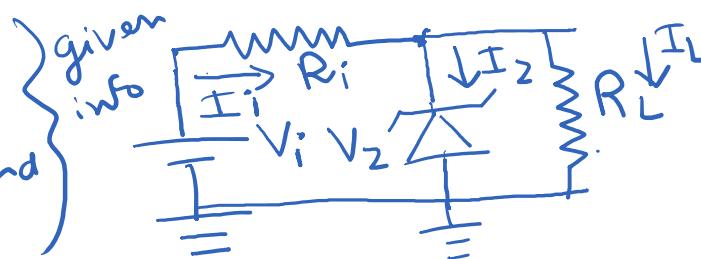
$$I_2 = I_i - I_L \Rightarrow I_2^{\text{max}} = I_i^{\text{max}} - I_L^{\text{min}}$$



Equation when the current across the Zener diode is at the minimum value.

$$V_i^{\min} = R_i(I_L^{\max} + I_2^{\min}) + 10V.$$

$$\Rightarrow 15V = R_i(500mA + I_2^{\min}) + 10V$$

$$\Rightarrow R_i(500mA + I_2^{\min}) = 5V \quad - \textcircled{1}$$

Equation when the Zener diode current is at its maximum

$$V_i^{\max} = R_i(I_L^{\min} + I_2^{\max}) + V_Z$$

$$\Rightarrow 20V = R_i(50mA + I_2^{\max}) + V_Z$$

$$\Rightarrow R_i(50mA + I_2^{\max}) = 10V \quad - \textcircled{2}$$

$$\textcircled{2} \div \textcircled{1}$$

$$\frac{50mA + I_2^{\max}}{500mA + I_2^{\min}} = 2$$

$$\Rightarrow 50mA + I_2^{\max}$$

$$= 1000 + 2I_2^{\min}$$

$$= 1000 + 0.2I_2^{\max}$$

$$\Rightarrow 0.8I_2^{\max} = 950$$

$$\Rightarrow I_2^{\max} = 1187.5mA$$

$$= 1.1875A$$

$$R_i = \frac{10V}{50mA + 1187.5mA}$$


$$= 0.00808 k\Omega$$

$$= 0.00808 \text{ kN}$$
$$= 8.08 \text{ N}$$


Piecewise linear model with r_f and


$$I = 0 \text{ for } |V| < V_Z$$

$$I = \left| \frac{V - V_Z}{r_2} \right| \text{ for } |V| \geq V_Z$$

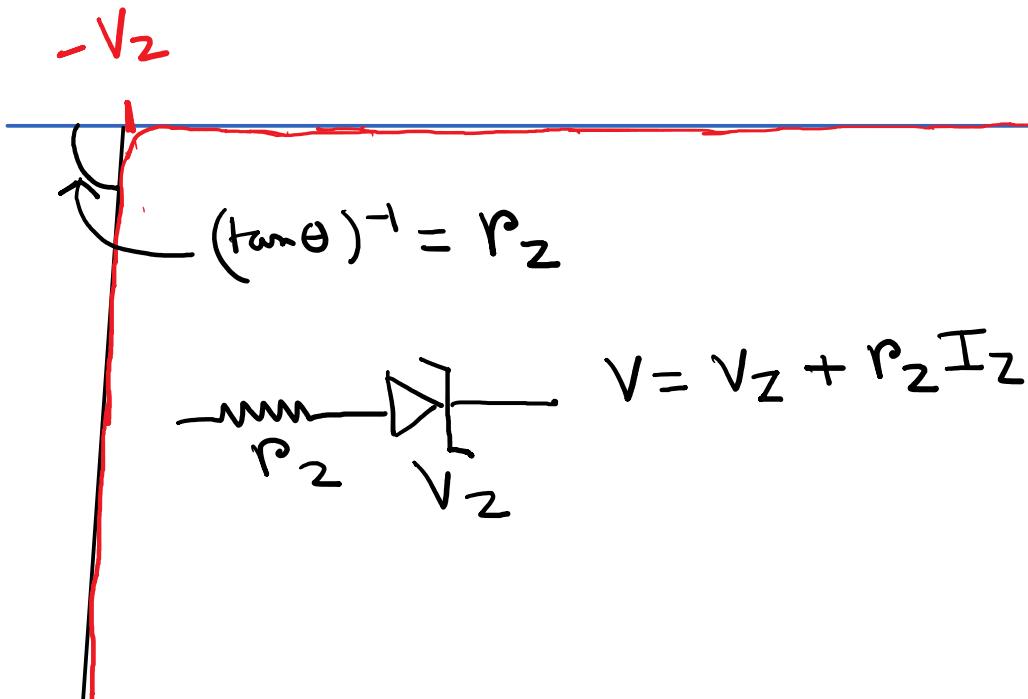

$$V = V_Z + r_2 I_Z$$

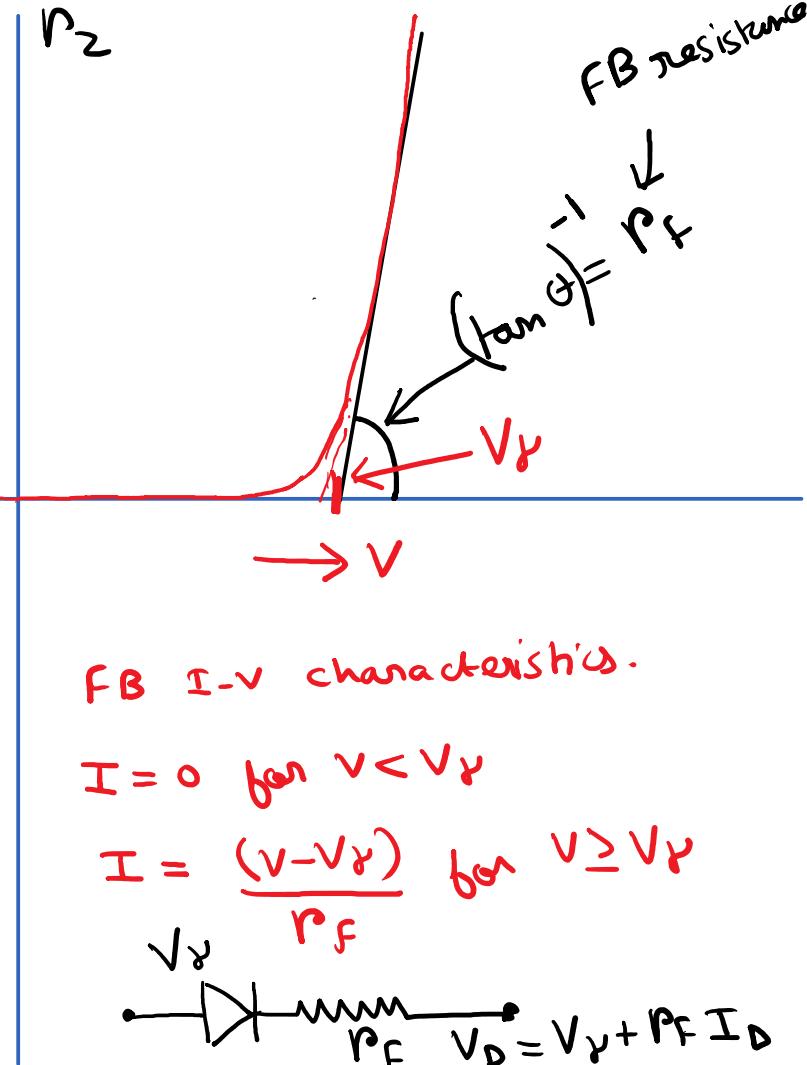

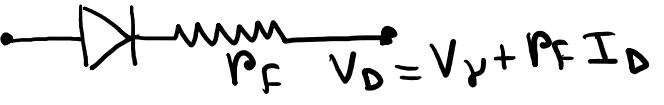
$$V_D = V_\gamma + r_f I_D$$

$$V_i = 20V \text{ (can vary by } \pm 25\%)$$

I_L can vary between 0mA to 20mA

Zener diode is non-ideal with


$$P_2 = 5\mu\text{W}$$

$$I_2(\min) = 5\text{mA}$$

The voltage across the Zener diode is

$$10V \text{ at } I_2 = 25\text{mA}$$

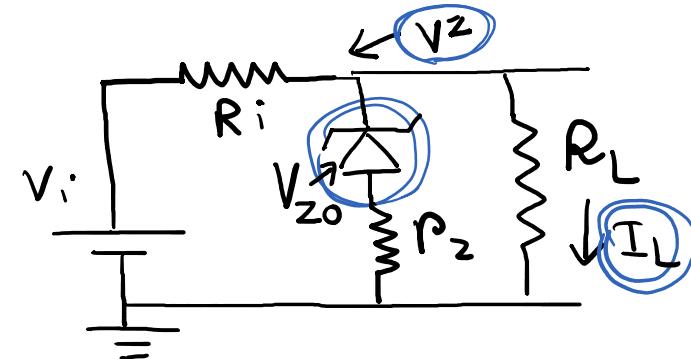What is the value of R_i such that $I_2(\min)$ can be maintained under all situations



$$V^2 = V_{Z0} + I_2 P_2$$

$$\Rightarrow 10V = V_{Z0} + 25\text{mA} \times 0.005\mu\text{W}$$

$$\Rightarrow V_{Z0} = 9.875V$$

Zener current is minimum when V_i is minimum
and I_L is max

$$V_i^{\min} = 20V - \frac{25}{100} \times 20V = 15V$$

$$I_L^{\max} = 20mA$$

$$V_i^{\min} = R_i \left\{ I_2^{\min} + I_L^{\max} \right\} + \left\{ V_{Z0} + R_Z I_2^{\min} \right\}$$

$$15V = R_i \left\{ 5mA + 20mA \right\} + \left\{ 9.875 + 5\Omega \times 0.005A \right\}$$

$$\Rightarrow R_i \times 25mA = 15V - 9.875V - 0.025V = 5.1V$$

$$\Rightarrow R_i = \frac{5.1V}{25mA} = 0.204k\Omega$$

Parameters to judge the efficiency of a voltage regulator:-

Source regulation: $\frac{\Delta V_L}{\Delta V_S} \times 100\% \approx \frac{P_2}{R_i} \times 100\%$

$P_2 \ll R_i, R_L$


Load Regulation = $\frac{V_{L, no\text{-load}} - V_{L, full\text{-load}}}{V_{full\text{-load}}} \times 100\%$

$V_{L, no\text{-load}}$ = output voltage when $I_L = 0$
 \rightarrow it will be at maximum rated

V_L , full-load = output voltage at 100% load current

Assumption:-

$$P_2 \ll R_i \text{ and } R_L$$

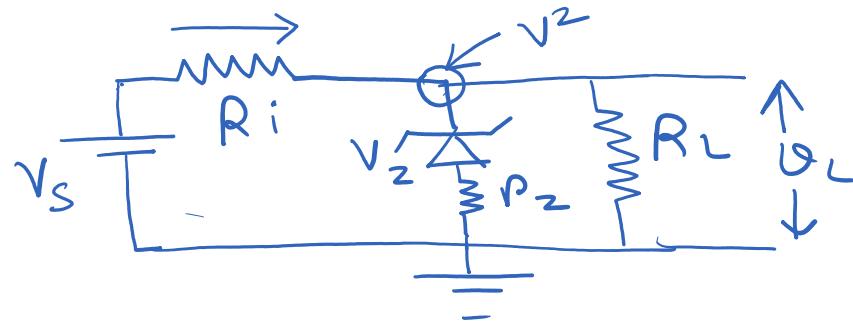

Source regulation.

$$\frac{\Delta V_L}{\Delta V_s} \times 100 \%$$


$$\Delta I_{R_i} = \frac{\Delta V_s}{R_i} \quad (\because V_L \approx V_2)$$

$$\Delta I_2 \approx \Delta I_{R_i} = \frac{\Delta V_s}{R_i}$$

$$\left. \begin{aligned} \Delta V_L &\approx \Delta V_2 \approx \Delta I_2 \times R_2 \\ &\approx \frac{\Delta V_s}{R_i} \times P_2 \\ \Rightarrow \Delta V_L / \Delta V_s &\approx \frac{P_2}{R_i} \end{aligned} \right\}$$

Clippers:

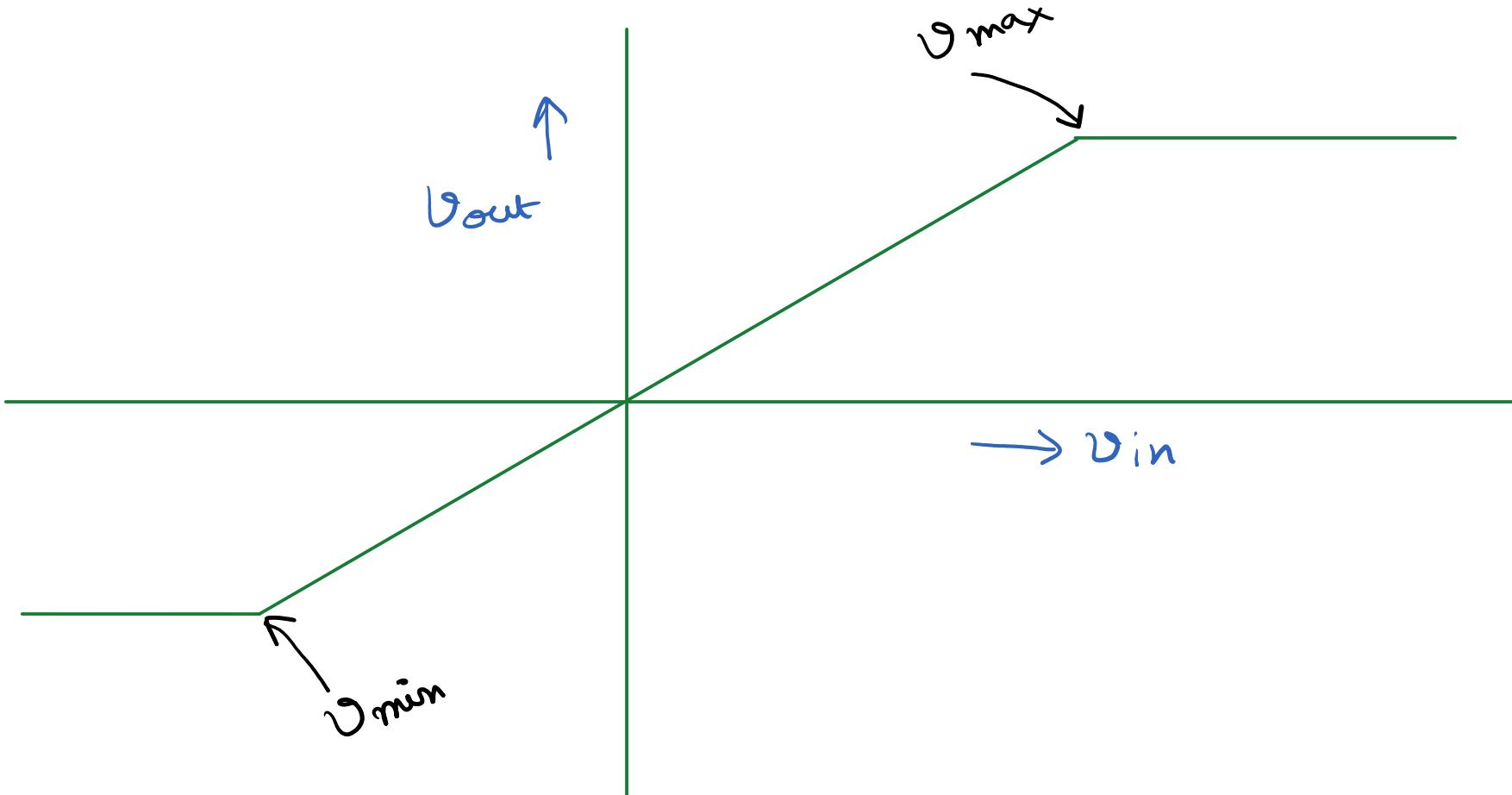Clippers limit the output voltage upto a maximum possible value or a minimum possible value or both. They basically limit the output voltage to a maximum or minimum possible value or both. These are also known as voltage limiters.



Clippers that limit the maximum positive voltage are called positive clippers.

Clippers that limit the minimum negative voltage are known as negative clippers.

And clippers that limit both the maximum positive voltage and the minimum negative voltage are called Dual clippers

① $V_{in} \geq V_B + V_f \rightarrow$ Diode is conducting.

$V_{in} < V_B + V_f \rightarrow$ Diode is non-conducting


② Diode is conducting $\rightarrow V_o \approx V_B + V_f$

Diode is not conducting

\rightarrow no current flows through the resistor $\rightarrow V_o = V_i$

③ $V_{in} \geq V_B + V_f, V_o \approx V_B + V_f$


$V_{in} < V_B + V_f, V_o = V_{in}$

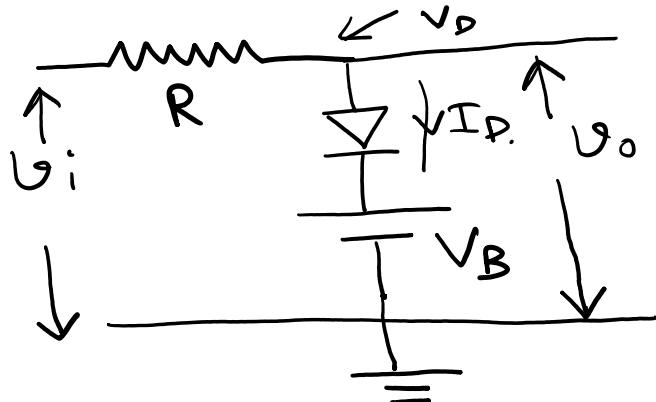

Assume: Ideal diode

$$V_f = 0$$

Positive clipper

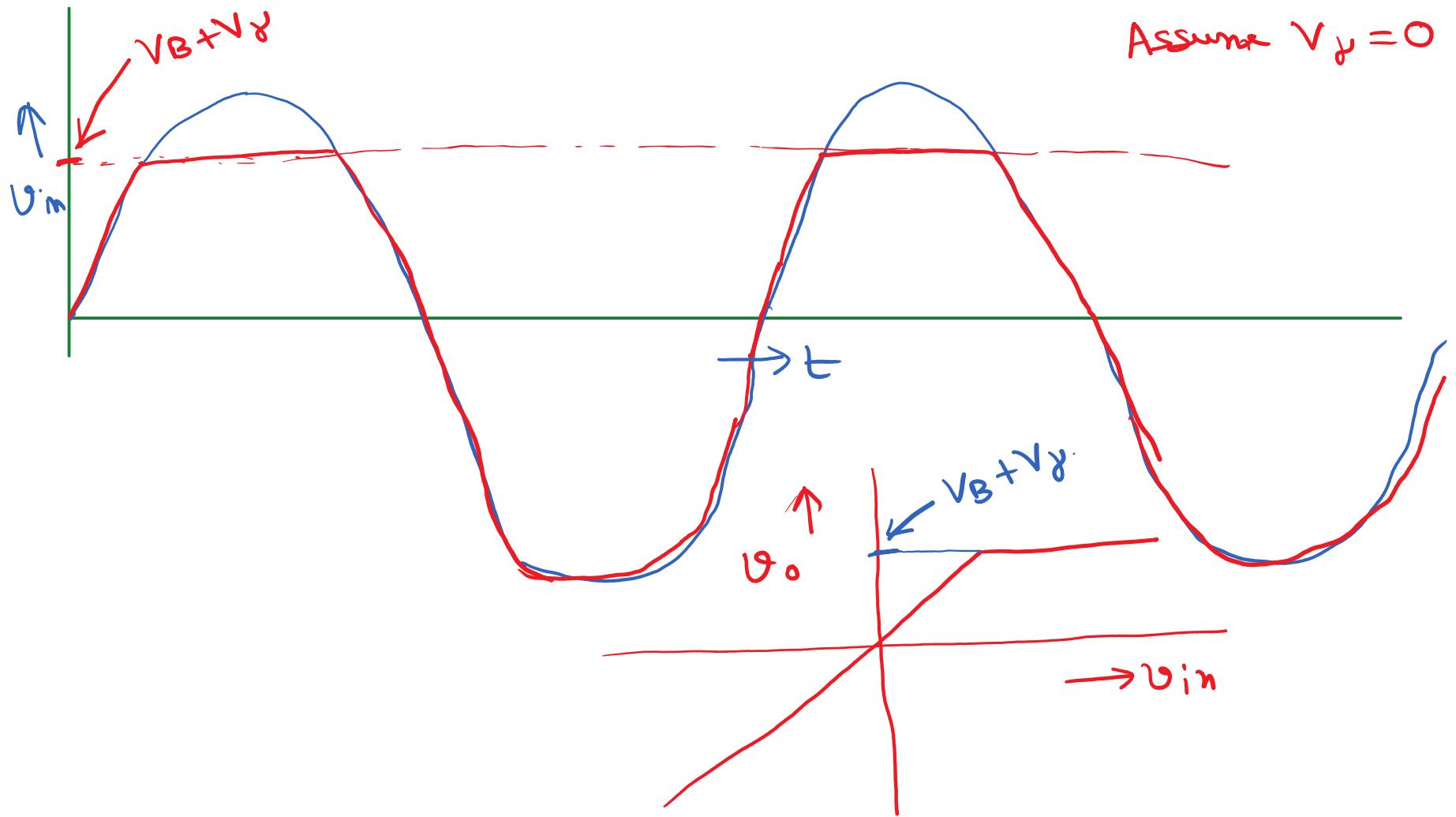

Diode conducting $\rightarrow V_{in} \leq V_B - V_d$


Diode is non-conducting.


$$V_{in} > V_B - V_d$$

Diode is conducting $\rightarrow V_o = V_B - V_d$

Diode is non-conducting

$$\rightarrow V_o = V_{in}$$

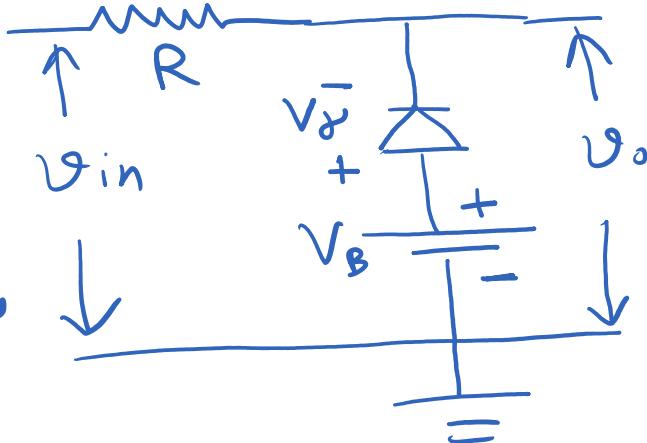


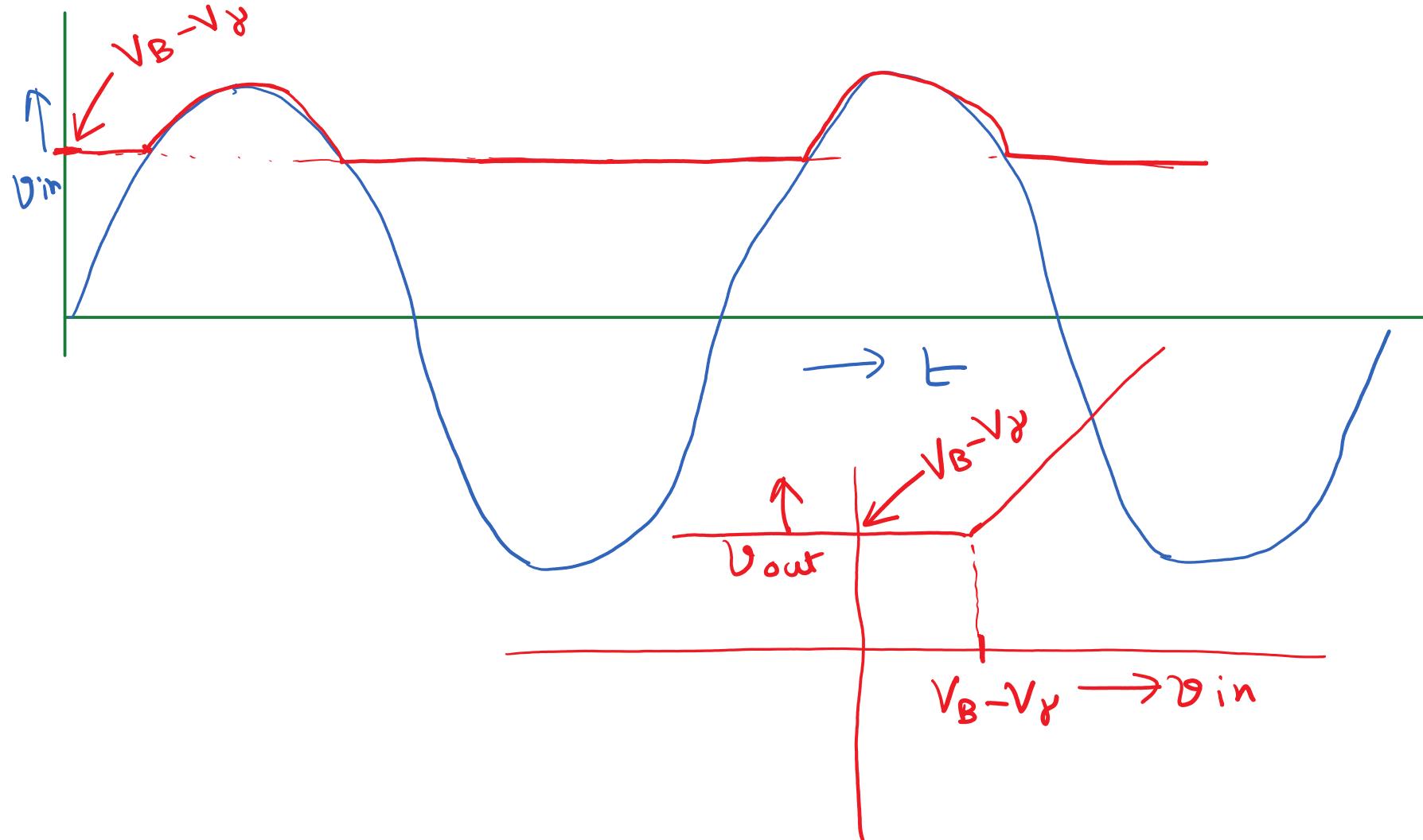

Diode is conducting $\rightarrow v_{in} \geq -V_B + V_d$


Diode is not conducting \rightarrow

$$v_{in} < -V_B + V_d$$

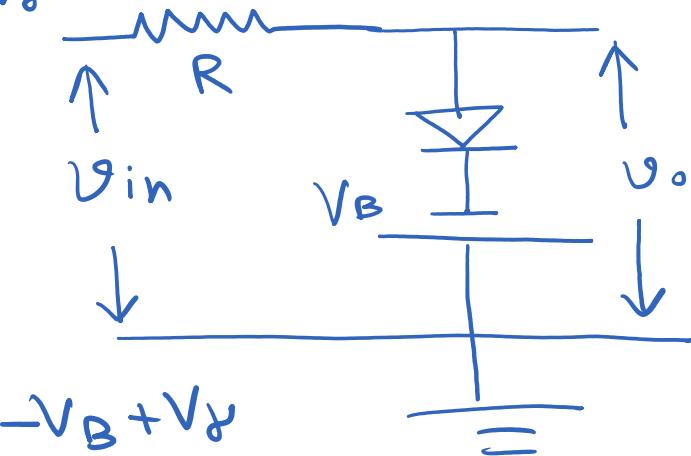

Diode is conducting $\rightarrow v_o \approx -V_B + V_d$

Diode is not conducting $v_o = v_{in}$

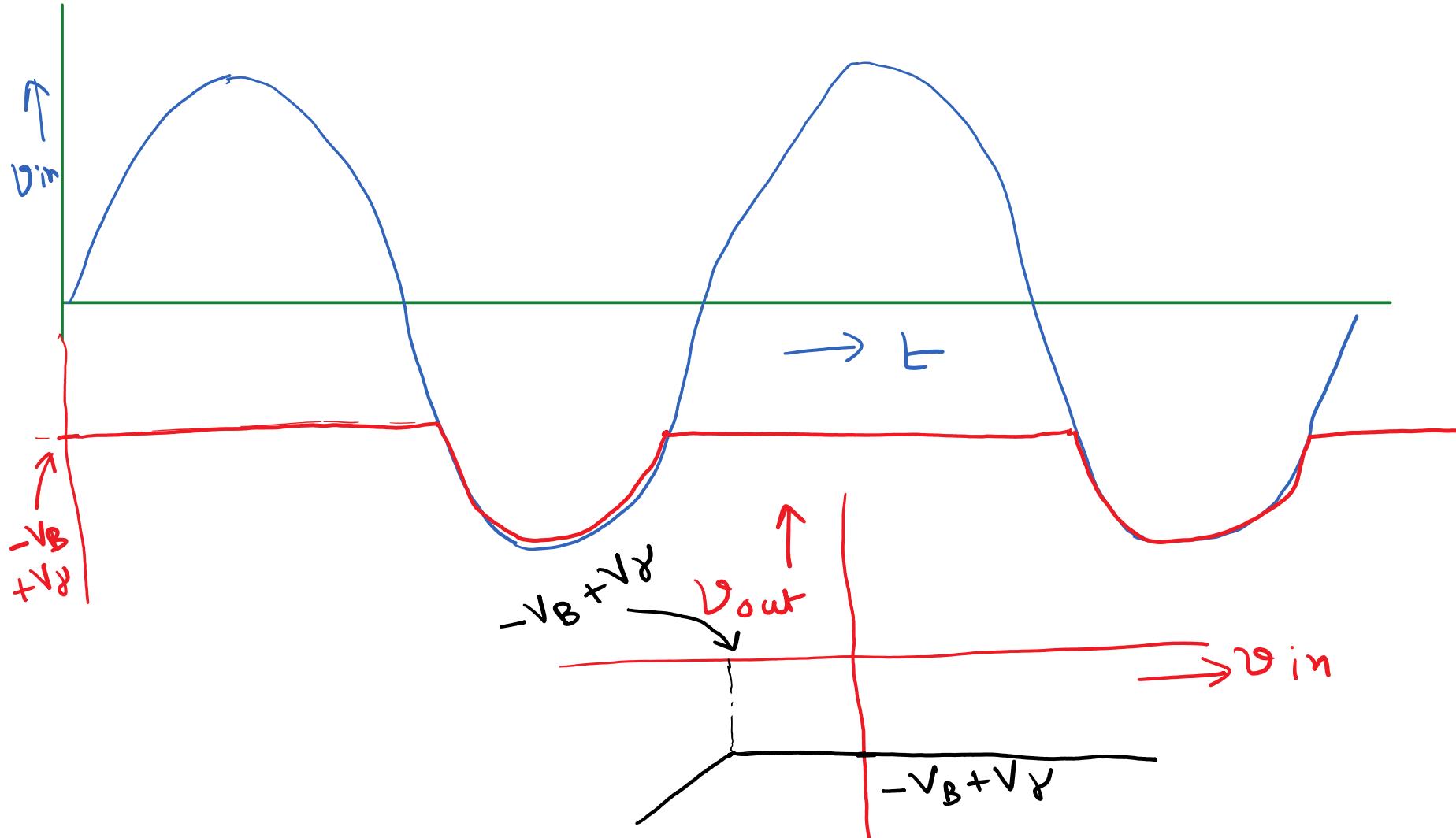

$-\nabla_B + \nabla_\chi$

Diode is conducting \rightarrow

$$v_i \leq -V_B - V_f$$

Diode is not conducting \rightarrow


$$v_i > -V_B - V_f$$


Diode is conducting


$$v_o \approx -V_B - V_f$$

Diode is non-conducting

$$v_o = v_{in}$$

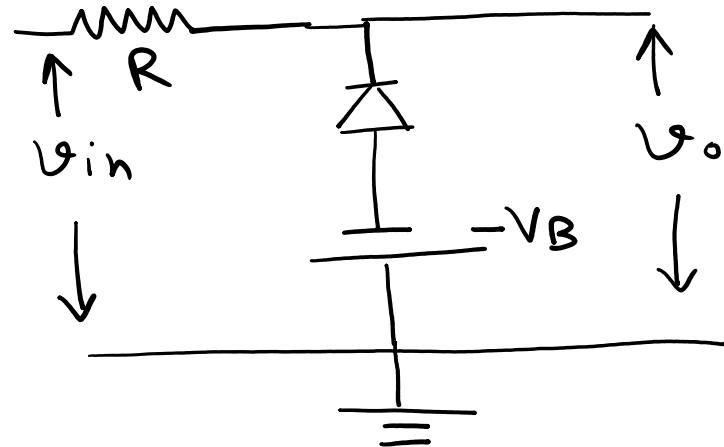

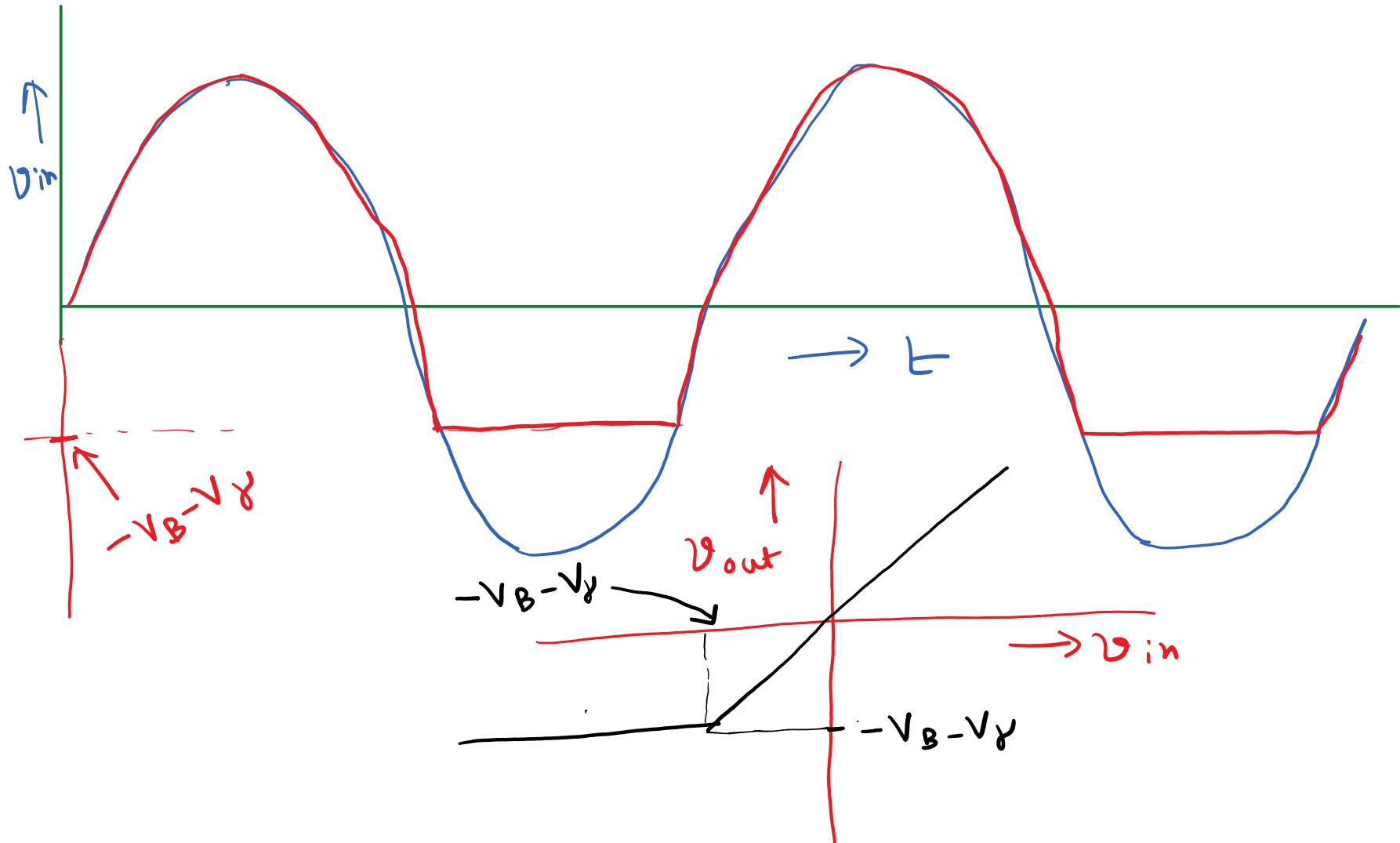

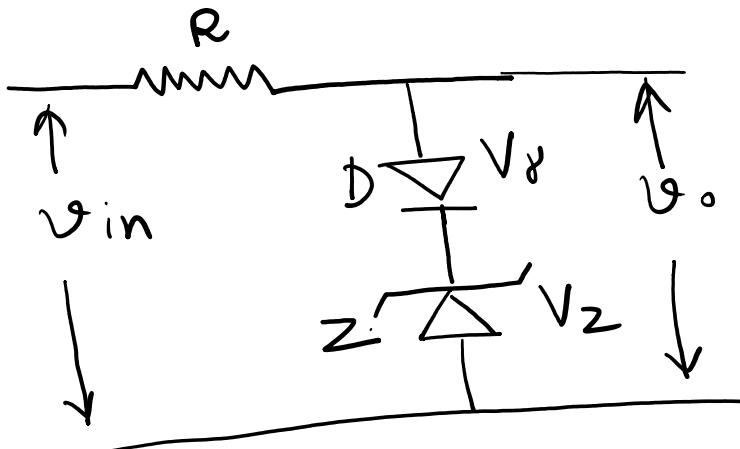

Assume that $v_x = 0$
 Assume that D
 never goes to
 the breakdown
 regime for the
 range of v_i


D is conducting when


$$v_{in} \geq v_z + v_x = v_z \quad (\because v_x = 0)$$

D is not conducting.

$$v_{in} < v_z + v_x = v_z \quad (\because v_x = 0)$$

$\left \begin{array}{l} \text{D conducting} \\ \Rightarrow v_o \approx v_z + v_x \\ = v_z \quad (\because v_x = 0) \end{array} \right.$	$\left \begin{array}{l} \text{D non-conducting} \\ v_o = v_{in} \end{array} \right.$
--	---

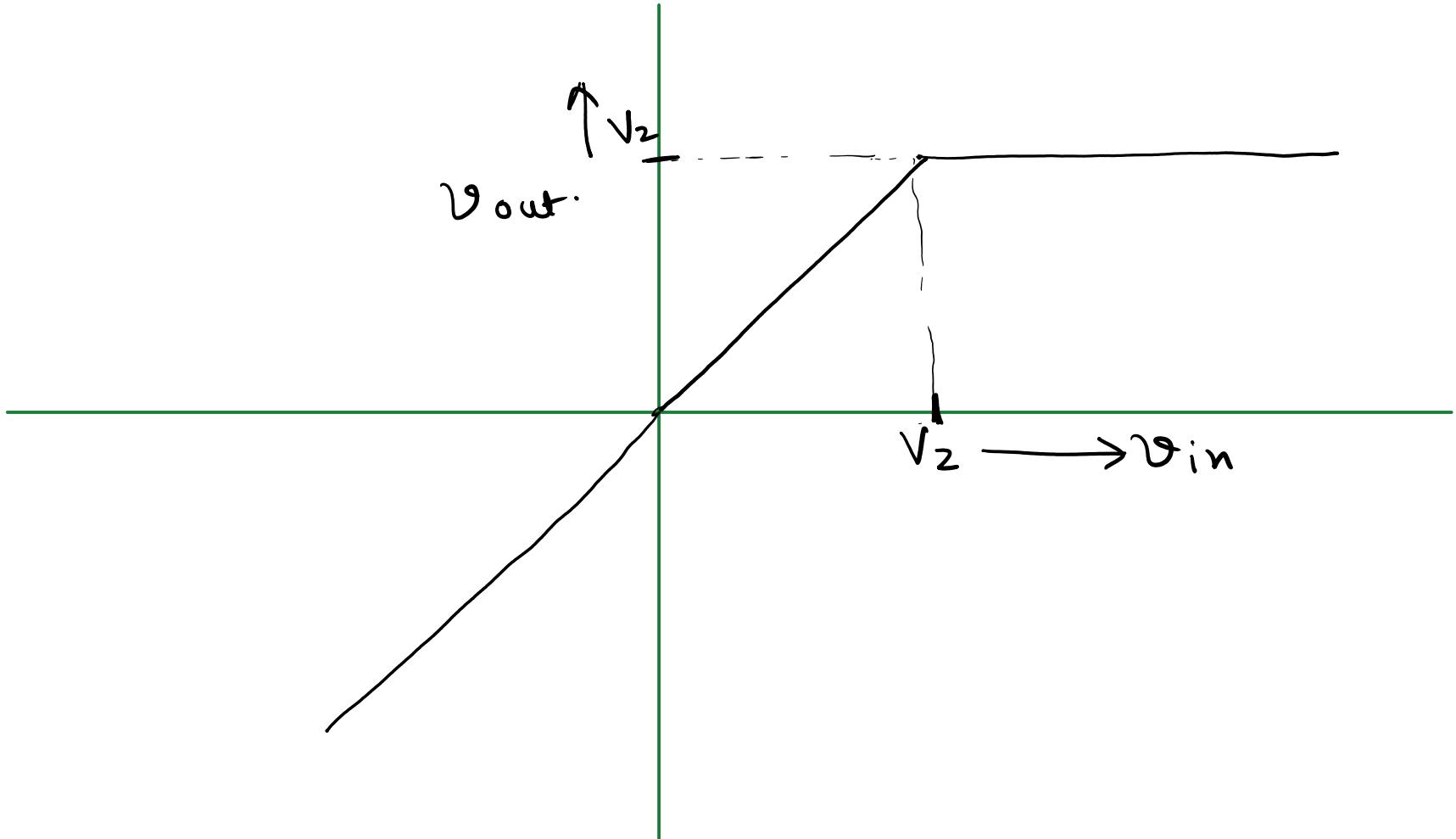

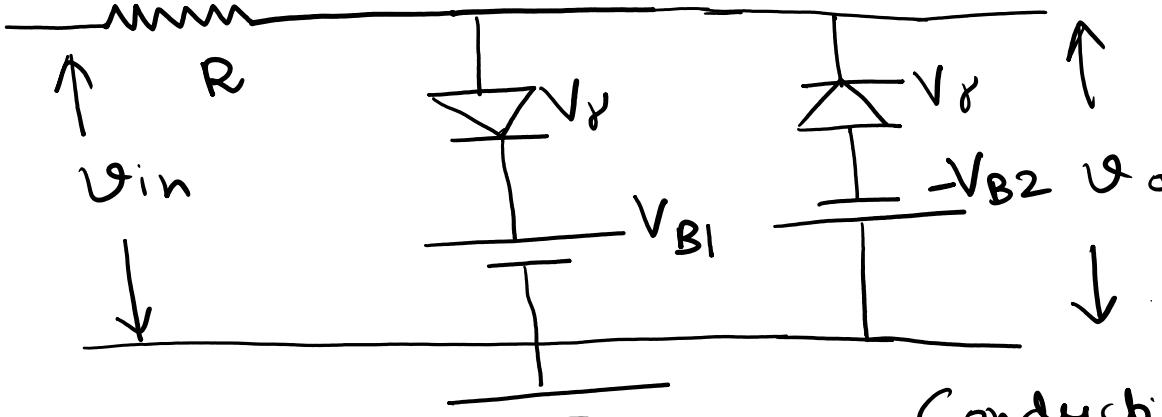

Conducting when

$$v_{in} \geq V_{B1} + V_d$$

$$\text{or } v_{in} \leq -V_{B2} - V_d$$

