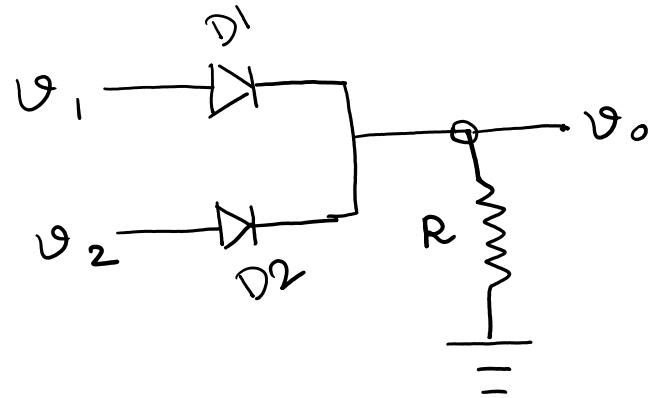


Class - 14.1

OR-Gate




$$V_f = 0.7V$$

$v_o > 2.5 \Rightarrow \text{logic high}$   
 $v_o \leq 2.5V \Rightarrow \text{logic low}$

$v_1$	$v_2$	$v_o$
0V	0V	0V
5V	0V	4.3V
0V	5V	4.3V
5V	5V	4.3V

Truth Table		
$v_1$	$v_2$	$v_o$
0	0	0
1	0	1
0	1	1
1	1	1

AND gate

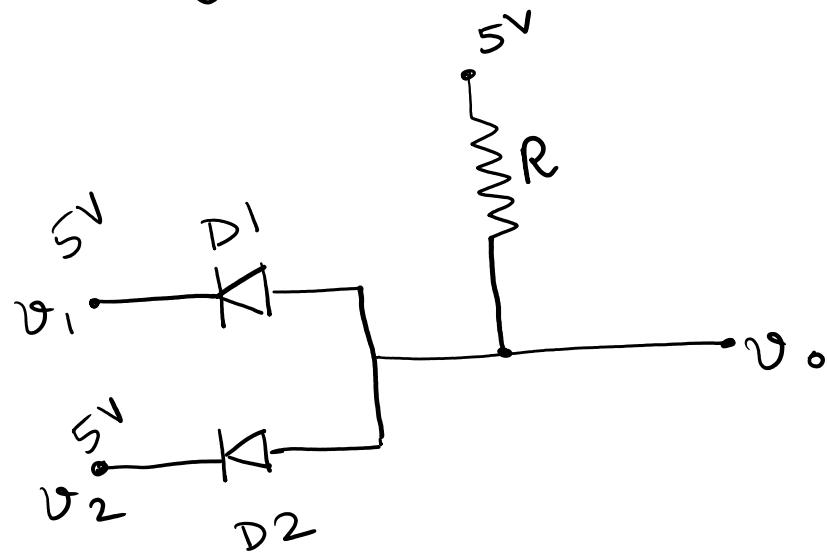

$v_1$	$v_2$	$v_o$
0V	0V	0.7V
5V	0V	0.7V
0V	5V	0.7V
5V	5V	5V


Truth Table

$v_1$	$v_2$	$v_o$
0	0	0
1	0	0
0	1	0
1	1	1

We can't construct not gates with the help of diode.

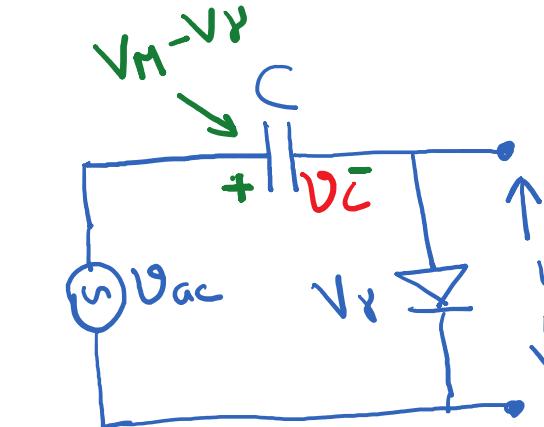
## Class-14.2


Clampers:- Circuits that alter or change the DC level of a signal.



$$V_{ac} = V_M \sin \omega t$$
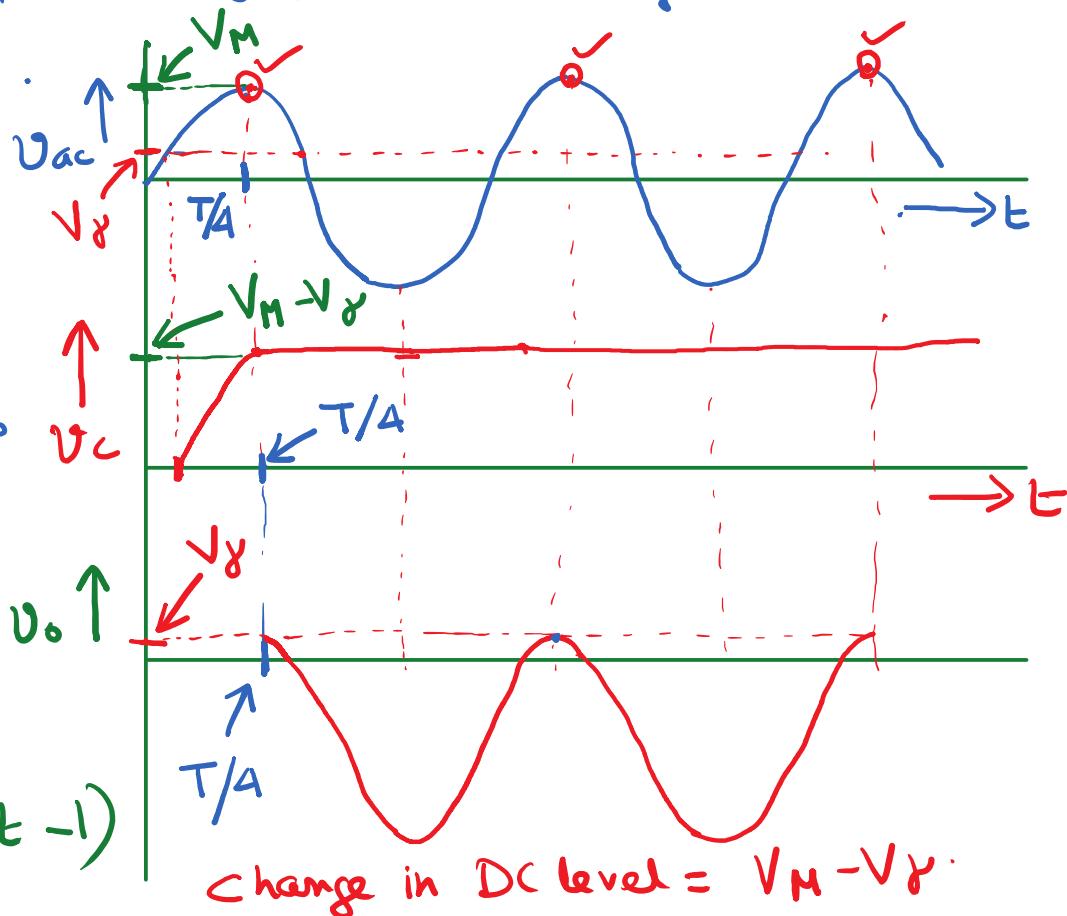
$$\begin{aligned} V_o &= V_{ac} - V_c \\ &= V_y + V_M (\sin \omega t - 1) \end{aligned}$$




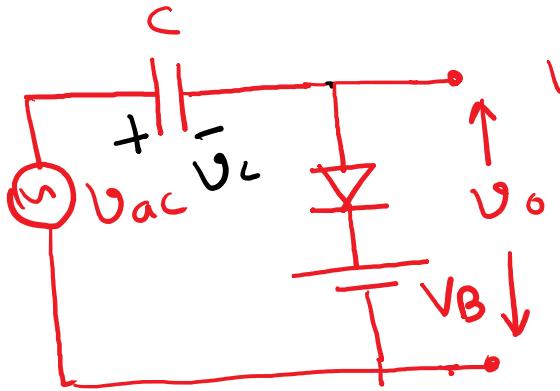

$$V_{ac}^{\max} = V_c^{\max} + V_\gamma + V_B$$

$$\Rightarrow V_c^{\max} = V_{ac}^{\max} - (V_\gamma + V_B)$$

$$= V_M - (V_\gamma - V_B)$$

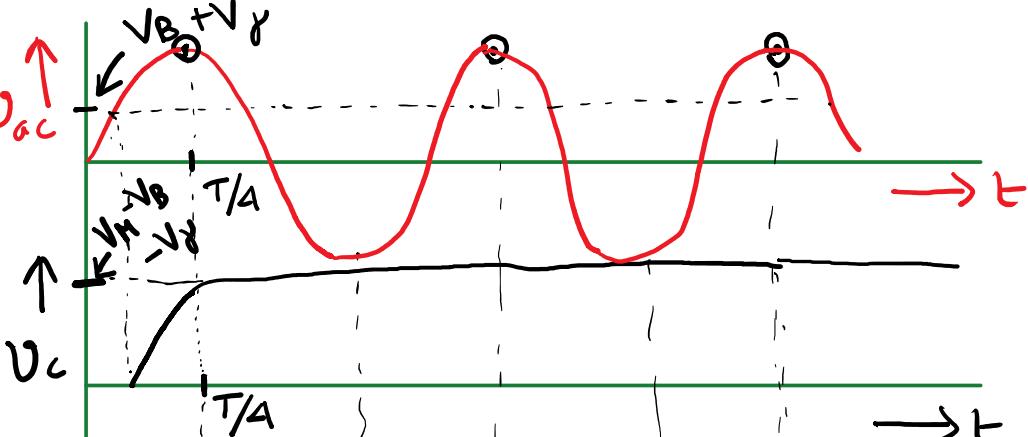


$$V_{ac} = V_c + V_B \Rightarrow V_o = V_{ac} - V_c$$

$$V_o = V_M \sin \omega t - \underbrace{(V_M - V_B - V_\gamma)}_{\text{shift in DC level.}}$$

$$V_\gamma = 0.7V, \quad 5V < V_{PS} < 10V.$$

$$I_D^{\min} = 2mA, \quad P_D^{\max} = 10mW.$$

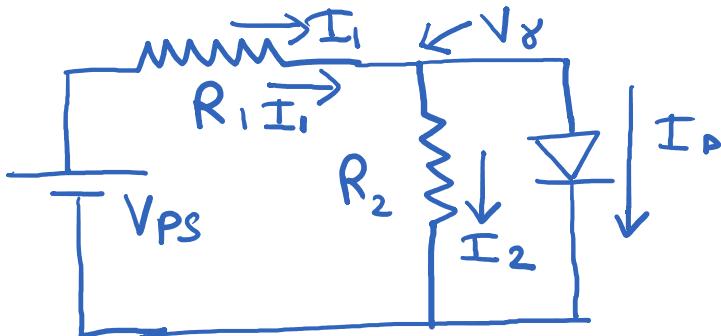Determine appropriate values of  
R<sub>1</sub> and R<sub>2</sub>



A:  $I_D^{\max} \approx \frac{P_D^{\max}}{V_\gamma} = \frac{10mW}{0.7V} = 14.28mA$

$$I_D^{\min} = 2mA$$

$$I_2 \equiv \frac{V_\gamma}{R_2}$$

$$\frac{V_{PS}^{\max} - V_\gamma}{R_1} = I_D^{\max} + I_2 \Rightarrow \frac{9.3}{R_1} = 14.28 + \frac{0.7}{R_2}$$

$$\Rightarrow 9.3/R_1 - 0.7/R_2 = 14.28 \quad - \textcircled{1}$$

$$\frac{V_{PS}^{\min} - V_\gamma}{R_1} = I_D^{\min} + \frac{0.7}{R_2}$$

$$\Rightarrow 4.3/R_1 - 0.7/R_2 = 2mA \quad - \textcircled{2}$$

$$\Rightarrow 4 \cdot 3 / R_1 - \frac{0.7}{R_2} = 2 \text{mA} \quad -\textcircled{2}$$

Subtracting ② from ① we get

$$5/R_1 = 12.28 \rightarrow R_1 = \frac{5}{12.28} \text{ kJ} = 0.407 \text{ kJ}$$

From ①


$$\begin{aligned}0.7/R_2 &= \frac{9.3}{R_1} - 14.28 \\&= 22.8 - 14.28 \\&= 8.57\end{aligned}$$

$$R_2 = \frac{0.7}{8.57} = 0.0816 \text{ kJ}$$

$$R_1 = 0.407 \text{ kJ}$$


$$R_2 = 0.0816 \text{ kJ}$$


Bipolar junction


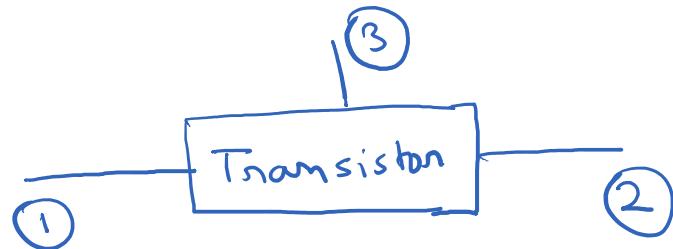
Transistor



Transistor: Three terminal devices. Conductance between two terminals is controlled by a current or voltage at the 3rd terminal.


Bipolar:- The action of both majority and minority carriers are required for the transistor action.


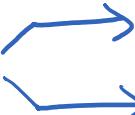
n-type  majority carrier  $\rightarrow$  electrons  
 minority carrier  $\rightarrow$  holes.

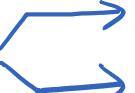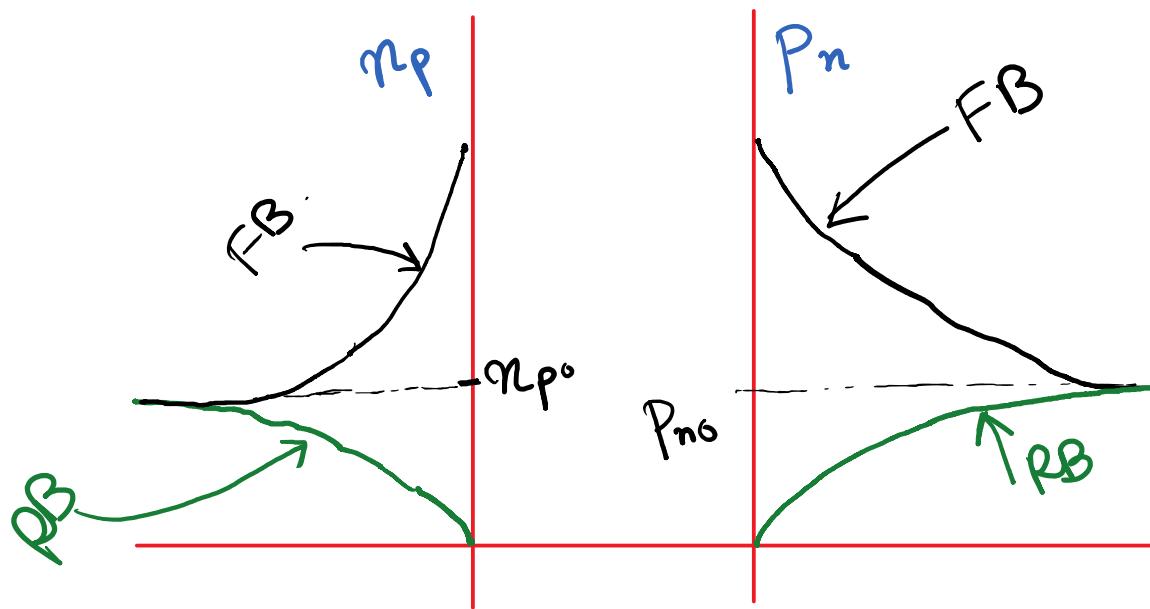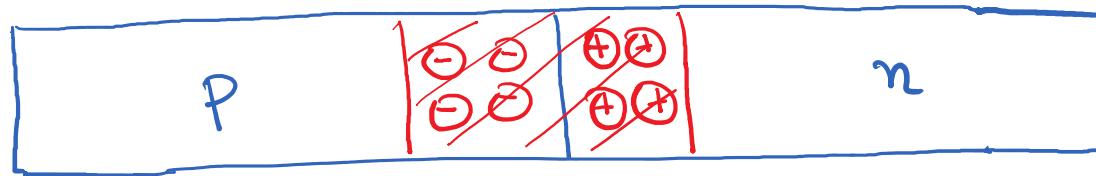p-type  majority carriers  $\rightarrow$  holes  
 minority carriers  $\rightarrow$  electrons.



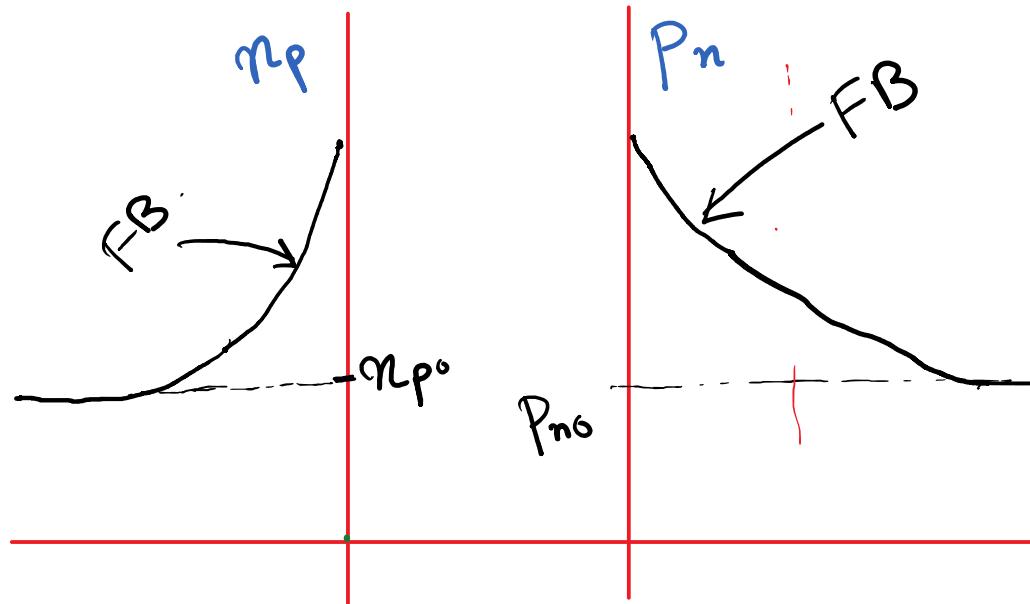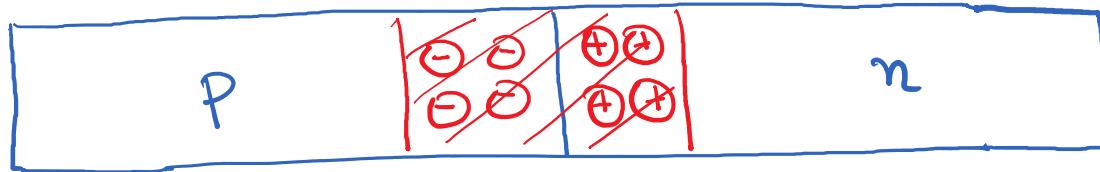

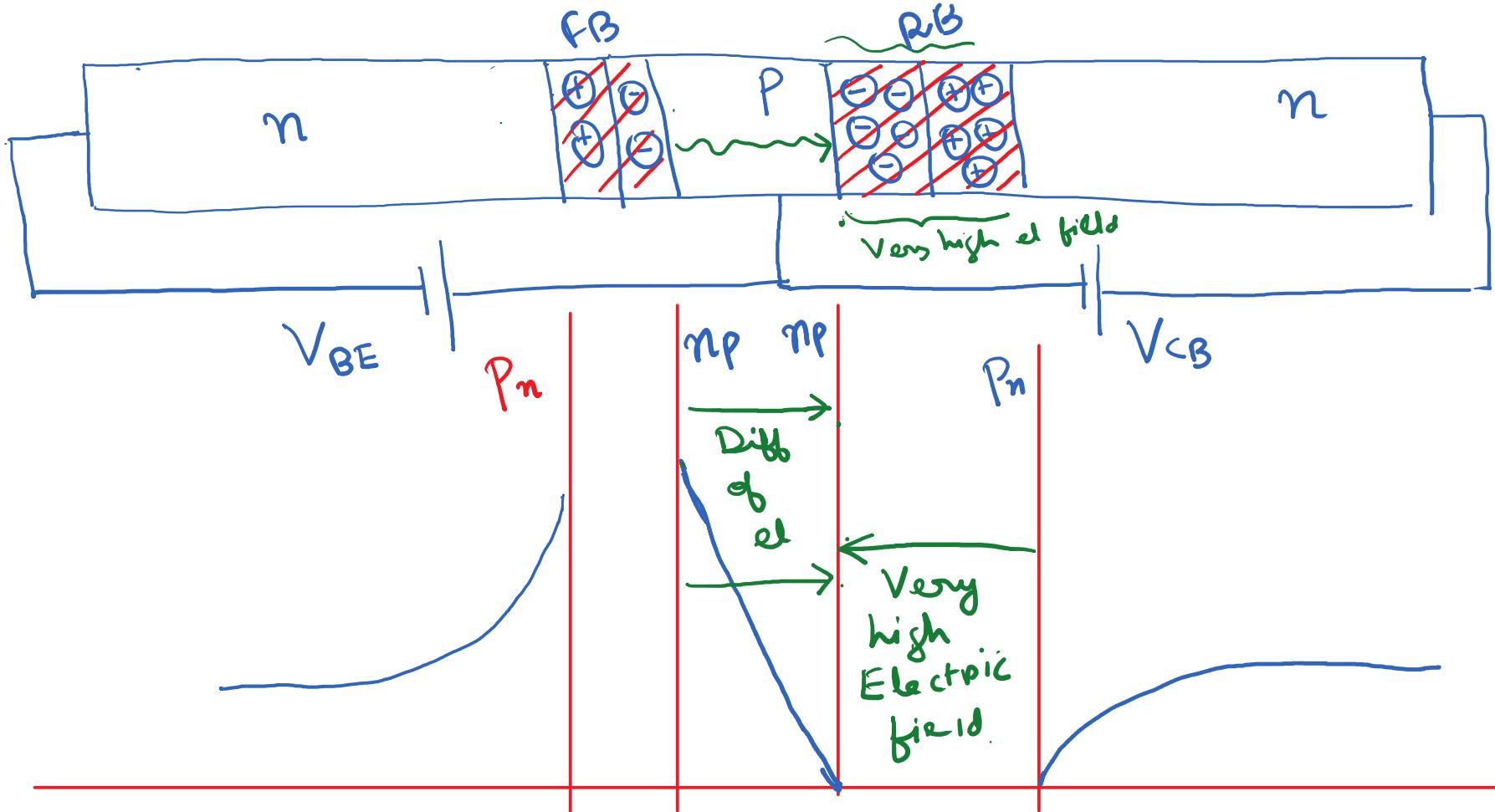

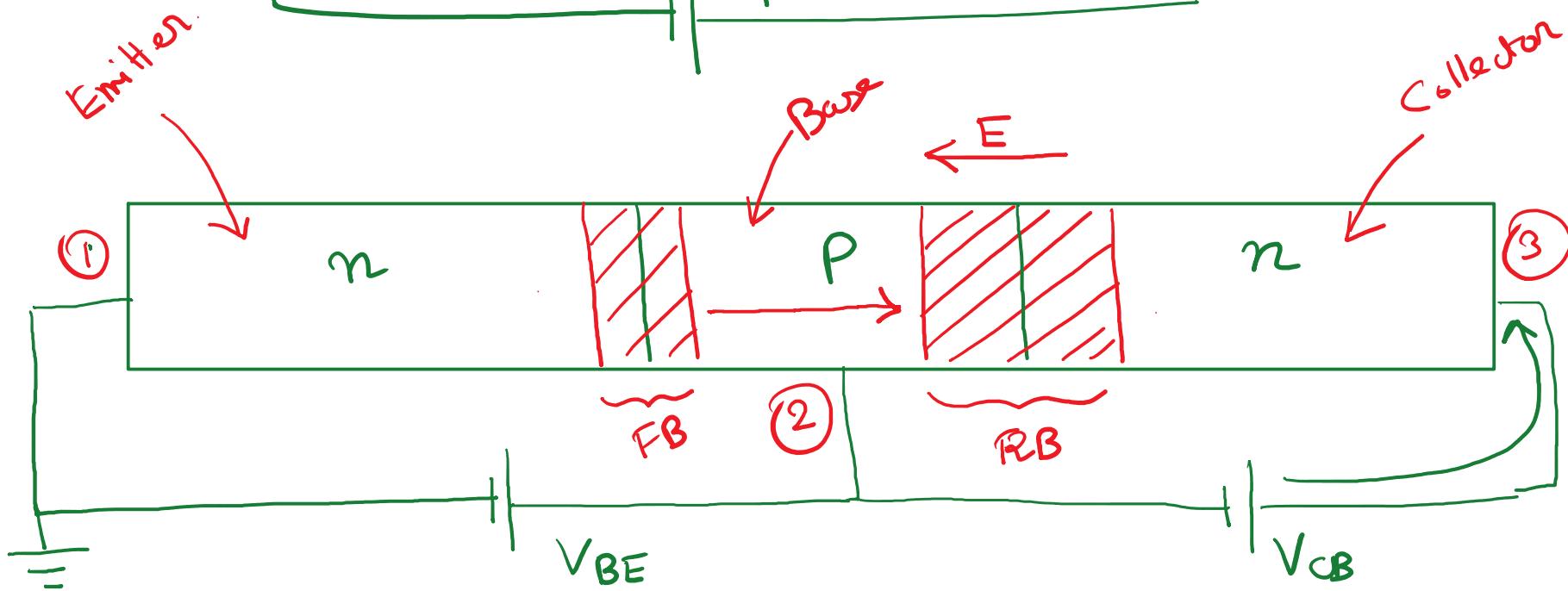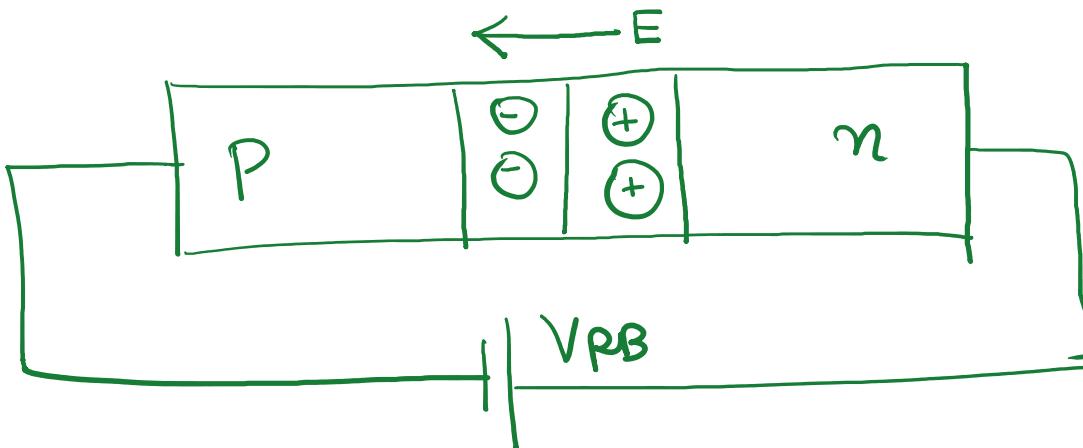

When  $V_{BE}$  increases, more electrons are injected from the emitter into the p-type Base. As the injected electrons in the p-type Base increase, more electrons are swept from the Base into the collector by the reverse biased base to collector junction. So, the collector current increases. So, with increase in  $V_{BE}$ , the collector current increases.


## nPn Transistor.

$$I_E = I_C + I_B$$

Collector

Emitter

Base

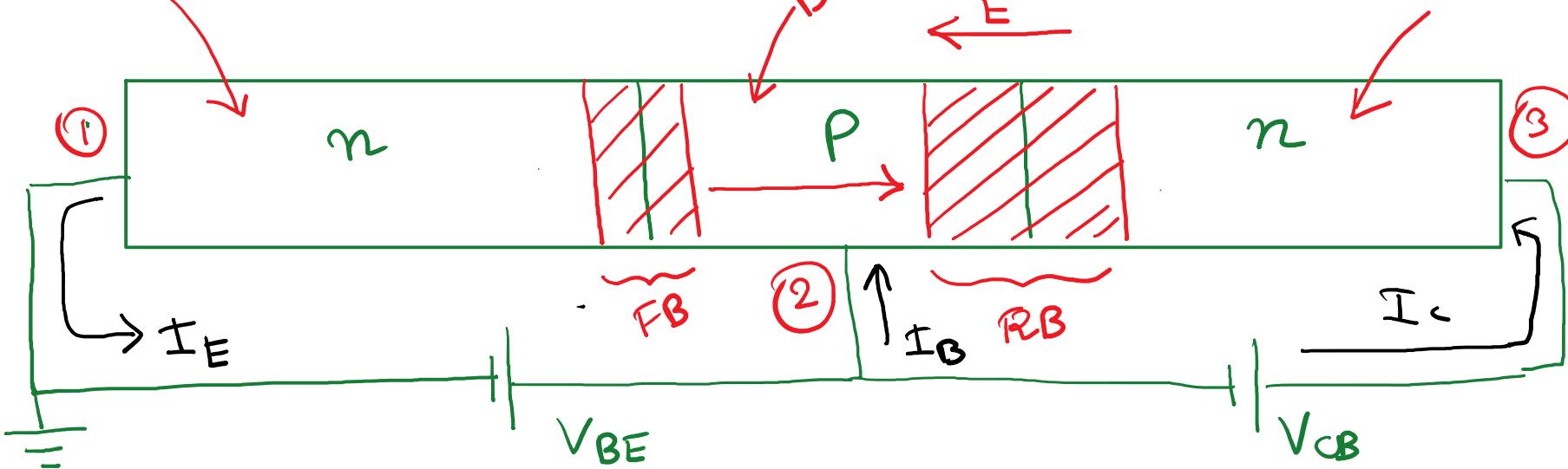

Components of  $I_B$ : ① Some of the electrons injected from the emitter to the Base flows out of the Base terminal.

② The Base also injects excess holes in the n-type emitter and these holes that diffuse from the base to the emitter needs to be replenished by the base current.

\* Emitter is heavily doped so that more electrons can diffuse from the emitter to the base during forward bias. This increases the electron concentration in the Base.

\* Collector is moderately doped. Base is lightly doped.

$$I_E = I_C + I_B$$

Our intention is to control the collector current via the base-to-emitter voltage or the base/emitter current.

For ideal transistor,  $I_B = 0$  and we want all the emitter current to flow through the collector.

For a good transistor, base current should be as low as possible.





For a good transistor  $\left\{ \begin{array}{l} I_B \ll I_E, I_C \\ I_E \approx I_C \end{array} \right.$

The Base current or the collector current is a fixed fraction of the emitter current.  
Generally for a good transistor,


$$\frac{I_C}{I_E} > 0.99$$
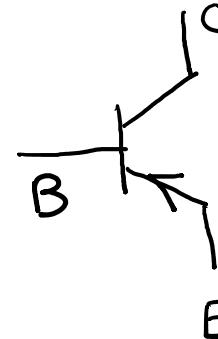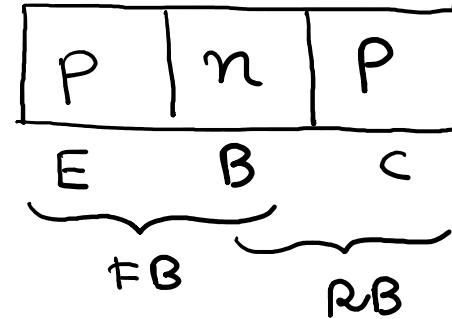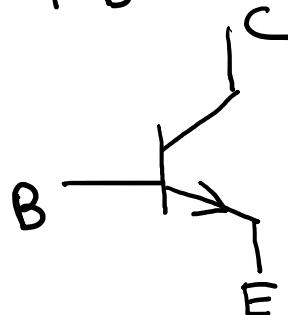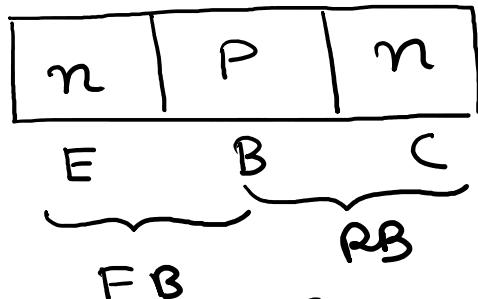
## Class-16

$$\frac{I_C}{I_E} = \alpha = \text{common-Base current gain.}$$



Common-Base configuration:-

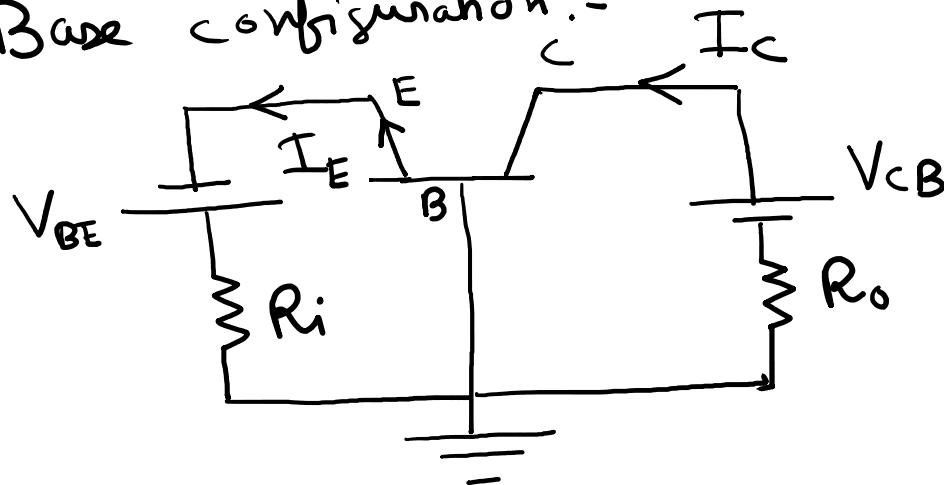

$I_E \rightarrow$  input current


$I_C \rightarrow$  output current

$$\frac{I_C}{I_E} = \alpha = \text{common-Base current gain}$$

$$I_E \approx I_S \exp \left\{ \frac{V_{BE}}{V_T} \right\} \quad (V_{BE} \gg V_T)$$

$$\left\{ \begin{array}{l} I_B \approx \frac{I_S}{\beta + 1} \exp \left\{ \frac{V_{BE}}{V_T} \right\} \\ I_C = I_E - I_B = \frac{\beta}{\beta + 1} I_S \exp \left\{ \frac{V_{BE}}{V_T} \right\} \end{array} \right.$$

### Common-Base Characteristics

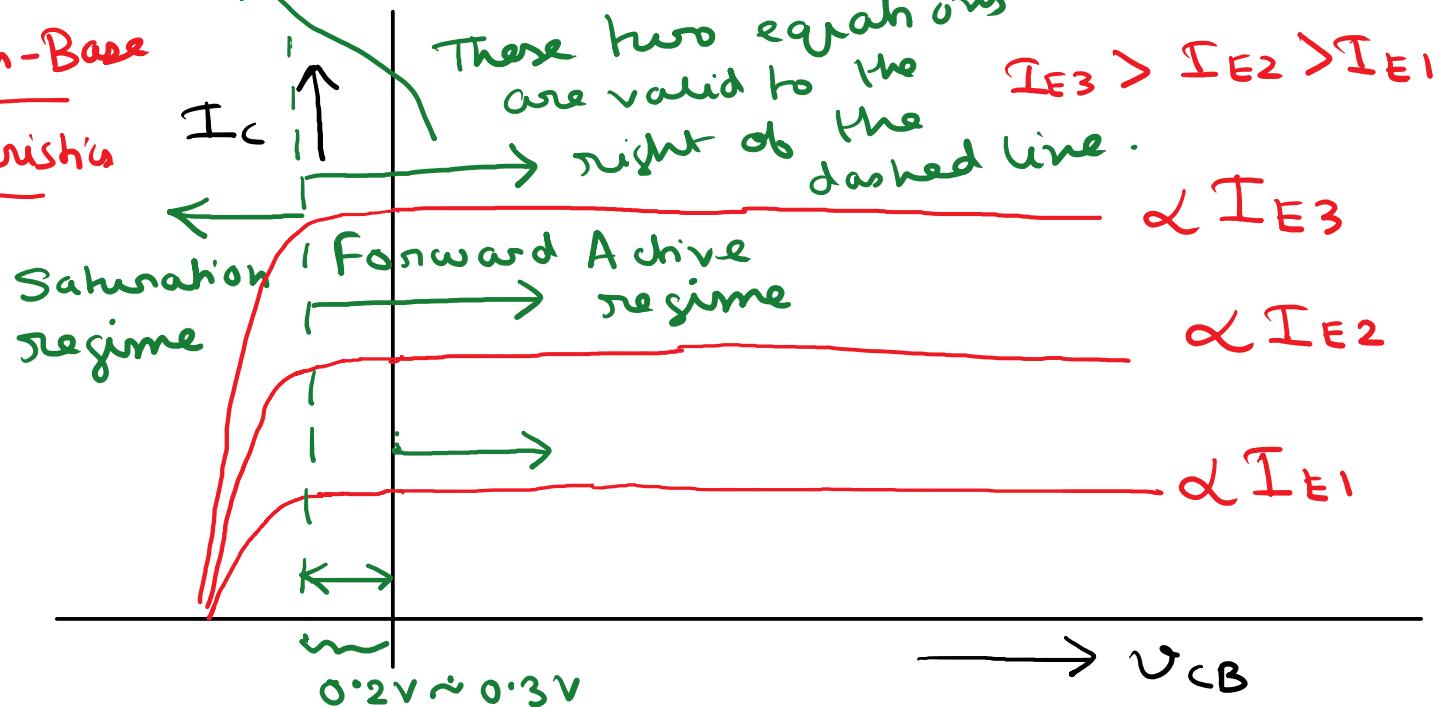

Ideally we do not want the collector current to vary with  $V_{CB}$ . We only want the collector current to vary with  $V_{BE}$ . So, it's important to see the variation of  $I_C$  with  $V_{CB}$

- ① forward Active regime  $\rightarrow$  collector current does not vary with  $V_{CB}$
- Base-emitter junction is forward Biased  
 $V_{BE} \geq V_x$
- The collector-Base junction is mainly reverse Biased
- ② Saturation regime:  $\rightarrow$  collector current varies with collector to Base voltage
- Base-emitter junction is forward biased.  
 $(V_{BE} \geq V_x)$
- The collector to Base junction is forward biased.

③ Cut-off regime  $\rightarrow$  The Base-to-Emitter is in cut-off.

The Base-Emitter junction is not conducting ( $V_{BE} < V_\alpha$ )

The Base-Emitter junction is reverse Biased.

④ Reverse Active regime  $\rightarrow$  The emitter and collector interchange their action

The Base-emitter junction is reverse Biased

Base -collector junction is forward Biased.

$$\alpha = \frac{50}{51}$$

$I_B, I_C, V_{CE}$ ?

$$I_C = \alpha I_E$$

$$I_B = I_E - I_C = (1 - \alpha) I_E$$


$$V_{BE(on)} = V_\beta = 0.7V$$

$$2V = I_B \times 10k\Omega + V_{BE(on)}$$

$$+ I_E \times 1k\Omega$$

$$= I_B \times 10k\Omega + 0.7V + \frac{I_B}{1-\alpha} \times 1k\Omega$$
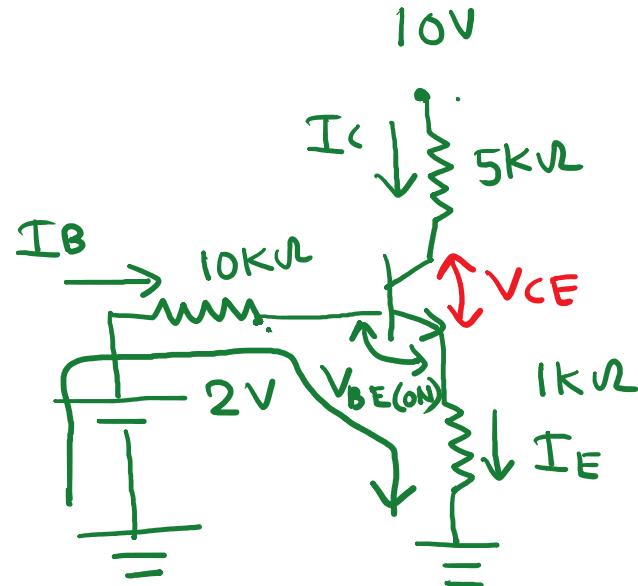
$$\Rightarrow 1.3V = 10I_B + 51I_B = 61I_B$$



$$\boxed{\begin{aligned}1 - \alpha &= \frac{1}{51} \\ \frac{1}{1 - \alpha} &= 51\end{aligned}}$$

$$I_B = \frac{1.3}{61} \text{ mA} = 0.0213 \text{ mA}$$

$$I_E = \frac{I_B}{1-\alpha}$$

$$I_C = \alpha I_E = \frac{\alpha}{1-\alpha} I_B = \frac{\frac{50}{51}}{\frac{1}{51}} I_B$$


$$\begin{aligned} &= 50 I_B = 50 \times 0.0213 \text{ mA} \\ &= 1.06 \text{ mA} \end{aligned}$$

$$10V = 5k\Omega \times I_C + V_{CE} + I_E \times 1k\Omega$$

$$= 5 \times 1.06 + V_{CE}$$

$$+ 5 \times 0.0213$$

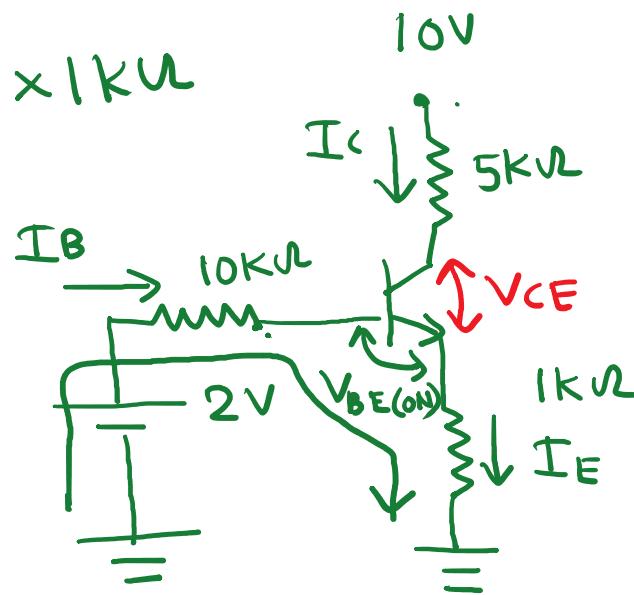
$$\Rightarrow V_{CE} = 10V - 6.45V \\ = 3.55V$$



Class - 17

Common Emitter Configuration:-


Common - Base  
config :-

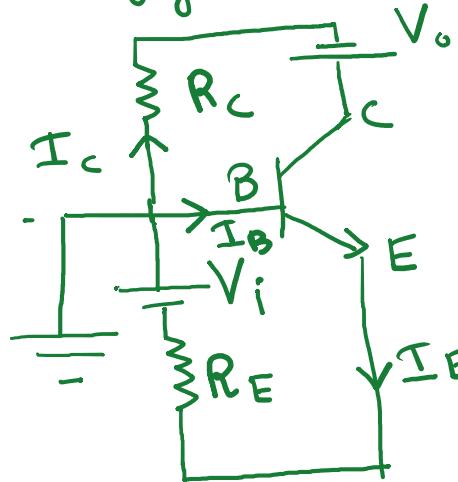

Input current :-  $I_E$

Output current :-  $I_C$

$$\alpha = \frac{I_C}{I_E}$$

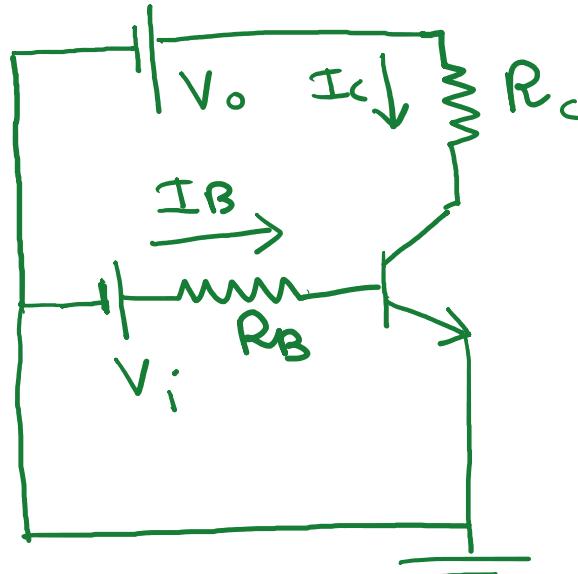

Input current :- Base current

Output current :- Collector current.

$$\frac{I_C}{I_B} = \beta \rightarrow \text{common-emitter current gain.}$$

$$\alpha = \frac{I_c}{I_E} \quad \textcircled{1} \quad \beta = \frac{I_c}{I_B} \quad \textcircled{2}$$

$$I_E = I_C + I_B$$

$$\Rightarrow \frac{I_E}{I_C} = 1 + \frac{I_B}{I_C} \quad \textcircled{3}$$

$$\Rightarrow \frac{1}{\alpha} = 1 + \frac{1}{\beta}$$

$$\Rightarrow \frac{1}{\beta} = \frac{1-\alpha}{\alpha}$$

$$\Rightarrow \beta = \frac{\alpha}{1-\alpha}$$

$$\Rightarrow \alpha = \frac{\beta}{1+\beta}$$

$$I_E = I_C + I_B$$

$$\Rightarrow I_E = \beta I_B + I_B$$

$$\Rightarrow (\beta + 1) I_B = I_E$$

$$\Rightarrow I_B = \frac{I_E}{(\beta + 1)}$$

These  
three eqn  
are only  
valid in  
the forward  
Active Mode

$$\left\{ \begin{array}{l} I_C = \alpha I_E \\ I_C = \beta I_B \\ I_B = \frac{I_E}{\beta + 1} \\ \alpha = \frac{\beta}{1 + \beta} \\ \beta = \frac{\alpha}{1 - \alpha} \end{array} \right.$$

For a good transistor

$$\begin{aligned} \alpha &> 0.99 \\ \beta &> 99 \end{aligned}$$

If the Base-to-emitter junction is a conducting state, then  $V_{BE} \approx V_{BE(\text{ON})} = V_\gamma$

If  $V_{BE} > 0$ , then this equation is valid irrespective of the Biasing condition of the collector-Base junction


The common Emitter configuration is mostly used in electronic circuits. This is because the emitter current is actually much higher than the base current. For the common Base config emitter current is the input current. So, the common Base config requires a large input current. In amplifiers, the signals to be amplified generally can't generate a large current. So, the common emitter configuration is mostly used because here the input current is the base current which is generally very low.

## Common Emitter characteristics:-

$$V_{CE} = V_{BE} + V_{CB}$$

$$\approx V_\gamma + V_{CB}$$


in FA mode

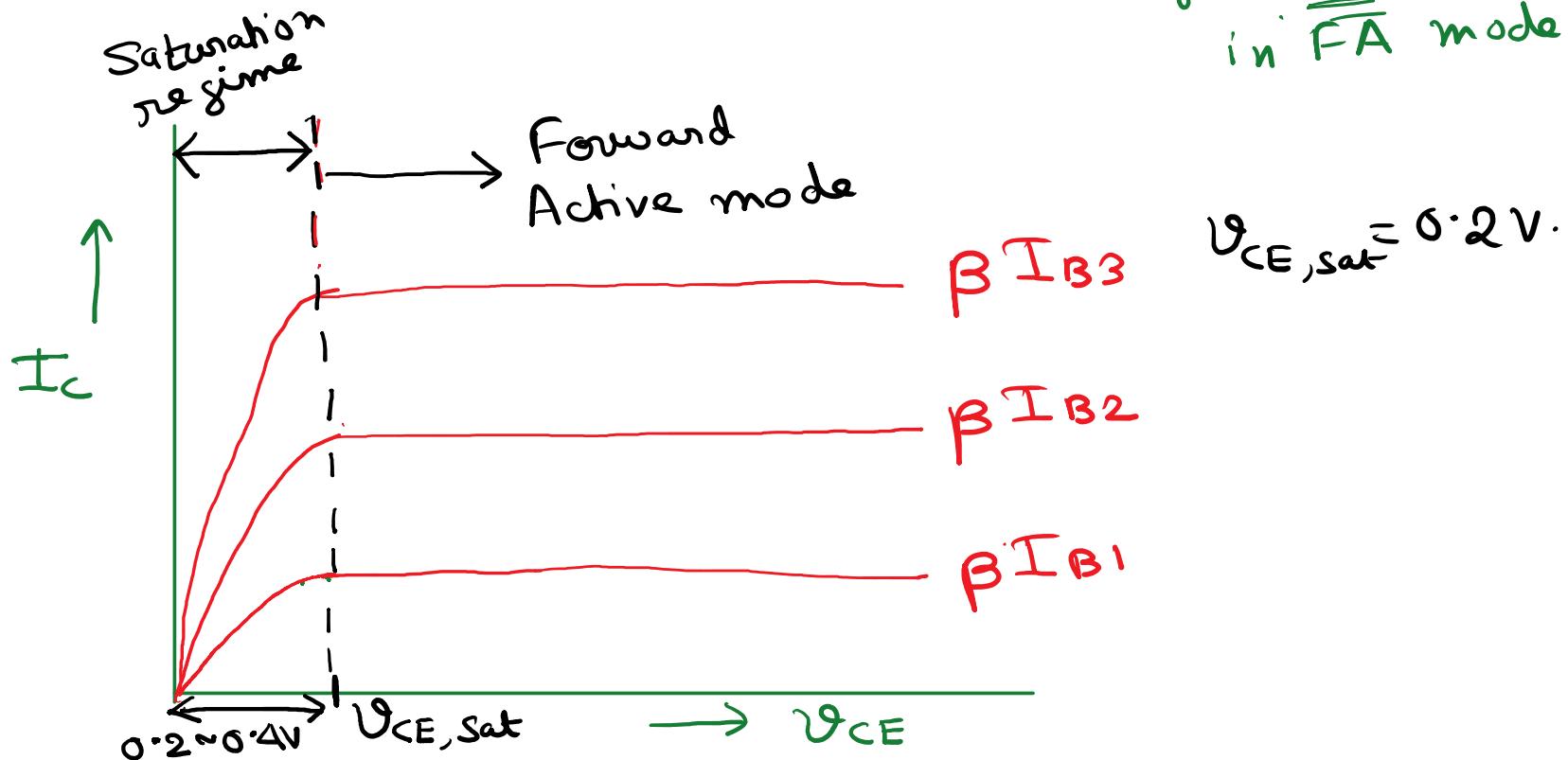


$$V_{CE,sat} = 0.2 \text{ V.}$$


In the Forward Active mode, the collector current does not depend on  $V_{CE}$  or  $V_{BE}$ . The collector current, in this case, only depends on the Base-to-emitter voltage or the emitter current or the Base current. The minimum value of  $V_{CE}$  for which the transistor is in Forward Active mode is denoted by  $V_{CE,\text{sat}}$ . Generally,  $V_{CE,\text{sat}}$  lies in the range of 0.2V to 0.4V. But we would mostly assume  $V_{CE,\text{sat}} = 0.2V$ .

Equivalent DC models:-

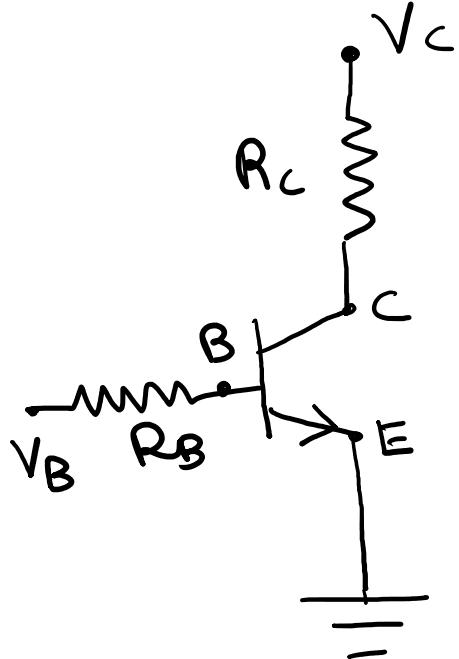


npn

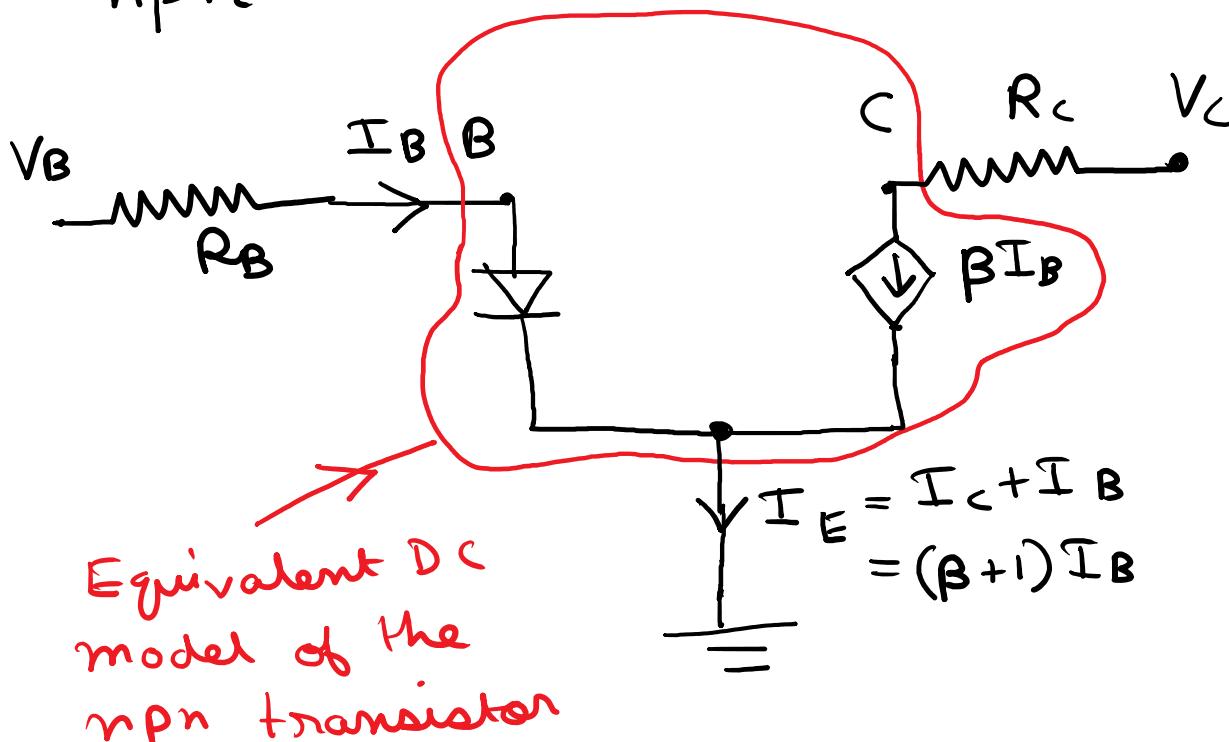


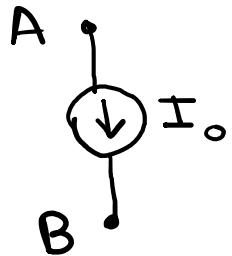


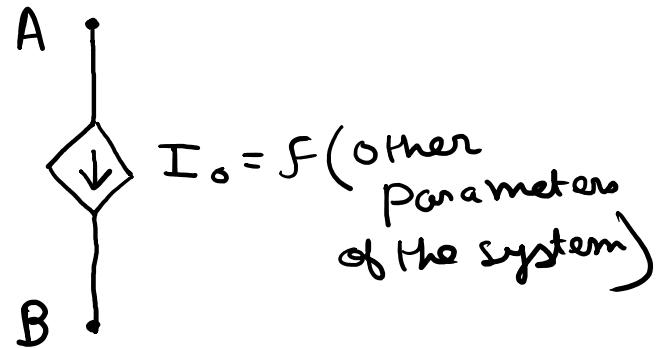Symbol for independent  
current source .



Dependent current  
source .

Equivalent DC model of a pnp transistor.

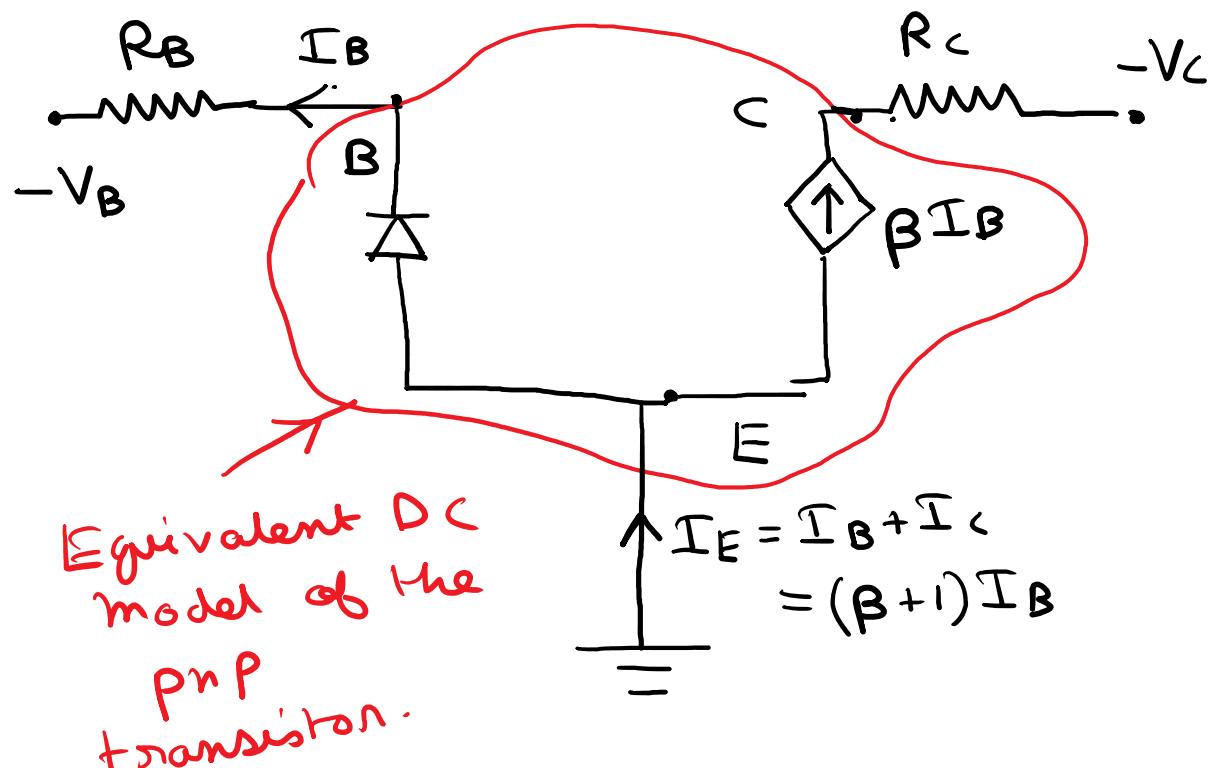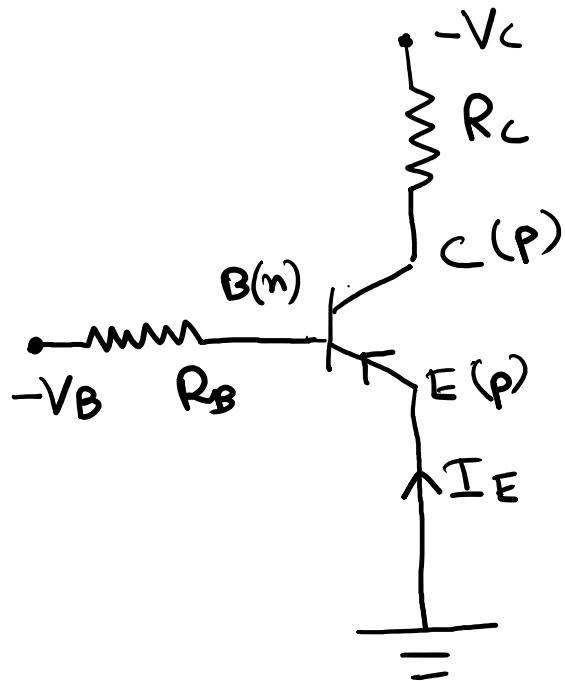

## Class - 18

Q: what is the value of  $V_I$ , such that

$$V_{CE} = 6V$$

A:

$$12V = 2.2k\Omega \times I_C + V_{CE}$$


$$\Rightarrow I_C = \frac{12 - V_{CE}}{2.2} \text{ mA}$$

$$= \frac{12 - 6}{2.2} \text{ mA} = 2.72 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{2.72 \text{ mA}}{30} \approx 0.09 \text{ mA}$$

In the Forward active mode,  $V_{BE} \approx V_{BE(on)} = 0.7V$
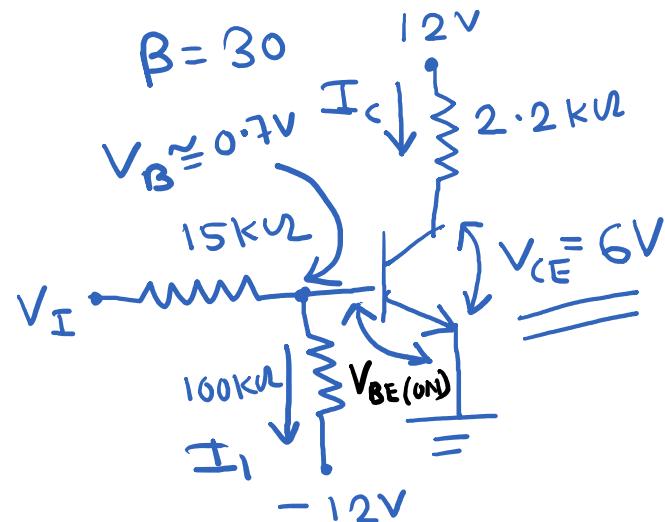
$$I_I = \frac{0.7V - (-12V)}{100k\Omega} = \frac{12.7}{100} \text{ mA} = 0.127 \text{ mA}$$



$$I_2 = \frac{V_I - V_B}{15\text{ k}\Omega}$$


$$= \frac{V_I - 0.7\text{ V}}{15\text{ k}\Omega} \quad \textcircled{1}$$

$$I_2 = I_1 + I_B$$

$$\begin{aligned} &= (0.127\text{ mA} + 0.09\text{ mA}) \\ &= 0.217\text{ mA} \quad \textcircled{2} \end{aligned}$$

$$\Rightarrow \frac{V_I - 0.7\text{ V}}{15\text{ k}\Omega} = 0.217\text{ mA} \quad (\text{from 1 and 2})$$
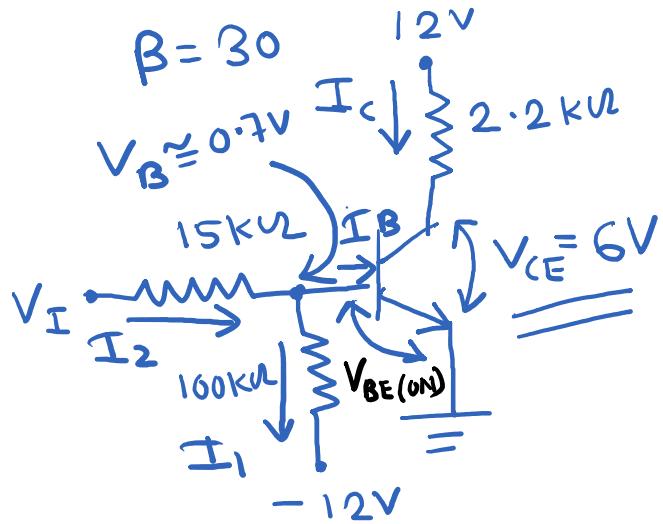
$$\Rightarrow V_I = 0.7\text{ V} + 15 \times 0.217\text{ V} = 3.955\text{ V}$$



$$Q: V_o = ?$$

$$A: V_{CB1} = 0 = V_{CB2}$$


The two transistors are therefore operating in forward active mode.

$$10I \approx I_s \exp\left\{\frac{V_{BE1}}{V_T}\right\} \quad (1)$$

$$I \approx I_s \exp\left\{\frac{V_{BE2}}{V_T}\right\} \quad (2)$$

$$10 = \exp\left\{\frac{V_{BE1} - V_{BE2}}{V_T}\right\} = \exp\left\{-\frac{(V_{E1} - V_{E2})}{V_T}\right\}$$
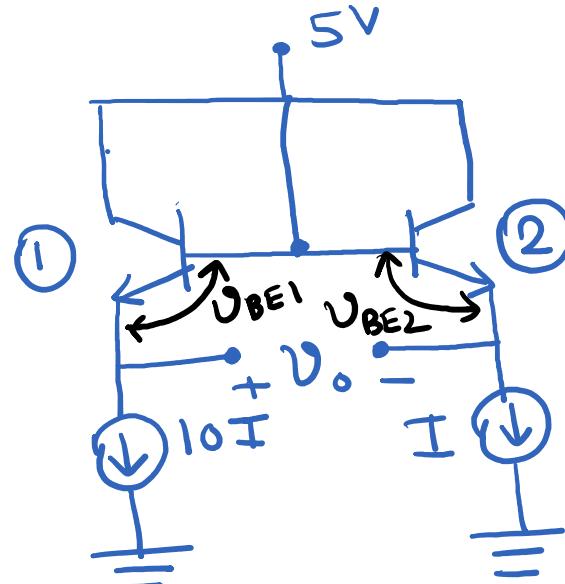
$$\Rightarrow 10 = \exp\left\{-\frac{V_o}{V_T}\right\} \Rightarrow V_o = -V_T \ln 10 = \frac{kT}{q} \ln 10$$



## Amplification:

$$V_{in} = V_{BE(on)} + I_B R_B$$


$$= I_B R_B (\because V_{BE(on)} = 0)$$

$$\Rightarrow I_B = \frac{V_{in}}{R_B}$$

$$I_C = \beta I_B = \frac{\beta V_{in}}{R_B}$$

$$V'_C = V_C - I_C R_C$$

$$= V_C - \frac{\beta V_{in} R_C}{R_B}$$

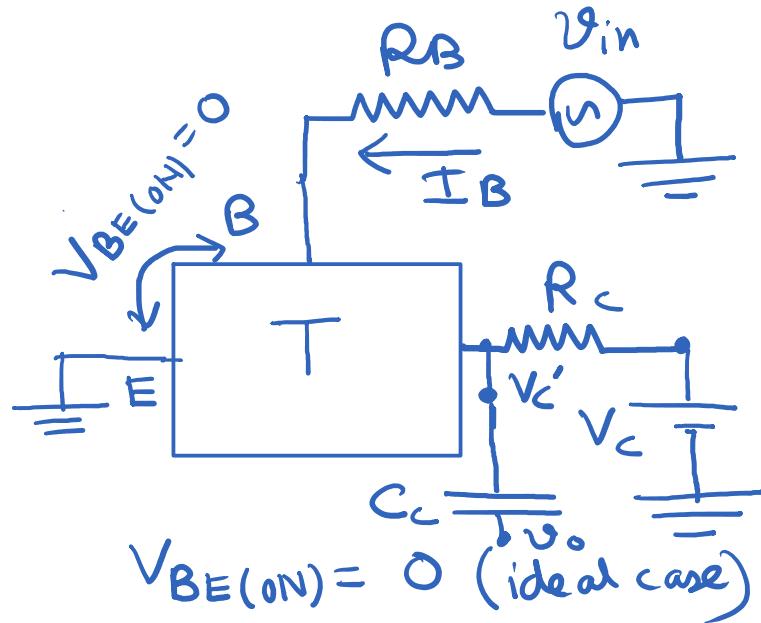

$$= V_C - \underbrace{\frac{\beta R_C}{R_B} V_{in}}_{AC}$$



$$V_o = \text{ac component of } V'_C$$

$$= -\frac{\beta R_C}{R_B} V_{in}$$

$$v_o = -\beta \frac{R_c}{R_B} v_{in}$$

The negative sign denotes that the output waveform is shifted in phase by  $180^\circ$  with respect to the input waveform.

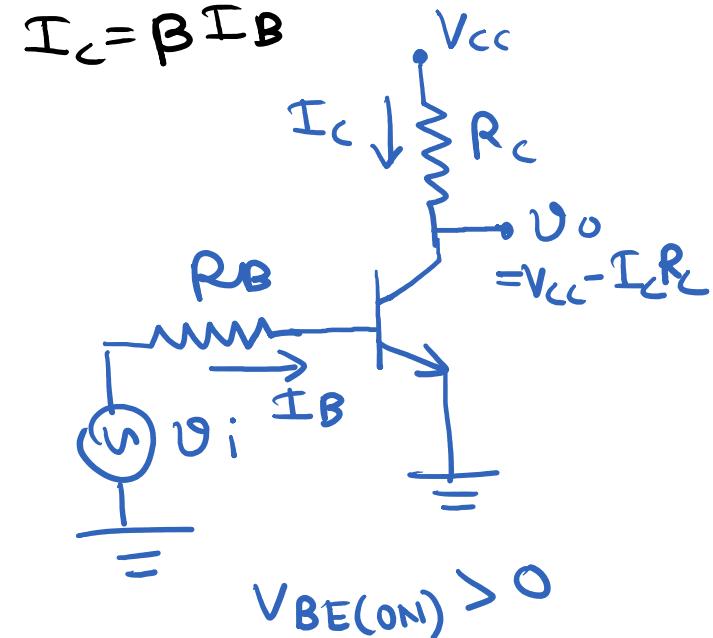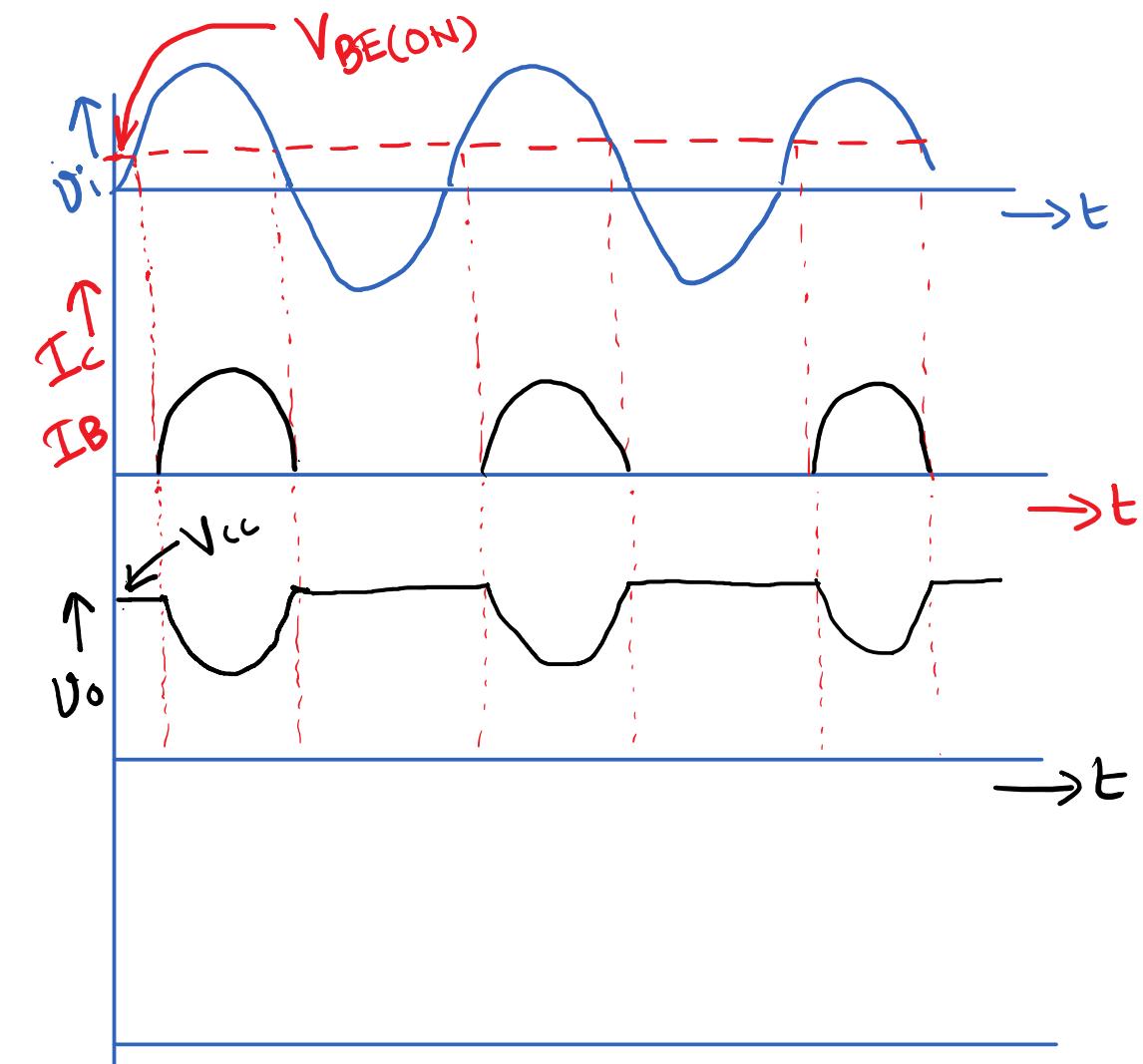If  $\beta \frac{R_c}{R_B} > 1$ , then we get a amplified but opposite phase version of the input signal at the output. For a good amplifier  $\beta \frac{R_c}{R_B} \gg 1$ .



$$V_{BE(ON)} > 0$$



$$I_B \approx \frac{V_i - V_{BE(ON)}}{R_B}$$

if  $V_i > V_{BE(ON)}$

$$I_B \approx 0 \text{ if } V_i < V_{BE(ON)}$$

If  $v_i$  is directly connected to the Base through a resistor, then we do not get a replica or a scaled version of the input signal at the output.

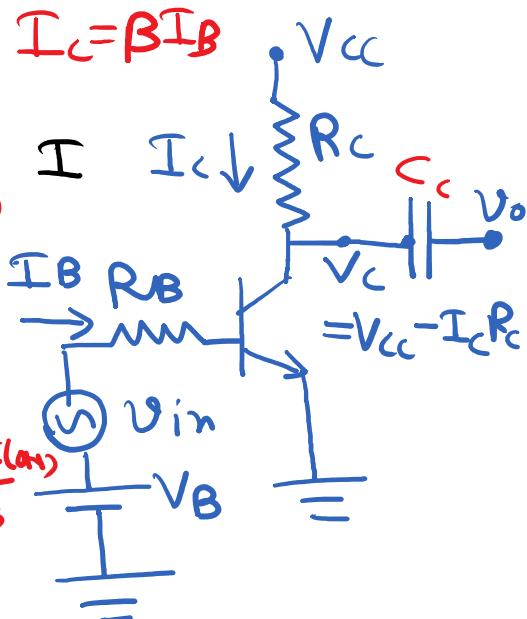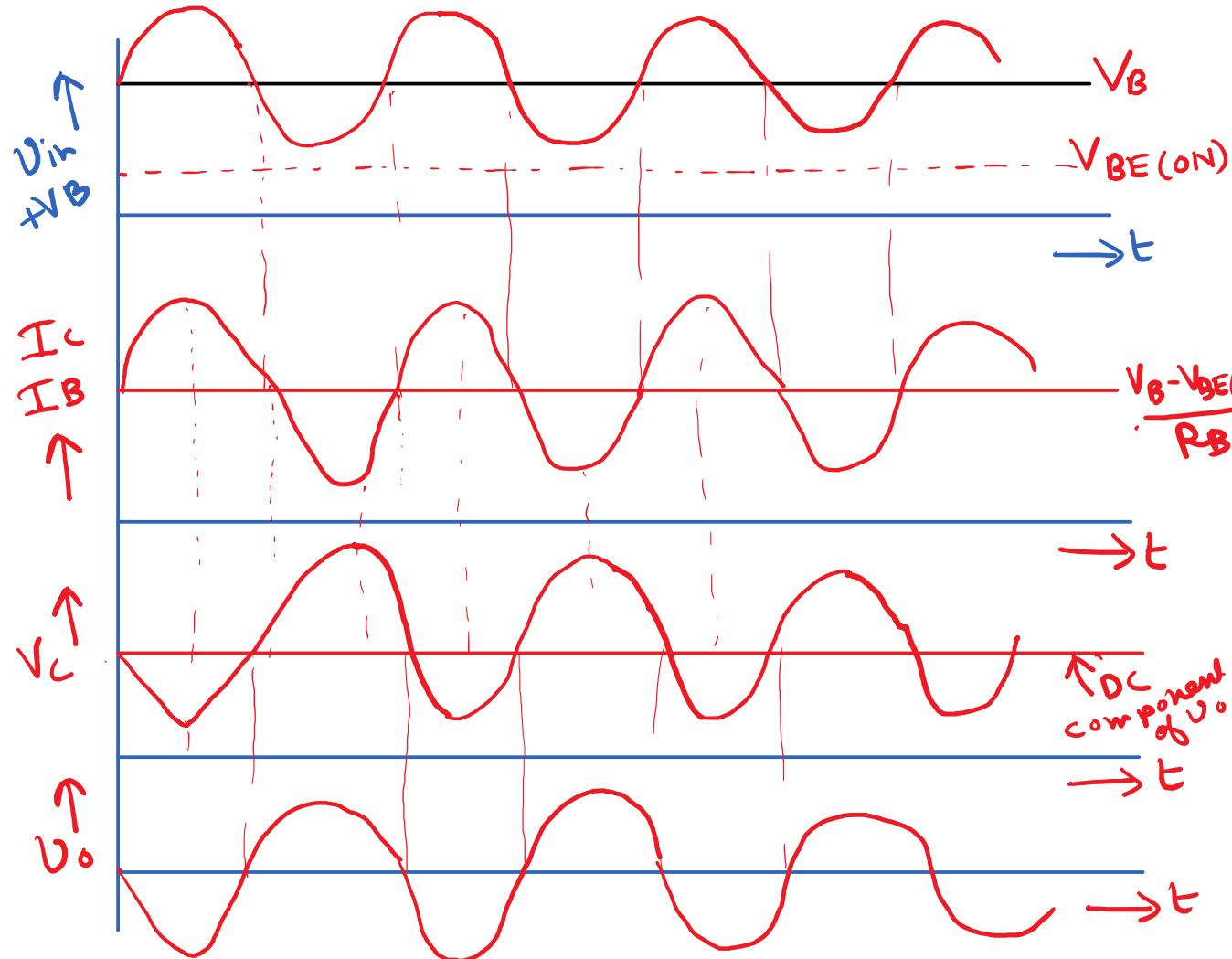In most of the cases, the amplitude of  $v_i$  is less than  $V_{BE(on)}$ . The amplitude of  $v_i$  is of the order of tens to hundreds of millivolts. In these cases, the transistor would never turn-on because the input voltage is always less than  $V_{BE(on)}$ . So, there is no Base current. So, we get a constant voltage at  $v_o$ .



$$\begin{aligned}
 I_B &\approx \frac{V_B + V_{in} - V_{BE(ON)}}{R_B} \\
 &= \left\{ \frac{V_B - V_{BE(ON)}}{R_B} \right\}_{DC} + \overbrace{V_{in}}^{\text{AC}}
 \end{aligned}$$

$$I_C = \frac{V_B - V_{BE(ON)}}{R_B} + \frac{V_{in}}{R_B}$$

• DC AC

The process of surpassing the cut-in voltage of the Base-emitter junction by applying a DC voltage in series with the input signal is called Biasing <sup>or DC biasing</sup> of the transistor. Both  $V_{ce}$  and  $V_B$  are a part of DC biasing of the transistor. DC biasing of the transistor is actually necessary for proper amplification and to get a scaled replica of the input signal at the output.

Q:

Class - 19

$$V_{CE} = 2.5V, I_C = 5mA, \beta = 120$$

$$R_B, R_C = ?$$

$$A: V_{CE} = 2.5V$$

$$V_{RC} = 5V - V_{CE} = 5V - 2.5V = 2.5V$$

$$I_C = \frac{V_{RC}}{R_C} = \frac{2.5V}{R_C} = 5mA$$

$$\Rightarrow R_C = \frac{2.5V}{5mA} = 0.5k\Omega$$


$$I_B = \frac{I_C}{\beta} = \frac{5mA}{120} = \frac{1}{24}mA$$

$$5V = I_B R_B + V_{BE(on)} = I_B R_B + 0.7V$$

$$\Rightarrow R_B = \frac{5V - 0.7V}{I_B} = \frac{5V - 0.7V}{1/24mA} = 4.3 \times 24 k\Omega = 103.2 k\Omega$$

Fixed Biasing Scheme

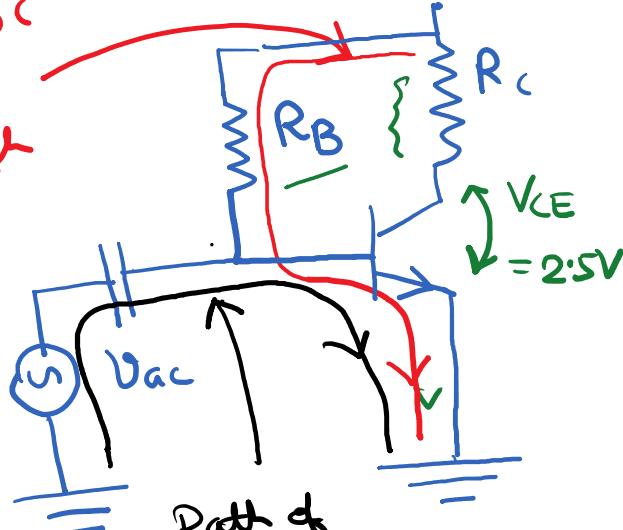Path of DC current flow through the base-emitter junction



Path of AC current flow through the base to emitter junction

$R_B$  basically controls the  $^{DC}$  base current, which in turn controls the  $^{DC}$  collector current ( $I_C = \beta I_B$ ). So to get a particular value of  $I_C$ , we need to manipulate  $R_B$ .

Once we get a desired DC value of the collector current, we can manipulate  $R_C$  to manipulate the DC value of the collector to emitter voltage.

If  $V_I < V_{BE(ON)}$ ,  $I_B = 0$ ,  $I_C = 0$ ,  $V_o = V_{CC}$

If  $V_I > V_{BE(ON)}$

$$\textcircled{1} I_B \cong \frac{V_I - V_{BE(ON)}}{R_B}$$


$$\textcircled{2} I_C = \beta I_B = \beta \frac{(V_I - V_{BE(ON)})}{R_B}$$

$$\begin{aligned} \textcircled{3} V_o &= V_{CC} - I_C R_C = V_{CC} - \beta \frac{R_C}{R_B} (V_I - V_{BE}) \\ &= \left( V_{CC} - \beta \frac{R_C}{R_B} V_{BE(ON)} \right) - \beta \frac{R_C}{R_B} V_I \end{aligned}$$

$$\textcircled{4} \frac{dV_o}{dV_I} = -\beta \frac{R_C}{R_B}$$


For amplification,  $\left| \frac{dV_o}{dV_I} \right| > 1$   
 $\Rightarrow \beta R_C / R_B > 1$

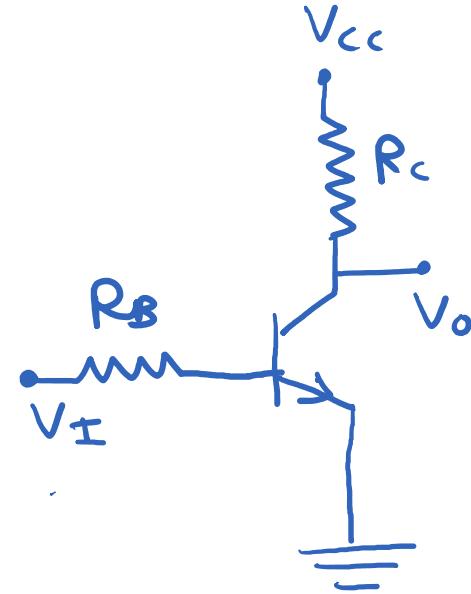
$V_I > V_{BE(ON)}$   
 $V_o > V_{CE,sat}$   
 Valid in Forward Active mode.




The output voltage varies with the input voltage only in this regime. So, for any value of the input signal, the total voltage at the input must be confined within this regime: only in this regime the transistor is in the forward active mode.

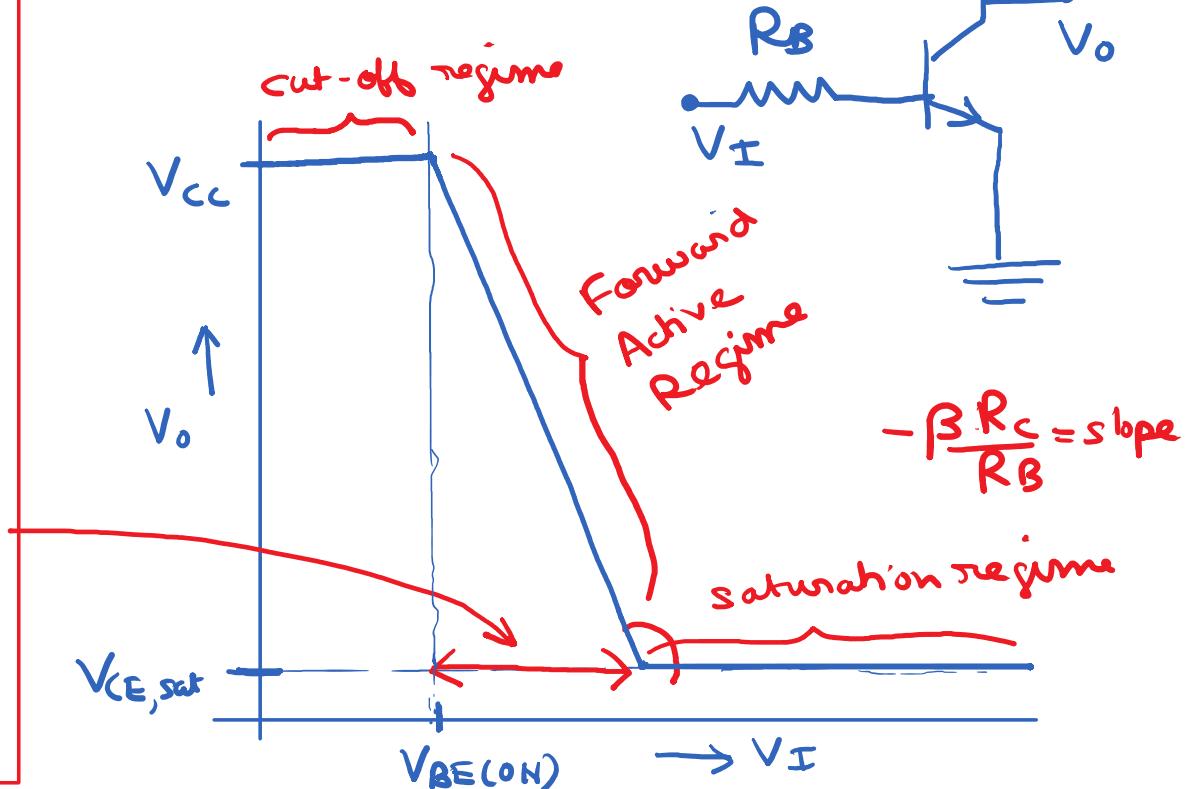
Transfer characteristics of the transistor circuit



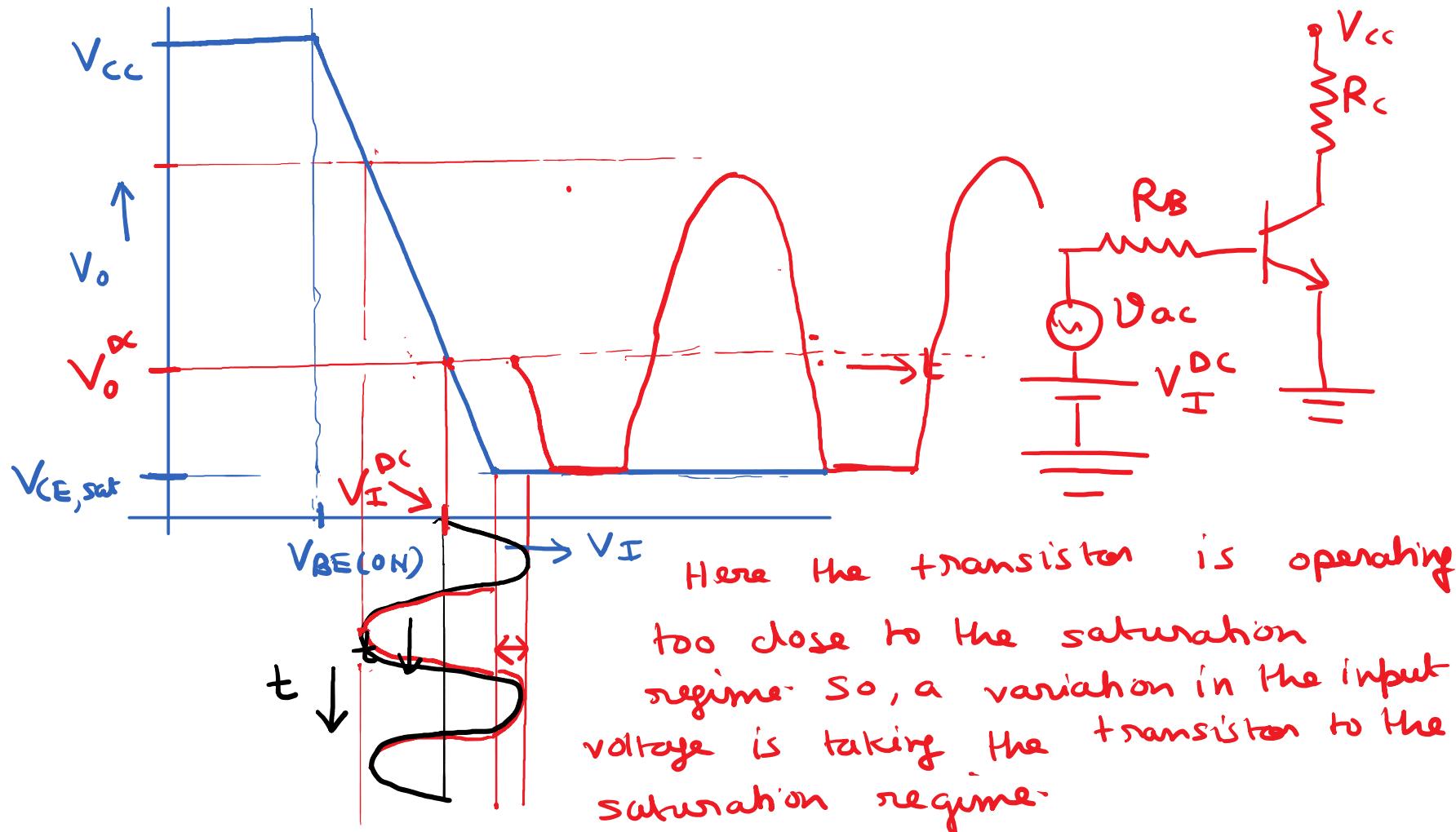

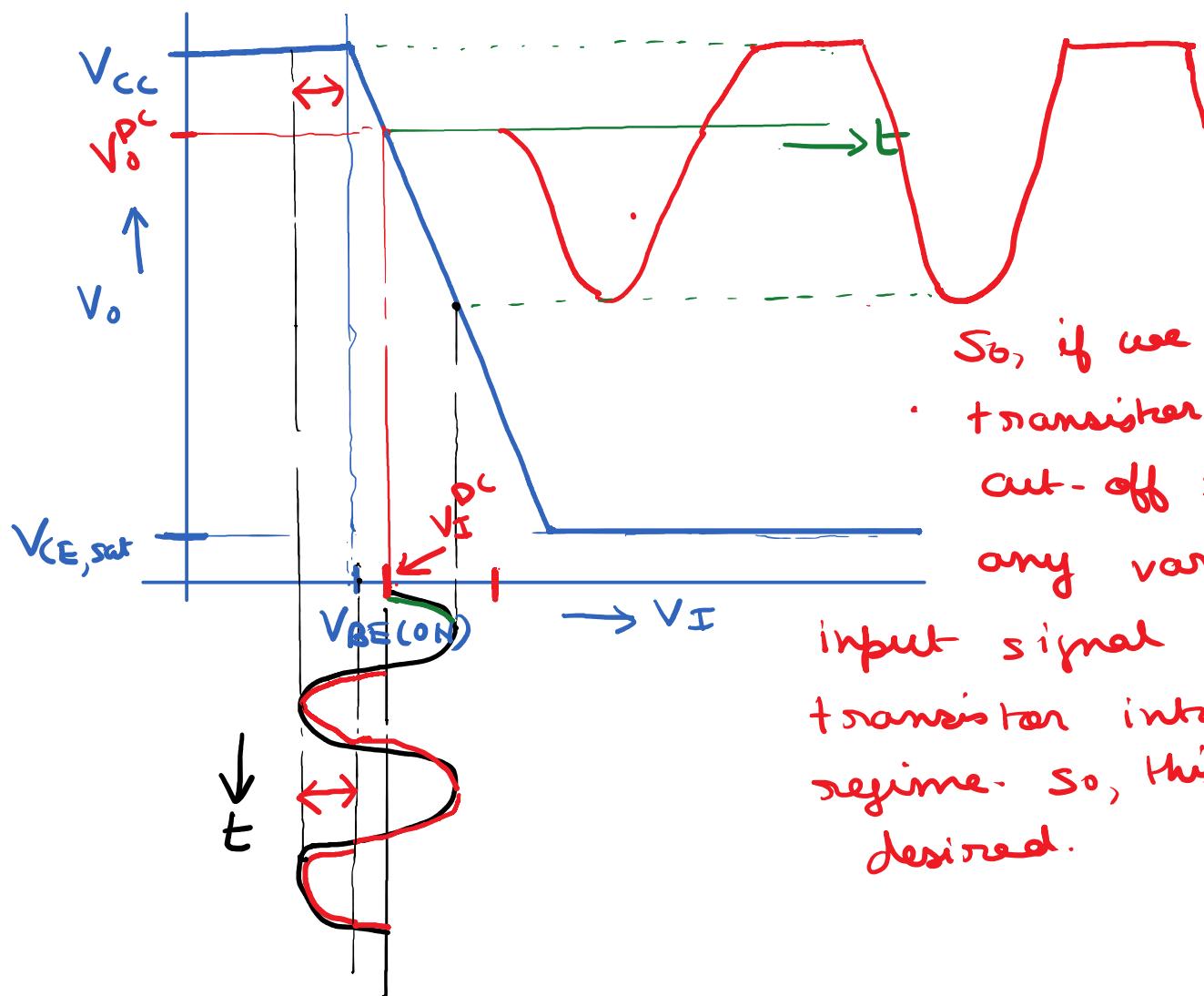

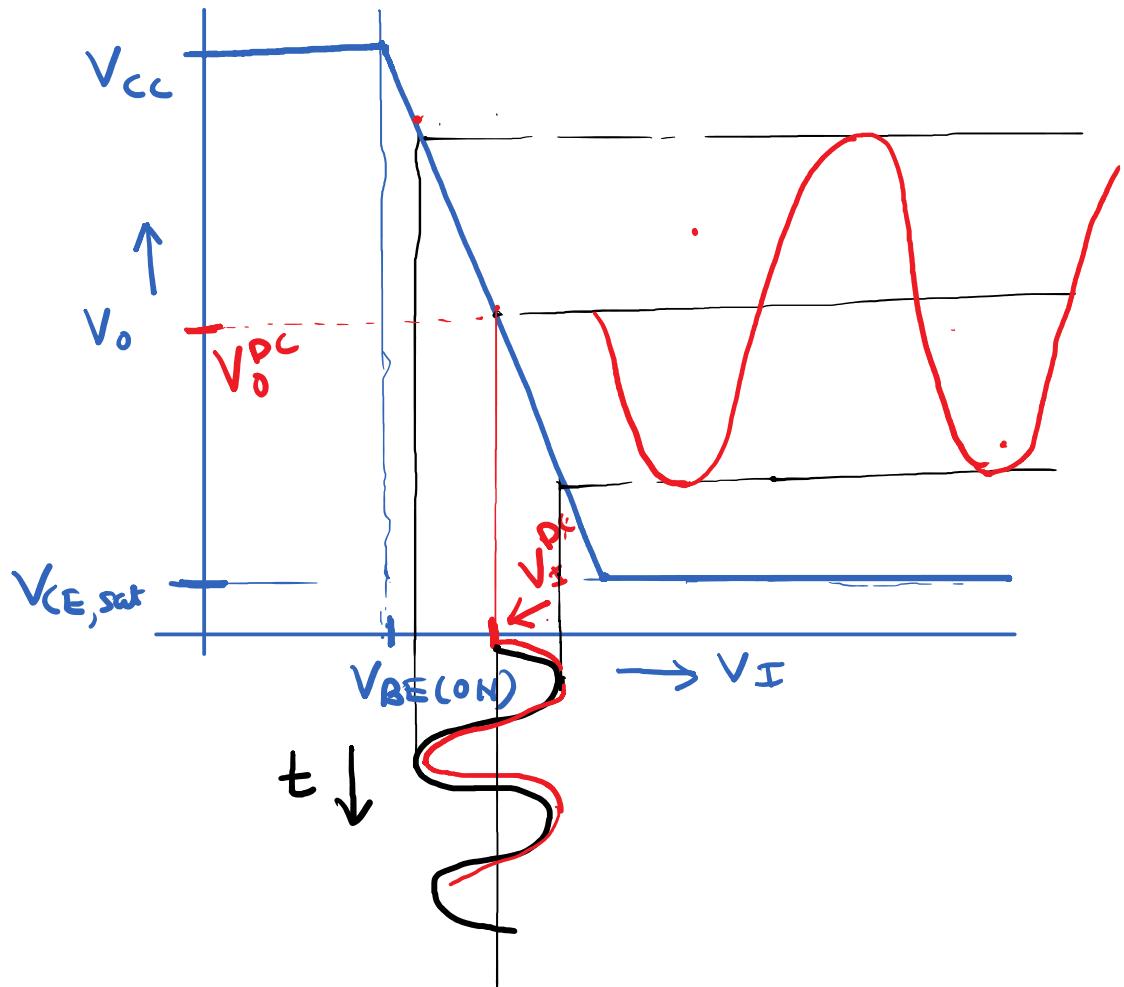So, if we bias the transistor close to the cut-off regime, then any variation of the input signal may take the transistor into the cut-off regime. So, this is not desired.



To ensure that the transistor is biased in the Forward Active mode for the entire range of variation of the input signal, a suitable value of  $V_I^{DC}$  is somewhere near the midpoint of the Forward active regime.