

# INDIAN INSTITUTE OF TECHNOLOGY

Date:    Feb 2013, FN/AN, Time: 2 Hrs., Full Marks: 60, No. of Students : 660 (Non-ECE branches); Mid Spring Semester,  
Sub. No.: EC21101, Sub. Name: Basic Electronics

## Instructions

- All waveform sketches / diagrams must be neatly drawn and clearly labeled. Answers must be brief and to the point.
- The final answers (numerical values with unit) should be underlined or enclosed within box with unit.
- For every Question No., start your answer from a new page.
- Avoid writing answers of the various parts of a single question at different locations in your answer-script.
- Given parameters which you might require: mass of electron:  $9.11 \times 10^{-31}$  kg, Boltzmann constant :  $1.38 \times 10^{-23}$  J/K, charge of electron :  $1.6 \times 10^{-19}$  C
- For any value related to any device parameter or circuit parameter, which you may find not given with a problem, assume suitable value for such parameter.
- **Answer any FOUR questions (out of SIX)**

1A. For the circuit shown in Fig. 1 consider  $V_{PS}=16$  V,  $R_1=20$  K $\Omega$ ,  $R_2=10$  K $\Omega$ ,  $V_T=0.7$  V, and  $v_i=0.5\sin\omega t$ . Determine the dc and ac output voltage as well as the diffusion capacitance considering the following two conditions

- when  $R_2$  decreases from 10 K $\Omega$  to 5 K $\Omega$
- when  $V_{PS}$  increases from 16 V to 20 V

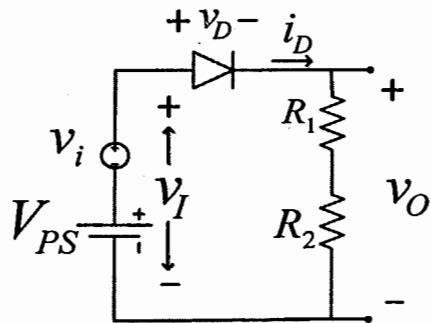


Fig. 1.

1B. Calculate the junction capacitance for Ge pn junction when 6 V reverse voltage is applied. Doping concentrations of  $N_a=5 \times 10^{16}$  /cm<sup>3</sup>,  $N_d=2 \times 10^{15}$  /cm<sup>3</sup> and let  $C_{j0}=0.8$  pF. Given the value of coefficient for Ge (B) is  $1.66 \times 10^{15}$  cm<sup>-3</sup>K<sup>-3/2</sup> and band gap ( $E_g$ ) is 0.66 eV at 300 K.

(8+7)

2A. For the circuit in Fig. 2 the cut in voltage of diode is  $V_T=0.7$  V. Plot the  $v_o$  versus  $v_i$ .

Given:  $R_1=2$  k $\Omega$ ,  $R_2=R_3=1$  k $\Omega$ ,  $V_1=15$  V

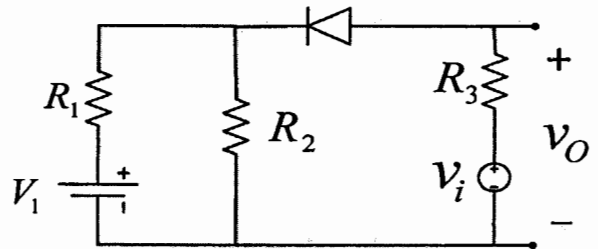


Fig. 2

2B. In the voltage regulator shown in Fig. 3, calculate the dissipated power in the Zener diode.

Given:  $V_1=50$  V,  $R_1=150$   $\Omega$ ,  $V_Z=15$  V (assume  $R_Z=0$ ) and  $R_2=75$   $\Omega$


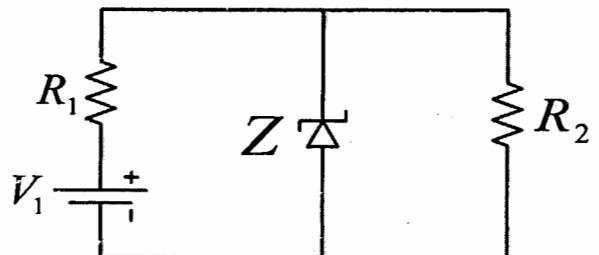



Fig. 3

(8+7)

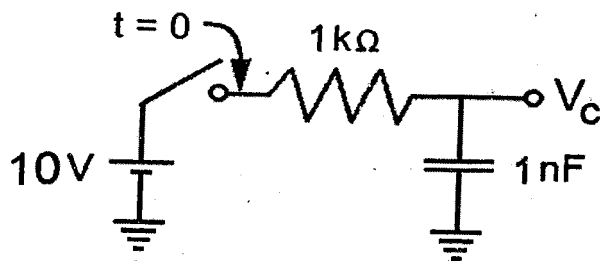
3A. In the circuit shown Fig. 4, the switch is closed at  $t = 0$ . Calculate the time  $t$  when the output voltage is 9 V.



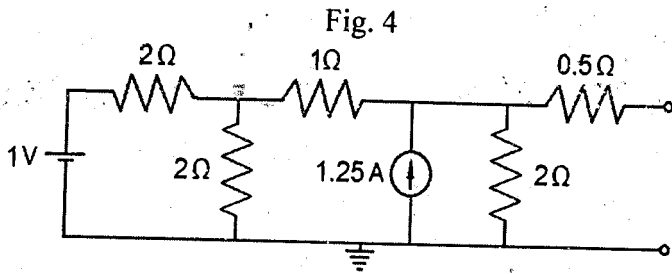3B. What is the equivalent Thevenin's voltage and Thevenin's resistance of the circuit shown in Fig. 5?




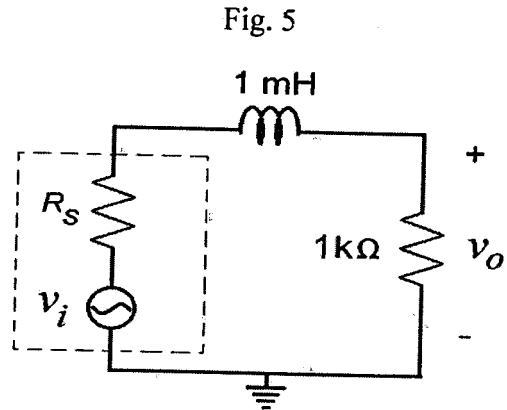3C. In the circuit shown in Fig. 6 a sinusoidal signal generator with internal resistance  $50\ \Omega$  is connected to a series LR circuit. If  $v_i = 12 \sin 2\pi ft$ , calculate the linear frequency at which the rms value of the output voltage  $v_o$  is 6 V.




4A. In the circuit shown in Fig. 7,  $v_{IN} = 5 \sin \omega t$  [volt],  $V_b = 2V$  and  $V_f = 0.7V$ .

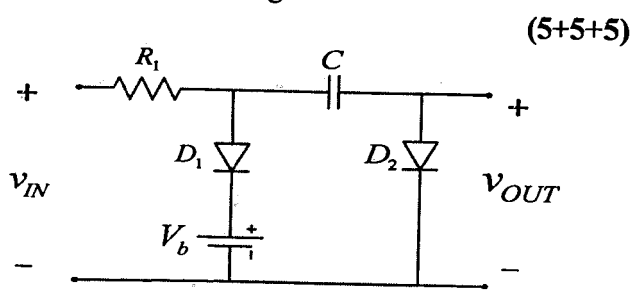- (i) Draw the output waveform  $v_{OUT}$  with respect to  $t$ .
- (ii) Draw the transfer characteristics ( $v_{OUT}$  vs  $v_{IN}$ ).



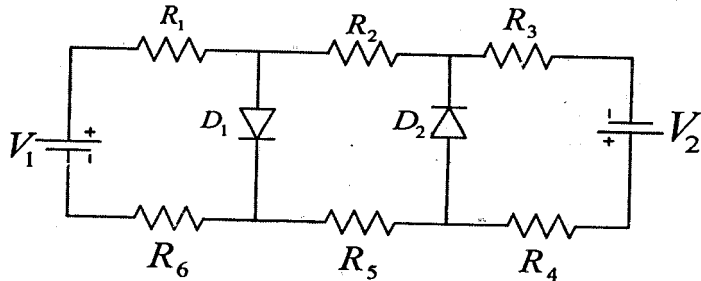B. In the circuit shown in Fig. 8, find out  $I_1$  (current through D1) and  $I_2$  (current through D2).

Given:  $R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = 1k\Omega$   
 $V_1 = 5V$ ,  $V_2 = 3V$  and  $V_f = 0.7V$  (for both the diodes)



(8+7)

5A. In the circuit shown in Fig. 9, Find  $R_2$  and  $R_4$ .

Given:  $V_{DD}=5V$ ,  $R_1=6k\Omega$ ,  $R_3=4k\Omega$ ,  $I_{DS}=0.25\text{ mA}$ ,  
 $V_{DS}=3.5V$ ,  $W=20\text{ }\mu\text{m}$ ,  $L=1\text{ }\mu\text{m}$ ,  $\mu_n C_{ox}=100\text{ }\mu\text{A/V}^2$ ,  
 $V_{th}$  (threshold voltage)  $=1\text{ V}$ .

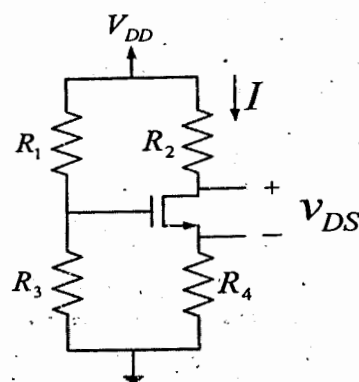


Fig.9

5B. In the circuit shown in Fig. 10, Find  $I_1$  and  $I_2$ .

Given:  $R=3k\Omega$ ,  $V_{DD}=5V$ ,  $W_1=20\text{ }\mu\text{m}$ ,  $W_2=60\text{ }\mu\text{m}$ ,  
 $L_1=L_2=1\text{ }\mu\text{m}$ ,  $\mu_n C_{ox}$  (for both  $M_1$  and  $M_2$ )  $=100\text{ }\mu\text{A/V}^2$ ,  $V_{th}$  (threshold voltage)  $=1\text{ V}$  (for both  $M_1$   
and  $M_2$ ).

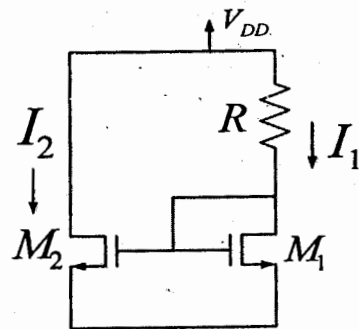


Fig. 10

(8+7)

6A. In a hypothetical structure, made with n type Si and n type Ge, shown in Fig. 11, find  $\rho$  (resistivity) of Si and Ge. Hence find out the equivalent resistance.

Given:  $N_D(\text{Si})=10^{16}/\text{cm}^3$ ,  $N_D(\text{Ge})=10^{15}/\text{cm}^3$ ,  $\mu_n(\text{Si})=1350\text{ cm}^2/\text{V-sec}$ ,  $\mu_n(\text{Ge})=3800\text{ cm}^2/\text{V-sec}$ ,  $A$  (cross-section)  $=0.1\text{ mm}^2$ ,  $L_1=1\text{ mm}$ ,  $L_2=0.5\text{ mm}$ .

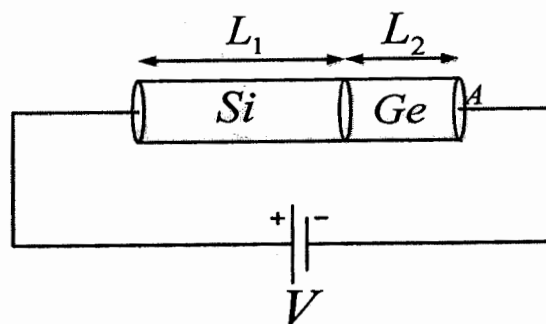


Fig. 11

6B. In a device, suppose  $i_D = K(v_D^3 + 2v_D^2 + 3v_D + 4)$ , find out small signal resistance of the device. Where,  $K$ -constant,  $i_D$  and  $v_D$  are total instantaneous values.

(8+7)