
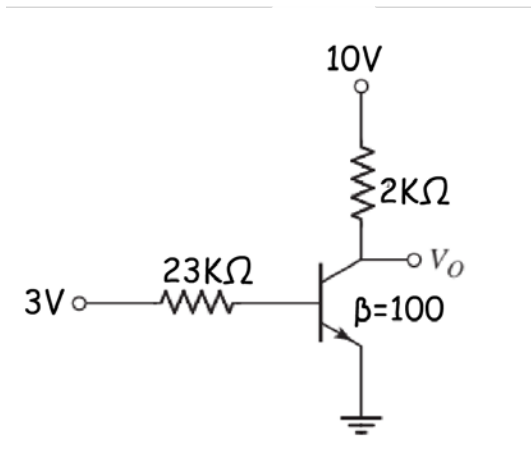


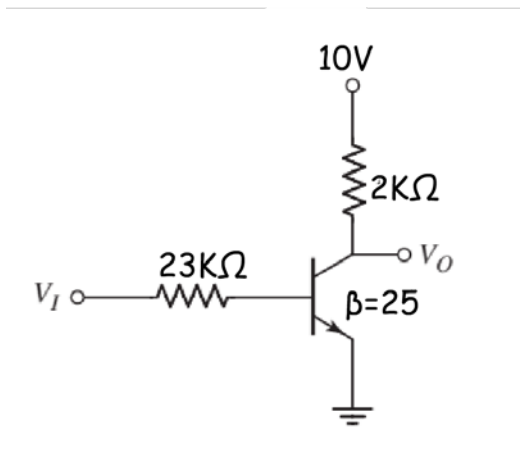1. For a given transistor circuit, the value of V_o is approximately given by _____ Volts.




Ans: Any value in the range of 0 and 0.4

2. In the circuit shown below, the input waveform V_I is given by a square pulse of amplitude 3V and zero mean value, that is the input oscillates between +3V and -3V. The mean value of the output V_o in that case is given by _____ Volts




Ans: 7.5

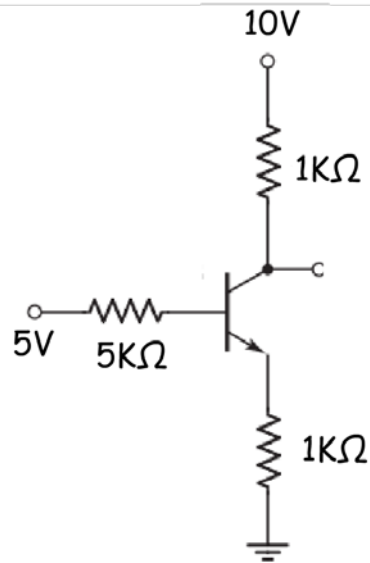3. In the circuit shown below, if β of the transistor changes from 100 to 150, then the percentage variation in collector current is _____ %




Ans: Any value in the range of 1.85 and 2

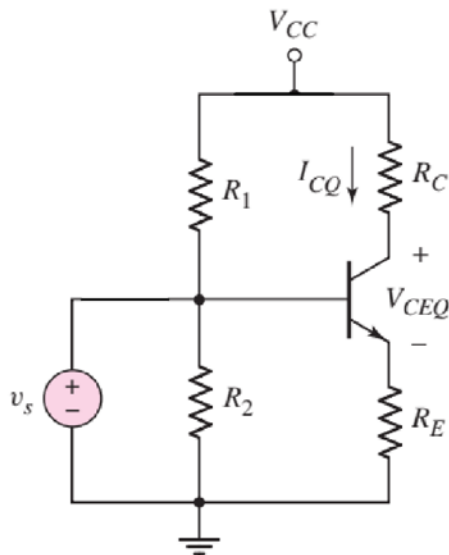4. In the Fig. below, v_s and V_{CC} are DC voltage sources. If $V_{CC} = 20V$, $v_s = 5V$, $R_1 = R_2 = R_E = R_C = 2K\Omega$ and $\beta = 50$, then the value of V_{CEQ} is given by _____ Volts




Ans: Any value in the range of 11 and 12

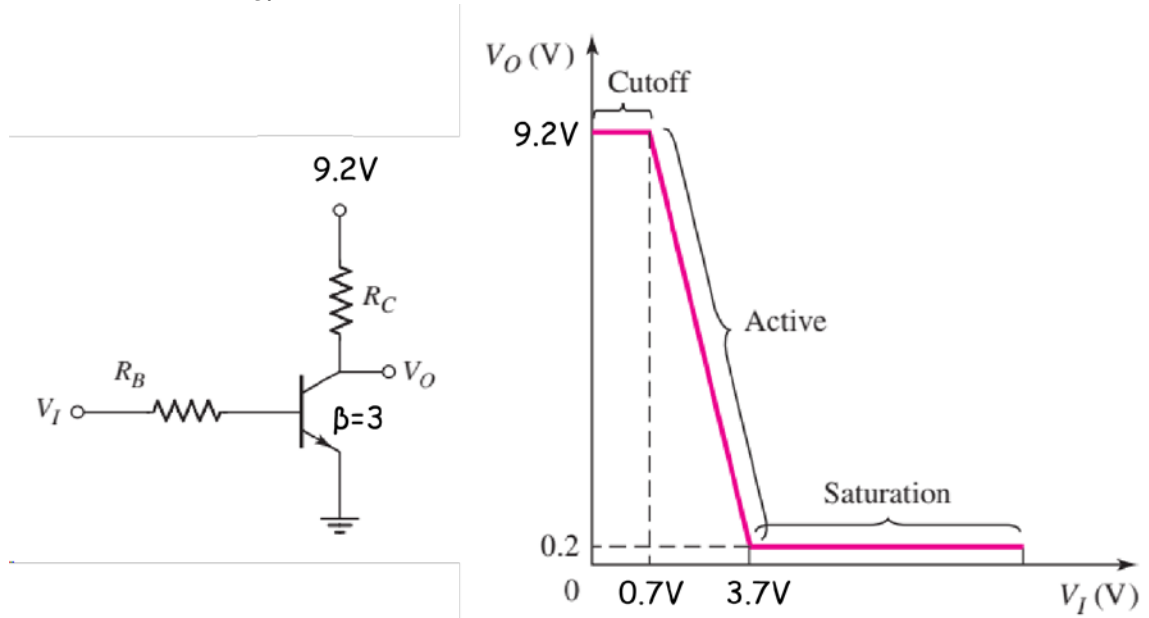5. If the following circuit on the left has the input-output voltage graph on the right, then the value of R_C/R_B is _____




Ans: 1

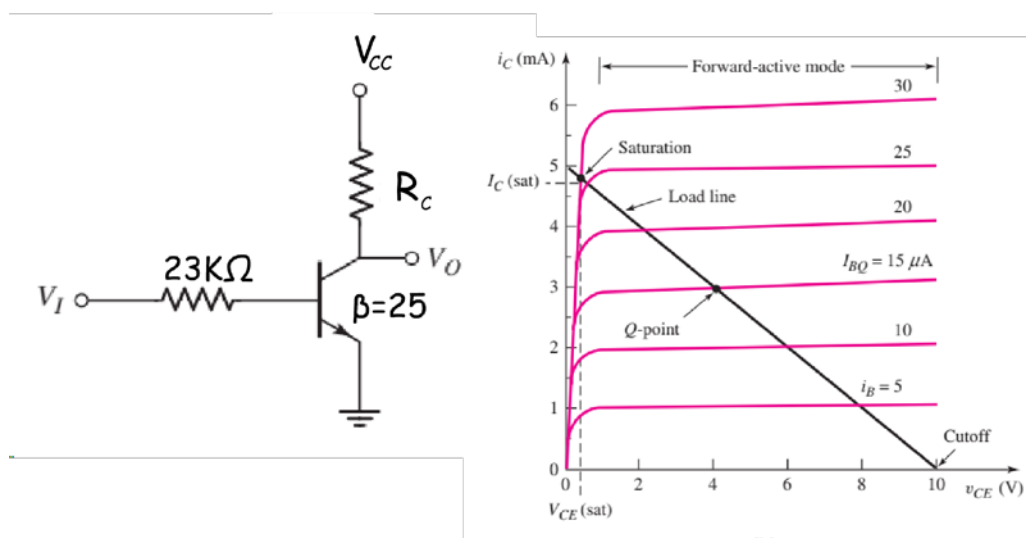6. For the following circuit in the left and the load line on the right, the value of V_{CC} is _____ Volts



Ans: 10

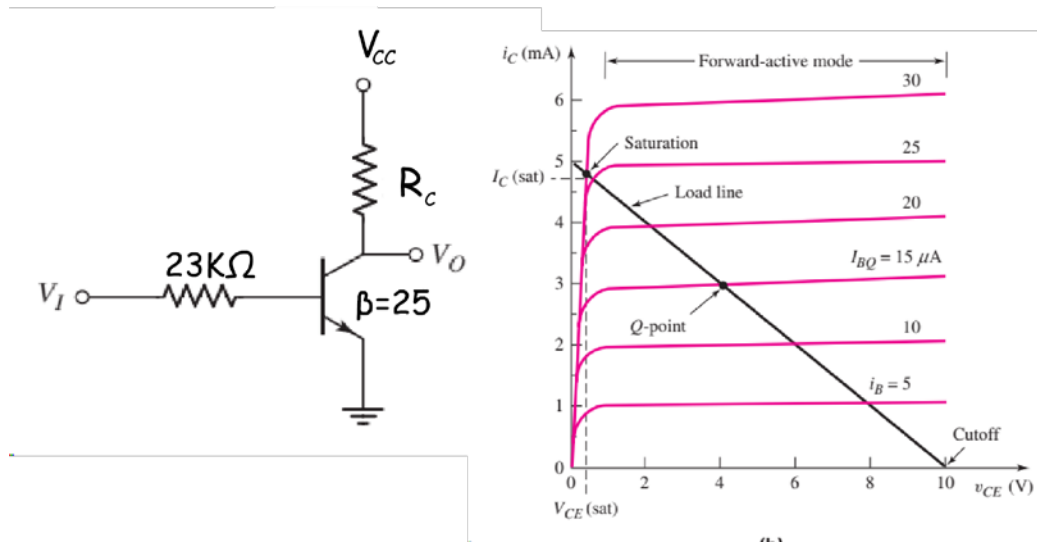7. For the following circuit in the left and the load line on the right, the value of R_C is _____ $k\Omega$




Ans: 2

8. If $\beta = 4$ for a transistor and the base current in the forward active mode is $I_B = 20\mu A$, then the emitter current is given by **100** _____ μA
9. For a BJT, $\beta = 1$. If β is doubled, then the emitter current will increase by a factor of **1.5** _____
10. For common emitter circuit with a fixed bias, $R_B = 220 k\Omega$, $R_C = 2k\Omega$, $V_{CC} = 10$ V, $V_{BE}(on) = 0.7$ V, and $\beta = 200$. If the input voltage applied at the base terminal is 4 V, then the power dissipated in the transistor is _____ mW.

Ans: Any value between 12 to 13


11. For common emitter circuit with a fixed bias, $R_B = 220 k\Omega$, $R_C = 2k\Omega$, $V_{CC} = 10$ V, $V_{BE}(on) = 0.7$ V, If the input voltage applied at the base terminal is 8 V and $V_{CE}(sat) = 0.2$ V, then value of common-emitter current gain, β is **74** _____ so that the transistor is now set into the forward active region.

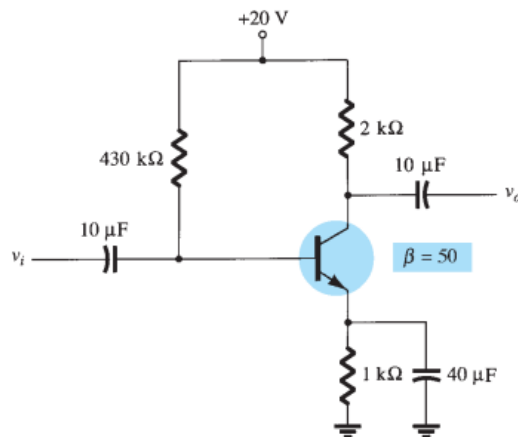12. For the given circuit, the output voltage (V_{CE}) is _____ V




Ans: Any value between 13.9 and 14.2

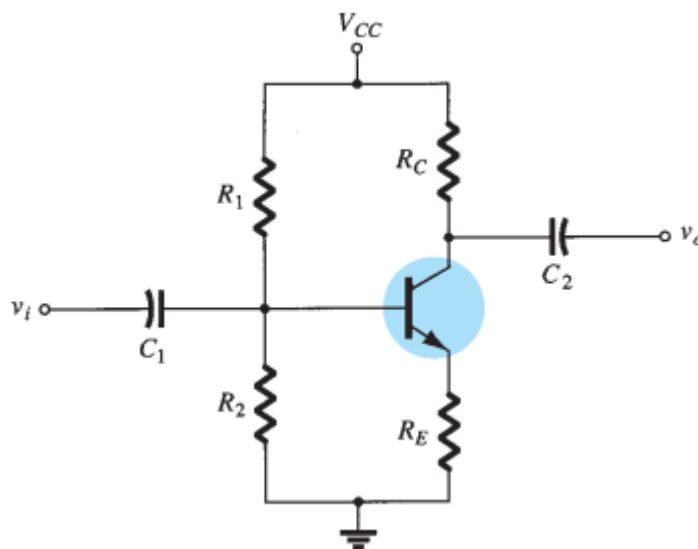13. For the circuit given below, $V_{CC}=10\text{ V}$, $R_1=56\text{ k}\Omega$, $R_2=12.2\text{ k}\Omega$, $R_C=2\text{ k}\Omega$, $R_E=0.4\text{ k}\Omega$, $V_{BE(on)}=0.7\text{ V}$, and $\beta=100$. If the $V_{CEQ}=0.5 V_{CC}$, the collector current at the Q-point will be _____ mA.



Ans: Any value in the range of 2.0 and 2.1

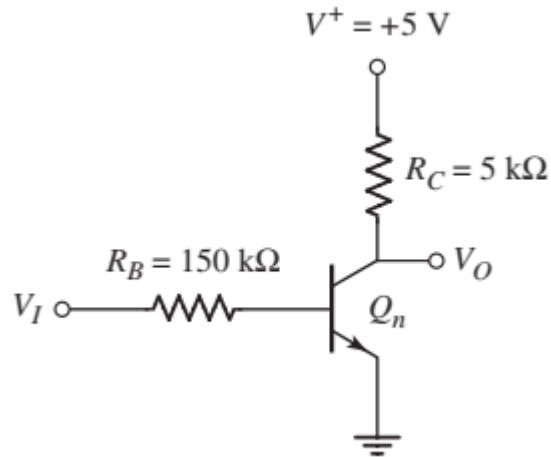14. For the given circuit, the transistor goes into saturation mode if the input voltage is greater than 1.9 V. Assume $\beta = 120$, $V_{BE}(\text{on}) = 0.7$ V and $V_{CE}(\text{sat}) = 0.2$ V and the Early voltage is infinite.



15. For the given circuit, the transistor will be in forward active mode if the input voltage is less than 1.9 V. Assume $\beta = 120$, $V_{BE}(\text{on}) = 0.7$ V and $V_{CE}(\text{sat}) = 0.2$ V and the Early voltage is infinite.

